

# Circuit Theorems

## 4.1 Introduction

In this chapter, several important theorems related to electric circuits are discussed: superposition principle, source transformation, Thévenin's theorem, Norton's theorem, and maximum power transfer.

If a circuit contains more than one source, the circuit can be analyzed by summing the response from each source with all other sources deactivated. This is called the *superposition principle*. Deactivating a voltage source is equivalent to short-circuiting it, and deactivating a current source is equivalent to open-circuiting it. The superposition principle reveals the contribution of each source to the voltages and currents in the circuit. It makes it easier to interpret the response of the circuit because we can trace the source of the response.

A voltage source with a series resistor is interchangeable with a current source in parallel to a resistor. This is called *source transformation*. The resistance value of both circuits is the same. The source transformation can be used to simplify the given circuit to find the desired voltages and currents.

According to Thévenin's theorem, a given circuit is equivalent to a voltage source  $V_{th}$  and a series resistor  $R_{th}$  between terminals  $a$  and  $b$ . The Thévenin equivalent voltage  $V_{th}$  can be obtained by finding the open-circuit voltage  $V_{oc}$  across  $a$  and  $b$  without modifying the circuit. The Thévenin equivalent resistance  $R_{th}$  can be found in one of the three methods. The first method is to find the equivalent resistance seen from  $a$  and  $b$  after deactivating the independent sources. The first method can be used only when a circuit does not contain dependent sources. The second method is to find the open-circuit voltage  $V_{oc}$  across  $a$  and  $b$  without modifying the circuit and to find the short-circuit current  $I_{sc}$  from  $a$  and  $b$  after connecting  $a$  and  $b$  by wire (a short-circuit). The Thévenin equivalent resistance  $R_{th}$  is the ratio of  $V_{oc}$  to  $I_{sc}$ ; i.e.,  $R_{th} = V_{oc}/I_{sc}$ . The third method is to apply a test voltage between terminals  $a$  and  $b$  after deactivating the independent sources and measure the current flowing out of the positive terminal of the test voltage source. The Thévenin equivalent resistance  $R_{th}$  is the ratio of the test voltage to the current flowing out of the positive terminal of the test voltage source. A test current source can be used instead of a test voltage source.

According to Norton's theorem, a given circuit is equivalent to a current source  $I_n$  and a parallel resistor  $R_n$  between terminals  $a$  and  $b$ . The Norton equivalent current  $I_n$  can be

obtained by finding the short-circuit current  $I_{sc}$  from  $a$  to  $b$  after connecting  $a$  and  $b$  by wire. The Norton equivalent resistance  $R_n$  can be found in one of the three methods. The first method is to find the equivalent resistance seen from terminals  $a$  and  $b$  after deactivating the independent sources. The first method can be used only when a circuit does not contain dependent sources. The second method is to measure the open-circuit voltage  $V_{oc}$  between  $a$  and  $b$  without modifying the circuit. The Norton equivalent resistance  $R_n$  is the ratio of  $V_{oc}$  to  $I_{sc}$ ; i.e.,  $R_n = V_{oc}/I_{sc}$ . The third method is to apply a test voltage between terminals  $a$  and  $b$  after deactivating the independent sources and measure the current flowing out of the positive terminal of the test voltage source. The Norton equivalent resistance  $R_n$  is the ratio of the test voltage to the current flowing out of the positive terminal of the test voltage source. A test current source can be used instead of a test voltage source.


Suppose that a load with resistance  $R_L$  is connected to a circuit between terminals  $a$  and  $b$ . We can find the Thévenin equivalent circuit with respect to the terminals  $a$  and  $b$  excluding the load resistance. Let  $V_{th}$  be the Thévenin equivalent voltage and  $R_{th}$  be the Thévenin equivalent resistance. It can be shown that the load resistance  $R_L$  that maximizes the power delivered to the load is given by the Thévenin equivalent resistance  $R_{th}$ .

## 4.2 Superposition Principle

Suppose that a circuit has  $N$  independent sources with  $N \geq 2$ . Create  $N$  circuits from the original circuit with only one independent source by deactivating the other  $N - 1$  independent sources. Deactivating a current source is to open-circuit it and deactivating a voltage source is to short-circuit it. The unknown voltages and currents of the original circuit can be found by adding the voltages and currents from the  $N$  circuits with one independent source. This is the superposition principle. The circuit shown in Figure 4.1 contains one voltage source and one current source. It is desired to find voltage  $V_1$  across  $R_2$ , which is also the voltage across the current source, using the superposition principle.

**FIGURE 4.1**

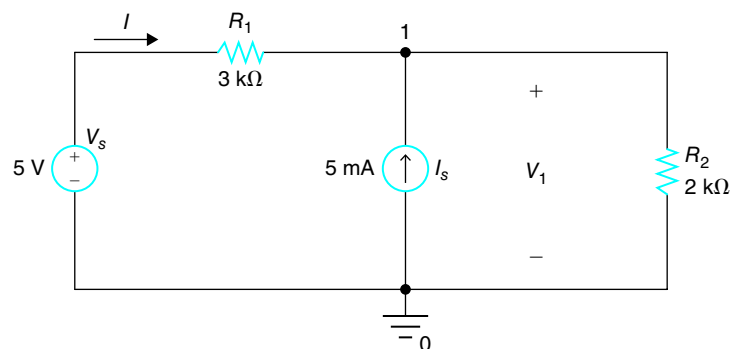
A circuit with a voltage source and a current source.



If the current from the current source is reduced to zero (that is,  $I_s = 0$ ), the current source is open-circuited, and the circuit reduces to the one shown in Figure 4.2.

**FIGURE 4.2**

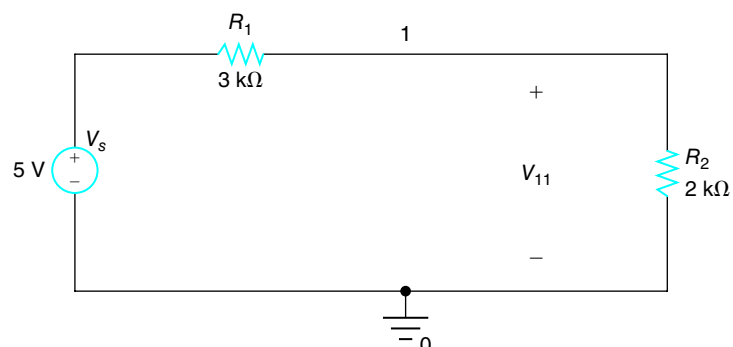Circuit shown in Figure 4.1 with the current source deactivated.




From the voltage divider rule, the voltage at node 1 is given by

$$V_{11} = \frac{R_2}{R_1 + R_2} V_s = \frac{2 \text{ k}\Omega}{3 \text{ k}\Omega + 2 \text{ k}\Omega} \times 5 \text{ V} = \frac{2}{5} \times 5 \text{ V} = 0.4 \times 5 \text{ V} = 2 \text{ V}$$

If the voltage from the voltage source is reduced to zero (that is,  $V_s = 0$ ), the voltage source is short-circuited, and the circuit reduces to the one shown in Figure 4.3.

**FIGURE 4.3**

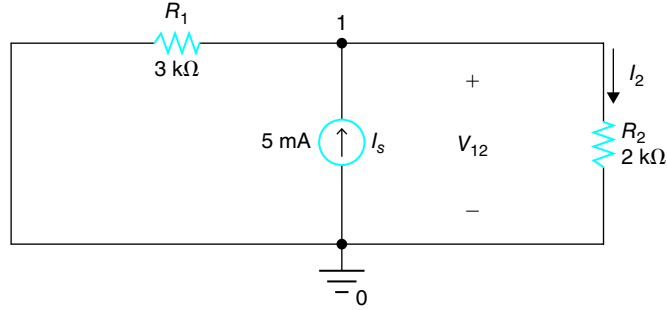Circuit shown in Figure 4.1 with the voltage source deactivated.



From the current divider rule, the current through  $R_2$  is given by

$$I_2 = \frac{\frac{1}{R_2}}{\frac{1}{R_2} + \frac{1}{R_1}} I_s = \frac{R_1}{R_1 + R_2} I_s = \frac{3000}{3000 + 2000} \times 5 \text{ mA} = 3 \text{ mA}$$

Thus, the voltage at node 1 is

$$V_{12} = R_2 I_2 = \frac{R_2 R_1}{R_1 + R_2} I_s = \frac{2000 \times 3000}{3000 + 2000} \Omega \times 5 \times 10^{-3} \text{ A} = 1200 \Omega \times 5 \times 10^{-3} \text{ A} = 6 \text{ V}$$

The sum of  $V_{11}$  and  $V_{12}$  is given by

$$V_1 = V_{11} + V_{12} = \frac{R_2}{R_1 + R_2} V_s + \frac{R_2 R_1}{R_1 + R_2} I_s = 0.4 V_s + 1200 I_s = 2 \text{ V} + 6 \text{ V} = 8 \text{ V} \quad (4.1)$$

As a check, let us find  $V_1$  using nodal analysis. Summing the currents leaving node 1 in the circuit shown in Figure 4.1, we have

$$\frac{V_1 - V_s}{R_1} + \frac{V_1}{R_2} - I_s = 0$$

This equation can be revised as follows:

$$\left( \frac{1}{R_1} + \frac{1}{R_2} \right) V_1 = \frac{V_s}{R_1} + I_s$$

Solving this equation for  $V_1$ , we have

$$\begin{aligned} V_1 &= \frac{\frac{V_s}{R_1} + I_s}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_2}{R_1 + R_2} V_s + \frac{R_2 R_1}{R_1 + R_2} I_s = \frac{2000}{3000 + 2000} V_s + \frac{2000 \times 3000}{3000 + 2000} I_s \\ &= 0.4 V_s + 1200 I_s = 0.4 \times 5 \text{ V} + 1200 \times 5 \times 10^{-3} \text{ V} = 2 \text{ V} + 6 \text{ V} = 8 \text{ V} \end{aligned} \quad (4.2)$$

Comparison of Equations (4.1) and (4.2) reveals that the answer derived from the superposition principle matches the one from the nodal analysis. This proves that the superposition principle works for the circuit shown in Figure 4.1. In general, if the circuit is linear, the superposition principle holds. Circuits consisting of independent and dependent voltage sources and current sources along with resistors are all linear circuits. Thus, the superposition principle works for these circuits. Equations (4.1) and (4.2) show that the voltage at node 1,  $V_1$ , consists of two components. The first component of  $V_1$ ,

$$V_{11} = \frac{R_2}{R_1 + R_2} V_s$$

is due to the voltage source  $V_s$ ; and the second component of  $V_1$ ,

$$V_{12} = \frac{R_2 R_1}{R_1 + R_2} I_s$$

is due to the current source  $I_s$ . The voltage at node 1,  $V_1$ , is the linear combination of two inputs  $V_s$  and  $I_s$ . The coefficients  $a_1$  and  $a_2$  in the representation,

$$V_1 = a_1 V_s + a_2 I_s \quad (4.3)$$

are given by

$$a_1 = \frac{R_2}{R_1 + R_2} = 0.4, \quad a_2 = \frac{R_2 R_1}{R_1 + R_2} = 1200 \, \Omega \quad (4.4)$$

Equation (4.3) is called linear because the output,  $V_1$ , is a linear function of inputs  $V_s$  and  $I_s$ ; that is,  $V_1$  is proportional to  $V_s$  and  $I_s$ . The proportionality constants are  $a_1$  and  $a_2$ . Notice that if  $I_s$  is set to zero in Equation (4.3), we obtain  $V_{11}$ , and if  $V_s$  is set to zero in Equation (4.3), we obtain  $V_{12}$ .

Let  $I$  be the current from the voltage source, as shown in Figure 4.1. The current  $I$  is given by

$$I = \frac{V_s - V_1}{R_1} = \frac{V_s - \frac{R_2}{R_1 + R_2} V_s - \frac{R_1 R_2}{R_1 + R_2} I_s}{R_1} = \frac{1}{R_1 + R_2} V_s - \frac{R_2}{R_1 + R_2} I_s \quad (4.5)$$


The current  $I$  is a linear combination of the two inputs  $V_s$  and  $I_s$ .

### EXAMPLE 4.1

Use the superposition principle to find voltage  $V_1$  in the circuit shown in Figure 4.4.

FIGURE 4.4

Circuit for  
EXAMPLE 4.1.

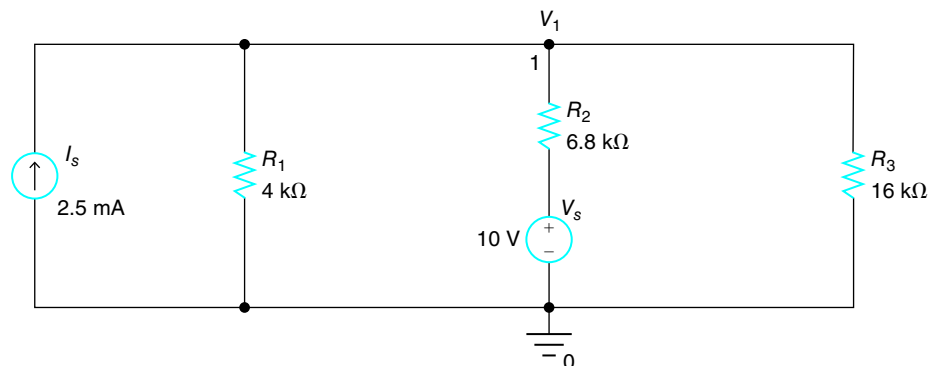


continued

Example 4.1 continued

When the current source is deactivated by open-circuiting it, the circuit shown in Figure 4.4 reduces to the one shown in Figure 4.5.

**FIGURE 4.5**

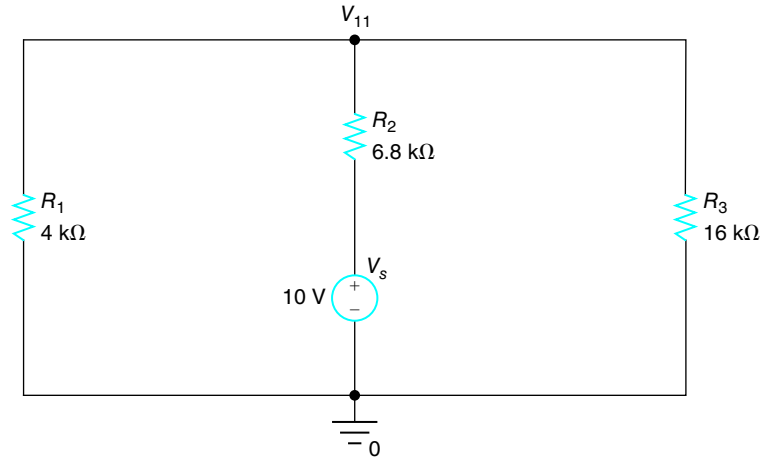The circuit in Figure 4.4, with the current source deactivated by open-circuiting.



The equivalent resistance of the parallel connection of  $R_1$  and  $R_3$  is given by

$$R_a = R_1 \parallel R_3 = \frac{R_1 R_3}{R_1 + R_3} = \frac{4 \text{ k}\Omega \times 16 \text{ k}\Omega}{4 \text{ k}\Omega + 16 \text{ k}\Omega} = \frac{64}{20} \text{ k}\Omega = 3.2 \text{ k}\Omega$$


Application of the voltage divider rule yields

$$V_{11} = \frac{R_a}{R_2 + R_a} V_s = \frac{3.2 \text{ k}\Omega}{6.8 \text{ k}\Omega + 3.2 \text{ k}\Omega} \times 10 \text{ V} = \frac{3.2}{10} \times 10 \text{ V} = 3.2 \text{ V}$$

When the voltage source is deactivated by short-circuiting it, the circuit shown in Figure 4.4 reduces to the one shown in Figure 4.6.

**FIGURE 4.6**

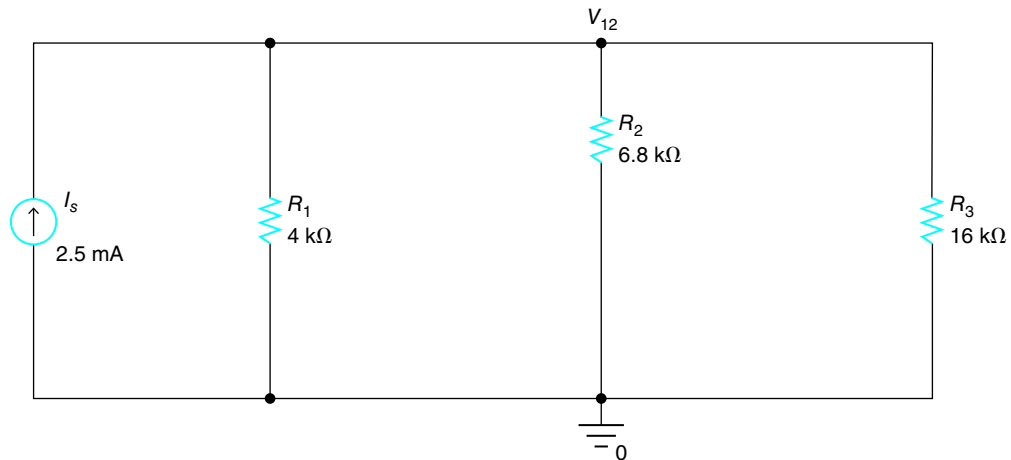The circuit in Figure 4.4, with the current source deactivated by closed-circuiting.



The equivalent resistance of the parallel connection of  $R_1$ ,  $R_3$ , and  $R_2$  is given by

$$R_b = R_a \parallel R_2 = \frac{R_a R_2}{R_a + R_2} = \frac{3.2 \text{ k}\Omega \times 6.8 \text{ k}\Omega}{3.2 \text{ k}\Omega + 6.8 \text{ k}\Omega} = 2.176 \text{ k}\Omega$$

continued

Example 4.1 continued

Voltage  $V_{12}$  is the product of  $R_b$  and  $I_s$ . Thus, we have

$$V_{12} = R_b I_s = 2176 \, \Omega \times 2.5 \times 10^{-3} \, \text{A} = 5.44 \, \text{V}$$

Voltage  $V_1$  is the sum of  $V_{11}$  and  $V_{12}$ :

$$V_1 = V_{11} + V_{12} = 3.2 \, \text{V} + 5.44 \, \text{V} = 8.64 \, \text{V}$$

As a check, we can find  $V_1$  directly from the circuit shown in Figure 4.4 by applying nodal analysis. Summing the currents leaving node 1, we obtain

$$-2.5 \times 10^{-3} + \frac{V_1}{4000} + \frac{V_1 - 10}{6800} + \frac{V_1}{16,000} = 0$$

which can be rearranged as

$$\left( \frac{1}{4000} + \frac{1}{6800} + \frac{1}{16,000} \right) V_1 = 2.5 \times 10^{-3} + \frac{10}{6800}$$

Solving for  $V_1$ , we obtain

$$V_1 = \frac{2.5 \times 10^{-3} + \frac{10}{6800}}{\frac{1}{4000} + \frac{1}{6800} + \frac{1}{16,000}} = \frac{3.9705882353 \times 10^{-3}}{4.5955882353 \times 10^{-4}} = 8.64 \, \text{V}$$


This value is the same as the one obtained from the superposition principle.

### Exercise 4.1

Use the superposition principle to find voltage  $V_1$  in the circuit shown in Figure 4.7.

FIGURE 4.7

Circuit for  
EXERCISE 4.1.

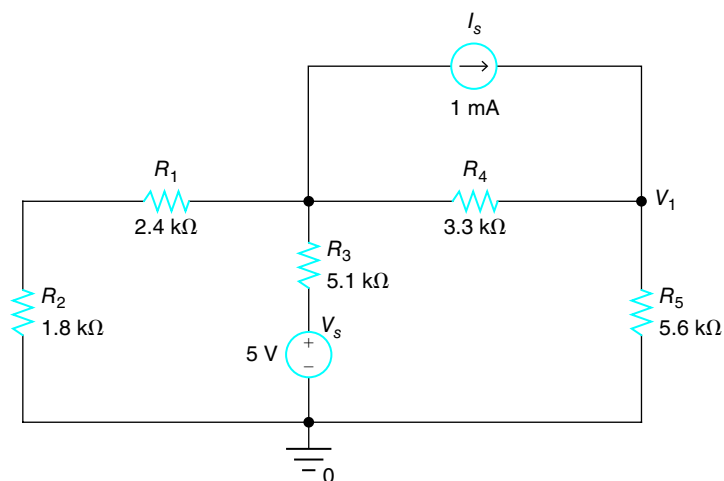

**Answer:**


$$V_1 = 2.7782 \, \text{V}, 1.1287 \, \text{V from } V_s, 1.6495 \, \text{V from } I_s.$$

## EXAMPLE 4.2

Use the superposition principle to find the voltage across  $R_2$  in the circuit shown in Figure 4.8.

FIGURE 4.8


Circuit for  
EXAMPLE 4.2.

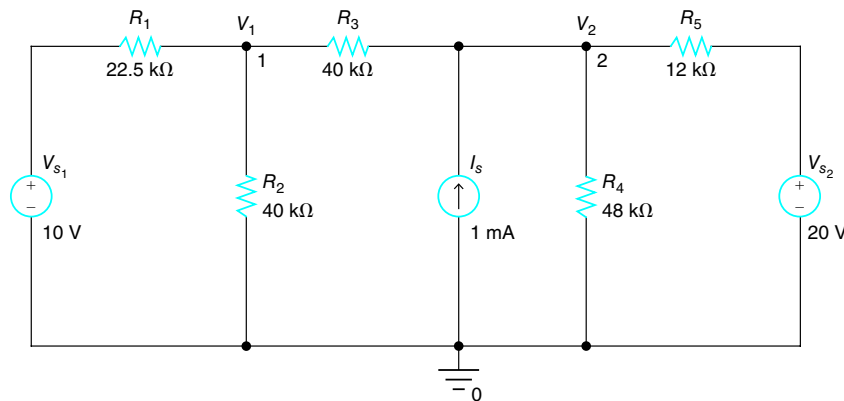

Deactivating the current source from the circuit shown in Figure 4.8 by removing it and also deactivating the voltage source  $V_{s2}$  by short-circuiting it, we obtain the circuit shown in Figure 4.9.

FIGURE 4.9

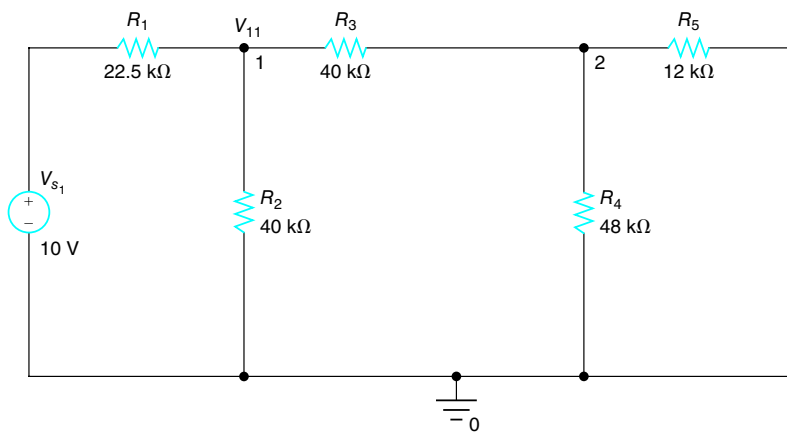The circuit shown in  
Figure 4.8 with  $I_s$  and  
 $V_{s2}$  deactivated.



Let  $R_a$  be the equivalent resistance of  $R_2$ ,  $R_3$ ,  $R_4$ , and  $R_5$  seen from  $R_1$ . Then, we have

$$\begin{aligned} R_a &= R_2 \parallel (R_3 + (R_4 \parallel R_5)) = 40,000 \parallel \left( 40,000 + \frac{48,000 \times 12,000}{48,000 + 12,000} \right) \\ &= 40,000 \parallel (40,000 + 9600) = 40,000 \parallel 49,600 = \frac{40,000 \times 49,600}{40,000 + 49,600} \\ &= \frac{1.984 \times 10^9}{89,600} = 22.142857 \text{ k}\Omega \end{aligned}$$

Applying the voltage divider rule, we get voltage  $V_{11}$  at node 1:

$$V_{11} = V_{s1} \times \frac{R_a}{R_1 + R_a} = 10 \text{ V} \times \frac{22.142857 \text{ k}\Omega}{22.5 \text{ k}\Omega + 22.142857 \text{ k}\Omega} = 4.96 \text{ V} \quad (4.6)$$


continued

Example 4.2 continued

Deactivating the voltage sources  $V_{s_1}$  and  $V_{s_2}$  from the circuit shown in Figure 4.8 by short-circuiting both of them, we obtain the circuit shown in Figure 4.10.

**FIGURE 4.10**

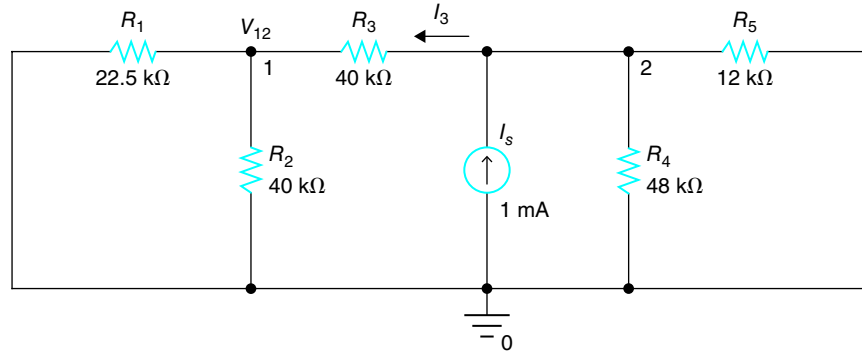The circuit shown in Figure 4.8 with voltage sources  $V_{s_1}$  and  $V_{s_2}$  deactivated.



Let  $R_b$  be the equivalent resistance of the parallel connection of  $R_1$  and  $R_2$ . Then, we have

$$R_b = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{22.5 \text{ k}\Omega \times 40 \text{ k}\Omega}{22.5 \text{ k}\Omega + 40 \text{ k}\Omega} = \frac{900}{62.5} \text{ k}\Omega = 14.4 \text{ k}\Omega$$

Let  $R_c$  be the equivalent resistance of the series connection of  $R_3$  and  $R_b$ . Then, we have

$$R_c = R_3 + R_b = 40 \text{ k}\Omega + 14.4 \text{ k}\Omega = 54.4 \text{ k}\Omega$$

Let  $R_d$  be the equivalent resistance of the parallel connection of  $R_4$  and  $R_5$ . Then, we have

$$R_d = \frac{R_4 \times R_5}{R_4 + R_5} = \frac{48 \text{ k}\Omega \times 12 \text{ k}\Omega}{48 \text{ k}\Omega + 12 \text{ k}\Omega} = \frac{576}{60} \text{ k}\Omega = 9.6 \text{ k}\Omega$$

From the current divider rule, the current through  $R_c$  is given by

$$I_3 = I_s \times \frac{R_d}{R_c + R_d} = 1 \text{ mA} \times \frac{9.6 \text{ k}\Omega}{54.4 \text{ k}\Omega + 9.6 \text{ k}\Omega} = 0.15 \text{ mA}$$

Voltage  $V_{12}$  across  $R_b$  is

$$V_{12} = I_3 \times R_b = 0.15 \times 10^{-3} \times 14,400 \text{ V} = 2.16 \text{ V} \quad (4.7)$$

Deactivating the current source from the circuit shown in Figure 4.8 by removing it and also deactivating the voltage source  $V_{s_1}$  by short-circuiting it, we obtain the circuit shown in Figure 4.11.

Let  $R_e$  be the equivalent resistance of the parallel connection of  $R_c$  and  $R_4$ . Then, we have

$$R_e = R_c \parallel R_4 = 54,400 \parallel 48,000 = \frac{54,400 \times 48,000}{54,400 + 48,000} = 25.5 \text{ k}\Omega$$

Applying the voltage divider rule, we get voltage  $V_{23}$  at node 2:

$$V_{23} = V_{s_2} \times \frac{R_e}{R_5 + R_e} = 20 \text{ V} \times \frac{25.5 \text{ k}\Omega}{25.5 \text{ k}\Omega + 12 \text{ k}\Omega} = 13.6 \text{ V}$$


continued



Example 4.2 continued

**FIGURE 4.11**

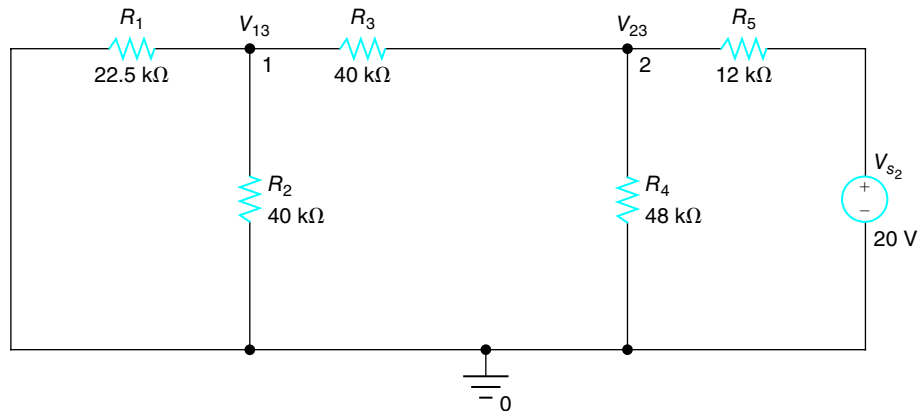The circuit shown in Figure 4.8 with  $I_s$  and  $V_{s1}$  deactivated.



Applying the voltage divider rule, we get voltage  $V_{13}$  at node 1:

$$V_{13} = V_{23} \times \frac{R_b}{R_c} = 13.6 \text{ V} \times \frac{14.4 \text{ k}\Omega}{54.4 \text{ k}\Omega} = 3.6 \text{ V} \quad (4.8)$$

Adding the three voltages, we obtain voltage  $V_1$ :

$$V_1 = V_{11} + V_{12} + V_{13} = 4.96 \text{ V} + 2.16 \text{ V} + 3.6 \text{ V} = 10.72 \text{ V}$$

To verify this answer, we can find voltage  $V_1$  across  $R_2$  directly from the original circuit shown in Figure 4.8 using nodal analysis, as shown in the **MATLAB** script given here:

**MATLAB**

```
%EXAMPLE 4.2
%Function P.m should be in the same folder as this file.
clear all;format long;
R1=22500;R2=40000;R3=40000;R4=48000;R5=12000;
Vs1=10;Vs2=20;Is=1e-3;
%V11 from Vs1
Ra=P([R2,R3+P([R4,R5])])
V11=Vs1*Ra/(Ra+R1)
%V12 from Is
Rb=P([R1,R2])
Rc=R3+Rb
Rd=P([R4,R5])
I3=Is*Rd/(Rc+Rd)
V12=Rb*I3
%V13 from Vs2
Re=P([Rc,R4])
V23=Vs2*Re/(R5+Re)
V13=V23*Rb/Rc
%Sum of V11, V12, V13
V1b=V11+V12+V13
%Check from nodal analysis
syms V1 V2
[V1,V2]=solve((V1-Vs1)/R1+V1/R2+(V1-V2)/R3,...
(V2-V1)/R3-Is+V2/R4+(V2-Vs2)/R5);
V1=vpa(V1,8)
V2=vpa(V2,8)
```

continued

Example 4.2 continued  
MATLAB continued

```


Answers:
Ra =
    2.214285714285715e+04
V11 =
    4.960000000000000
Rb =
    14400
Rc =
    54400
Rd =
    9600
I3 =
    1.500000000000000e-04
V12 =
    2.160000000000000
Re =
    25500
V23 =
    13.600000000000000
V13 =
    3.600000000000000
V1b =
    10.719999999999999
V1 =
    10.72
V2 =
    22.72
  
```

## Exercise 4.2

Use the superposition principle to find voltage  $V_1$  in the circuit shown in Figure 4.12.

**FIGURE 4.12**

Circuit for  
EXERCISE 4.2.

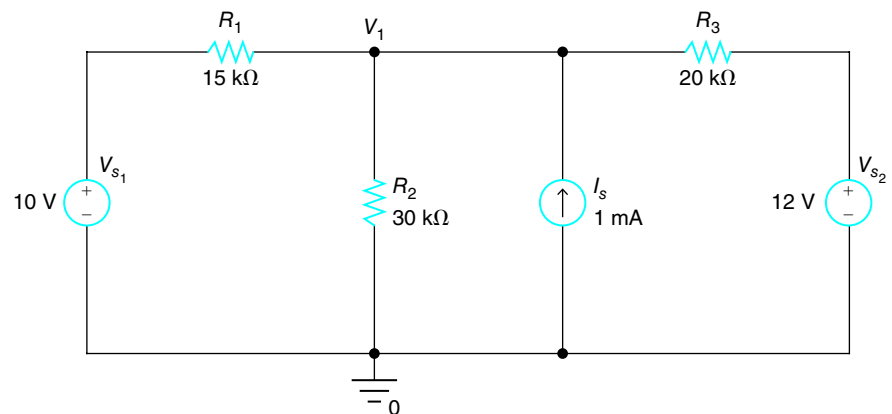

**Answer:**


$V_1 = 15.1111$  V. 4.4444 V from  $V_{s1}$ , 4 V from  $V_{s2}$ , 6.6667 V from  $I_s$ .

## EXAMPLE 4.3

Use the superposition principle to find voltage  $V_0$  across  $R_4$  in the circuit shown in Figure 4.13.

FIGURE 4.13


Circuit for  
EXAMPLE 4.3.

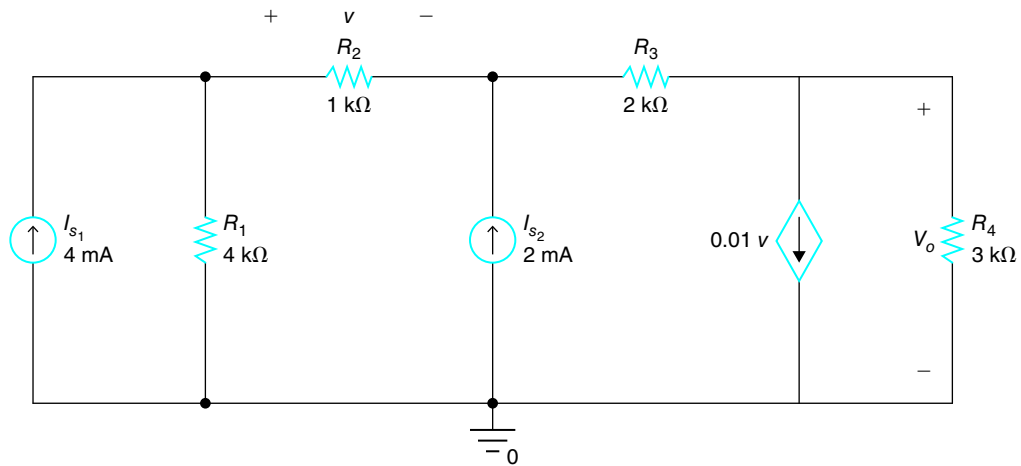

Deactivating the current source  $I_{s2}$  from the circuit shown in Figure 4.13, we obtain the circuit shown in Figure 4.14.

FIGURE 4.14

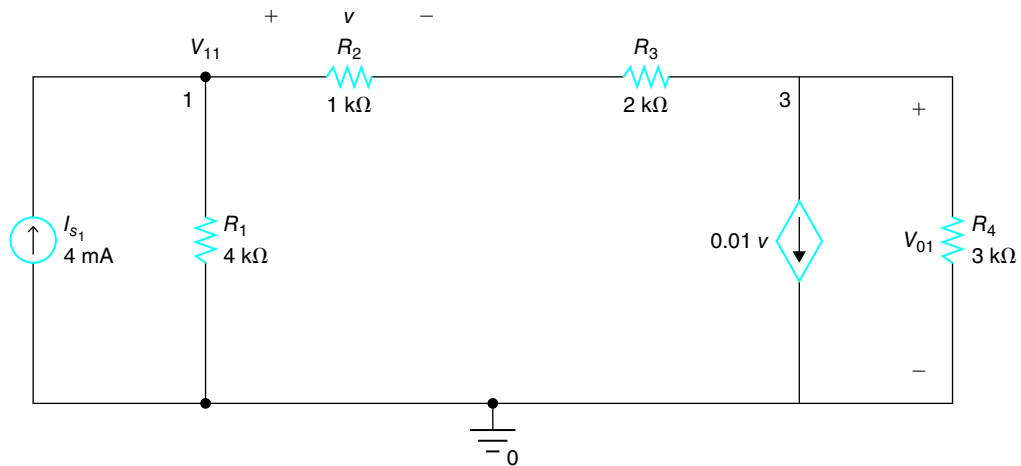The circuit shown  
in Figure 4.13 with  
the current source  
 $I_{s2}$  deactivated.



Applying the voltage divider rule, we can find the controlling voltage  $v$  to be

$$v = (V_{11} - V_{01}) \frac{R_2}{R_2 + R_3} = (V_{11} - V_{01}) \frac{1}{3} \quad (4.9)$$

Summing the currents leaving node 1, we obtain

$$-0.004 + \frac{V_{11}}{4000} + \frac{V_{11} - V_{01}}{3000} = 0$$

*continued*

Example 4.3 continued

Multiplication by 12,000 yields

$$-48 + 3V_{11} + 4(V_{11} - V_{01}) = 0$$

which can be rearranged as

$$7V_{11} - 4V_{01} = 48 \quad (4.10)$$

Summing the currents leaving node 3, we get

$$\frac{V_{01} - V_{11}}{3000} + 0.01 \frac{V_{11} - V_{01}}{3} + \frac{V_{01}}{3000} = 0$$

Multiplication by 3000 yields

$$V_{01} - V_{11} + 10(V_{11} - V_{01}) + V_{01} = 0$$

which can be rearranged as

$$9V_{11} - 8V_{01} = 0 \quad (4.11)$$

Solving Equation (4.11) for  $V_{11}$ , we obtain

$$V_{11} = \frac{8}{9}V_{01} \quad (4.12)$$

Substitution of Equation (4.12) into Equation (4.10) yields

$$7\frac{8}{9}V_{01} - 4V_{01} = \frac{20}{9}V_{01} = 48$$


Thus, voltage  $V_{01}$  across  $R_4$  from  $I_{s1}$  is given by

$$V_{01} = 48 \frac{9}{20} = \frac{108}{5} = 21.6 \text{ V} \quad (4.13)$$

Deactivating the current source  $I_{s1}$  from the circuit shown in Figure 4.13, we obtain the circuit shown in Figure 4.15.

**FIGURE 4.15**

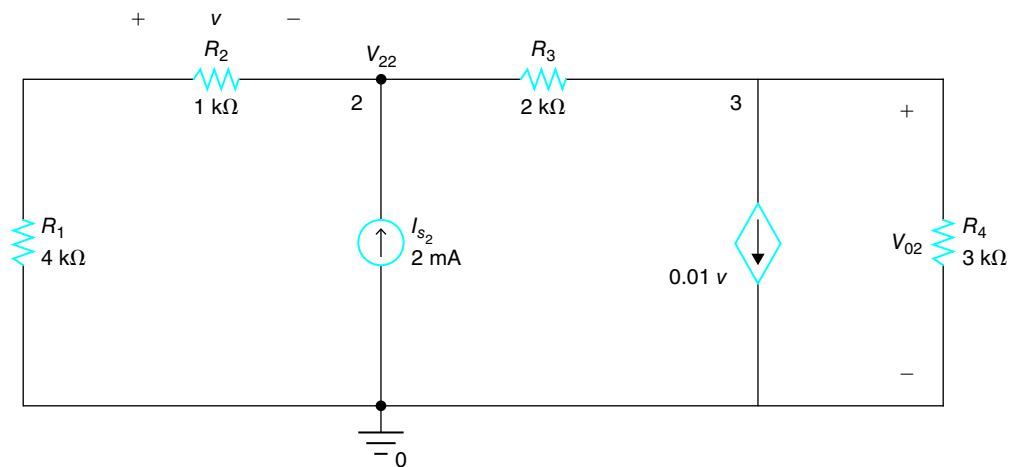Circuit shown in Figure 4.13 with the current source  $I_{s1}$  deactivated.



continued

*Example 4.3 continued*Applying the voltage divider rule, we can find the controlling voltage  $v$  to be

$$v = -V_{22} \frac{R_2}{R_1 + R_2} = \frac{-V_{22}}{5} \quad (4.14)$$

Summing the currents leaving node 2, we obtain

$$\frac{V_{22}}{5000} - 0.002 + \frac{V_{22} - V_{02}}{2000} = 0$$

Multiplication by 10,000 yields

$$2V_{22} - 20 + 5(V_{22} - V_{02}) = 0$$

which can be rearranged as

$$7V_{22} - 5V_{02} = 20 \quad (4.15)$$

Summing the currents leaving node 3, we get

$$\frac{V_{02} - V_{22}}{2000} + 0.01 \frac{-V_{22}}{5} + \frac{V_{02}}{3000} = 0$$

Multiplication by 6000 yields

$$3V_{02} - 3V_{22} - 12V_{22} + 2V_{02} = 0$$

which can be rearranged as

$$-15V_{22} + 5V_{02} = 0 \quad (4.16)$$

Solving Equation (4.16) for  $V_{22}$ , we obtain

$$V_{22} = \frac{1}{3} V_{02} \quad (4.17)$$

Substitution of Equation (4.17) into Equation (4.15) yields

$$7\frac{1}{3} V_{02} - 5V_{02} = -\frac{8}{3} V_{02} = 20$$

Thus, voltage  $V_{02}$  across  $R_4$  from  $I_{s_2}$  is given by

$$V_{02} = -20 \frac{3}{8} = -\frac{60}{8} = -7.5 \text{ V} \quad (4.18)$$

Voltage  $V_0$  across  $R_4$  is the sum of  $V_{01}$  and  $V_{02}$ . From Equations (4.13) and (4.18), we obtain


$$V_0 = V_{01} + V_{02} = 14.1 \text{ V}$$

### Exercise 4.3

Use the superposition principle to find voltage  $V_2$  in the circuit shown in Figure 4.16.

**FIGURE 4.16**

Circuit for  
EXERCISE 4.3.

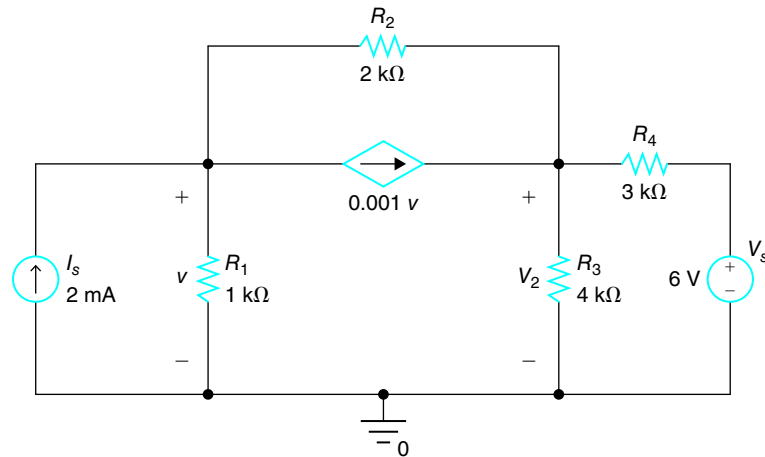

**Answer:**


$V_2 = 4.0851 \text{ V}$ . 1.5319 V from  $I_s$ , 2.5532 V from  $V_s$ .

## 4.3 Source Transformations

A circuit consisting of a voltage source with voltage  $V_s$  and a series resistor with resistance  $R_s$ , as shown in Figure 4.17(a), is equivalent to a circuit consisting of a current source with current  $V_s/R_s$  and a parallel resistor with resistance  $R_s$ , as shown in Figure 4.17(b). *Equivalence* means that the circuit shown in Figure 4.17(a) and the circuit shown in Figure 4.17(b) have the same open-circuit voltage across  $a$  and  $b$ , the same short-circuit current through  $a$  and  $b$ , and the same resistance looking into the circuit from  $a$  and  $b$  after deactivating the source. The open-circuit voltage across  $a$  and  $b$  for the circuit shown in Figure 4.17(a) is  $V_s$ , and that for the circuit shown in Figure 4.17(b) is  $R_s \times (V_s/R_s) = V_s$ . The short-circuit current (with  $a$  and  $b$  connected by wire) through  $a$  and  $b$  for the circuit shown in Figure 4.17(a) is  $V_s/R_s$ , and that for the circuit shown in Figure 4.17(b) is  $V_s/R_s$  based on the current divider rule. After short-circuiting  $V_s$ , the resistance across  $a$  and  $b$  for the circuit shown in Figure 4.17(a) is  $R_s$ , and that for the circuit shown in Figure 4.17(b) after open-circuiting the current source is  $R_s$ . The circuit shown in Figure 4.17(a) can be replaced by the circuit shown in Figure 4.17(b).

**FIGURE 4.17**

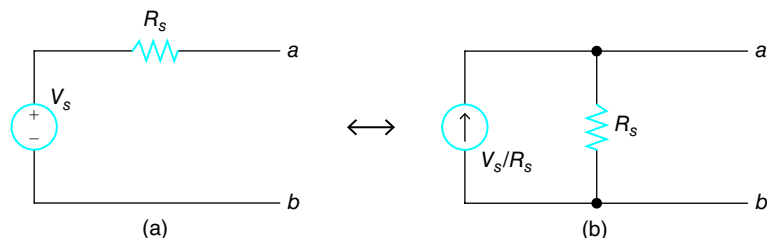
A voltage source and a series resistor are equivalent to a current source and a parallel resistor.



Also, the circuit shown in Figure 4.18(a) is equivalent to the circuit shown in Figure 4.18(b). The circuit shown in Figure 4.18(a) can be replaced by the circuit shown in Figure 4.18(b).

**FIGURE 4.18**

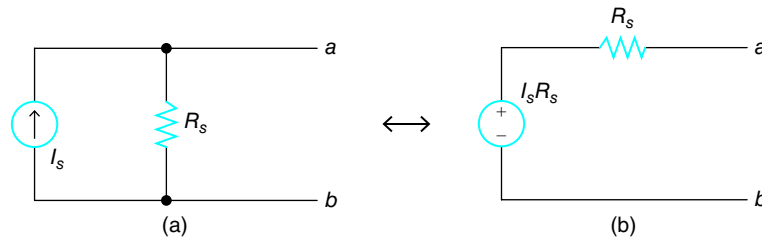
A current source and a parallel resistor are equivalent to a voltage source and a series resistor.



The source transformations apply to dependent sources as well. Figures 4.19 and 4.20 show the equivalence of a voltage source and a series resistor, and a current source and a parallel resistor.

**FIGURE 4.19**

A dependent voltage source and a series resistor are equivalent to a dependent current source and a parallel resistor.

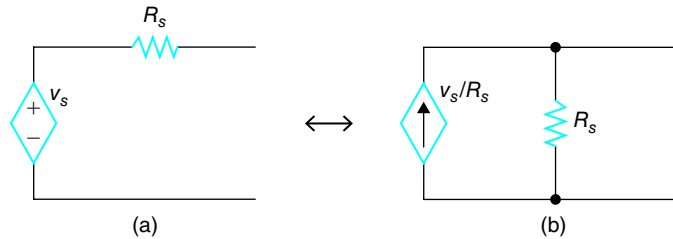**FIGURE 4.20**

A dependent current source and a parallel resistor are equivalent to a dependent voltage source and a series resistor.

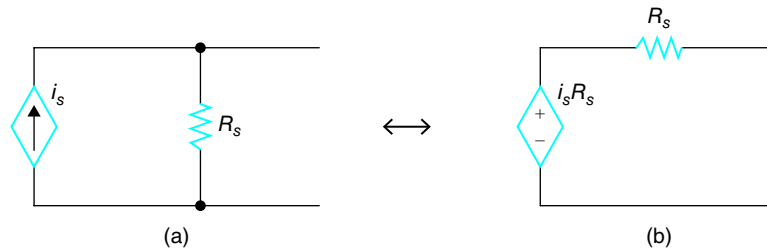


Figure 4.21(a) shows a circuit with a voltage source and a series resistor connected to the rest of the circuit. The voltage  $v$  is the voltage at the input of the rest of the circuit, and  $i$  is the current into the rest of the circuit. Writing a mesh equation in the clockwise direction, we obtain

$$-v_s + R_s i + v = 0 \quad (4.19)$$

which can be rewritten as

$$v = v_s - R_s i \quad (4.20)$$

Solving Equation (4.20) for  $i$ , we get


$$i = \frac{v_s}{R_s} - \frac{v}{R_s} \quad (4.21)$$

The first term,  $v_s/R_s$ , on the right side of Equation (4.21) represents a current source with current  $v_s/R_s$ , and the second term,  $v/R_s$ , on the right side of Equation (4.21) represents a current through a resistor with resistance  $R_s$  whose voltage is  $v$ . Based on Equation (4.21), we can draw an equivalent circuit, as shown in Figure 4.21(b). Writing a node equation at node 1 of the circuit shown in Figure 4.21(b) as a check, we obtain Equation (4.21). Rearrangement of Equation (4.21) results in Equation (4.20). This shows the equivalence of the circuits shown in Figures 4.21(a–b).


Consider a circuit shown in Figure 4.22. We are interested in finding voltage  $V_o$  across  $R_5$  using source transformation.

**FIGURE 4.21**

Circuit showing proof of equivalence.

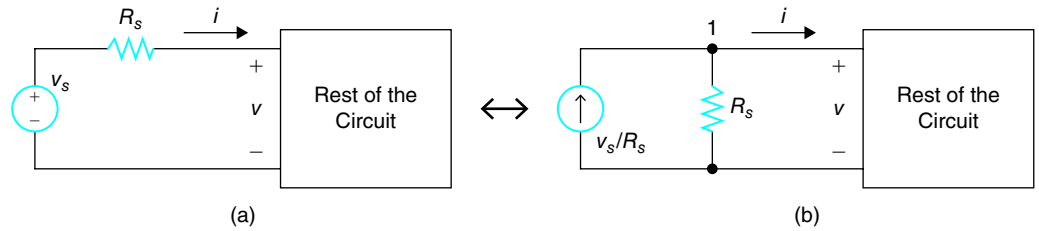**FIGURE 4.22**

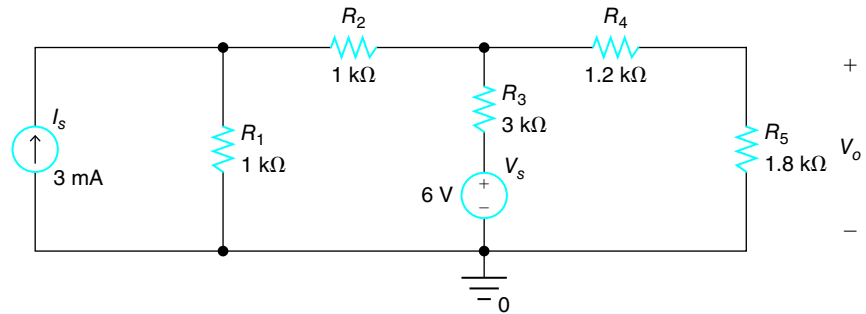A circuit used to illustrate source transformation.




The current source  $I_s$  and the parallel resistor  $R_1$  can be transformed into a voltage source with voltage

$$V_{s_1} = R_1 I_s = 1000 \times 3 \times 10^{-3} = 3 \text{ V}$$

and a series resistor  $R_1$ , as shown in Figure 4.23.

**FIGURE 4.23**

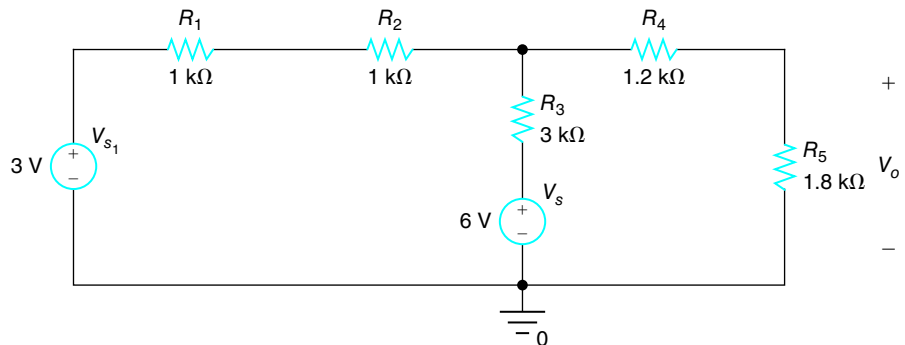$I_s$  and  $R_1$  are transformed into  $V_{s_1}$  and  $R_1$ .



Let  $R_a$  be the sum of  $R_1$  and  $R_2$ . Then, we have

$$R_a = R_1 + R_2 = 1 \text{ k}\Omega + 1 \text{ k}\Omega = 2 \text{ k}\Omega$$

The voltage source  $V_{s_1}$  and the series resistor  $R_a$  can be transformed into a current source with current

$$I_{s_1} = \frac{V_{s_1}}{R_a} = \frac{3 \text{ V}}{2 \text{ k}\Omega} = 1.5 \text{ mA}$$

and a parallel resistor  $R_a$ , as shown in Figure 4.24. Similarly, the voltage source  $V_s$  and the series resistor  $R_3$  can be transformed into a current source with current


$$I_{s_2} = \frac{V_s}{R_3} = \frac{6 \text{ V}}{3 \text{ k}\Omega} = 2 \text{ mA}$$



and a parallel resistor  $R_3$ , as shown in Figure 4.24. Notice that the direction of  $I_{s_2}$  is identical to the direction of  $I_{s_1}$ .

**FIGURE 4.24**

A circuit after source transformations.

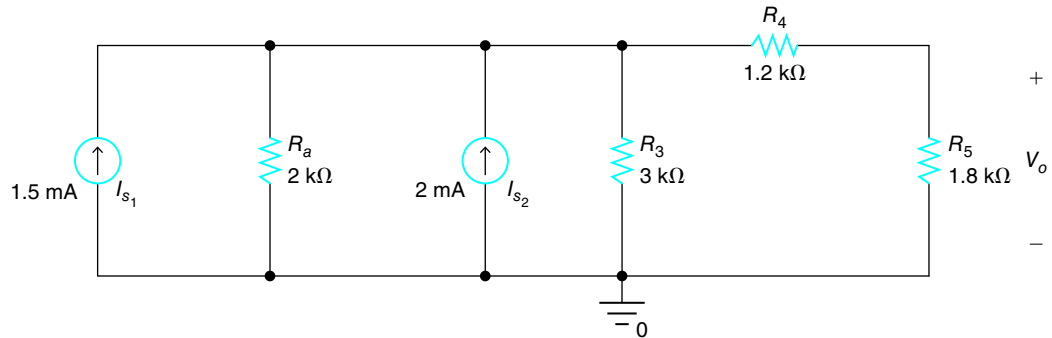

The combined current from the two parallel current sources is

$$I_{s_3} = I_{s_1} + I_{s_2} = 1.5 \text{ mA} + 2 \text{ mA} = 3.5 \text{ mA}$$


The equivalent resistance of the parallel connection of  $R_a$  and  $R_3$  is given by

$$R_b = R_a \parallel R_3 = \frac{R_a \times R_3}{R_a + R_3} = \frac{2000 \times 3000}{2000 + 3000} = 1.2 \text{ k}\Omega$$

Replacing the two current sources  $I_{s_1}$  and  $I_{s_2}$  and two parallel resistors  $R_a$  and  $R_3$  by current source  $I_{s_3}$  and parallel resistor  $R_b$ , we obtain the circuit shown in Figure 4.25.

**FIGURE 4.25**

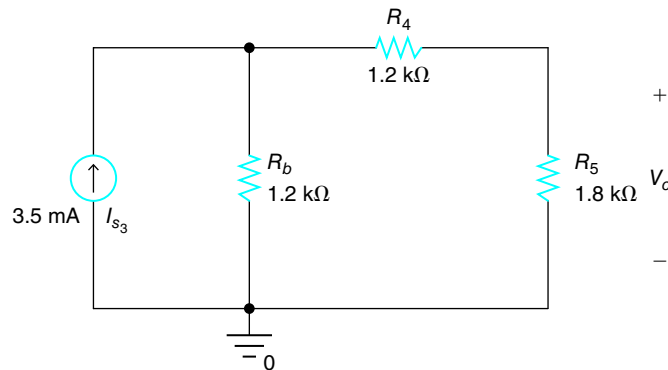The circuit in Figure 4.24 with one current source.



The current source  $I_{s_3}$  and the parallel resistor  $R_b$  can be transformed into a voltage source with voltage

$$V_{s_2} = I_{s_3} \times R_b = 3.5 \times 10^{-3} \times 1200 = 4.2 \text{ V}$$


and a series resistor with resistance  $R_b = 1.2 \text{ k}\Omega$ . The circuit shown in Figure 4.25 becomes the one shown in Figure 4.26.

Application of the voltage divider rule to the circuit shown in Figure 4.26 yields

$$\begin{aligned} V_o &= V_{s_2} \times \frac{R_5}{R_b + R_4 + R_5} = 4.2 \text{ V} \times \frac{1.8 \text{ k}\Omega}{1.2 \text{ k}\Omega + 1.2 \text{ k}\Omega + 1.8 \text{ k}\Omega} \\ &= 4.2 \text{ V} \times \frac{1.8}{4.2} = 1.8 \text{ V} \end{aligned}$$

**FIGURE 4.26**

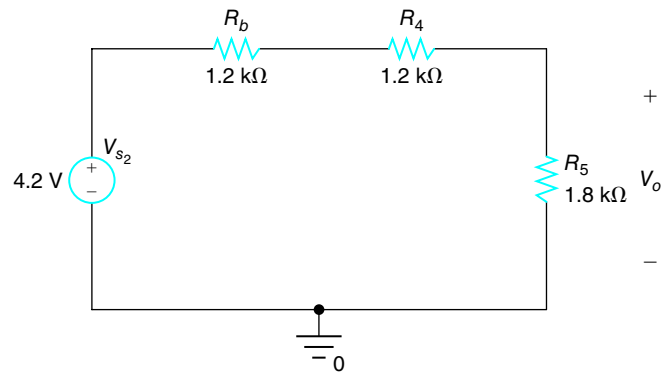
The circuit in Figure 4.25 with one voltage source.



Consider the circuit shown in Figure 4.27. We are interested in finding the voltage  $V_o$  using source transformation.

**FIGURE 4.27**

A circuit with a VCVS.

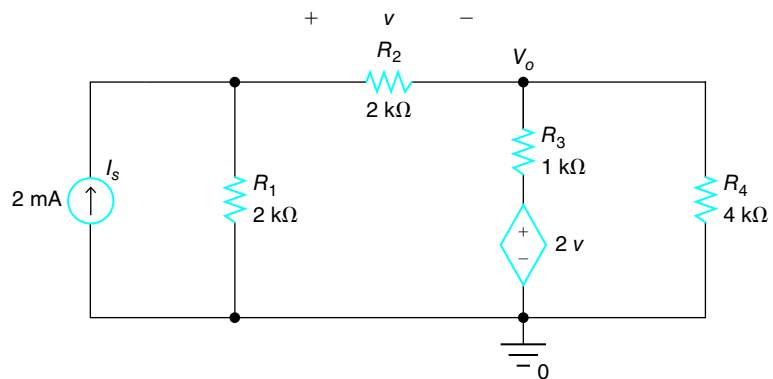


The current source  $I_s$  and parallel resistor  $R_1$  can be transformed into a voltage source  $V_s$  with voltage

$$V_s = R_1 \times I_s = 2 \text{ k}\Omega \times 2 \text{ mA} = 4 \text{ V}$$

and a series resistor  $R_1$ , as shown in Figure 4.28.

**FIGURE 4.28**

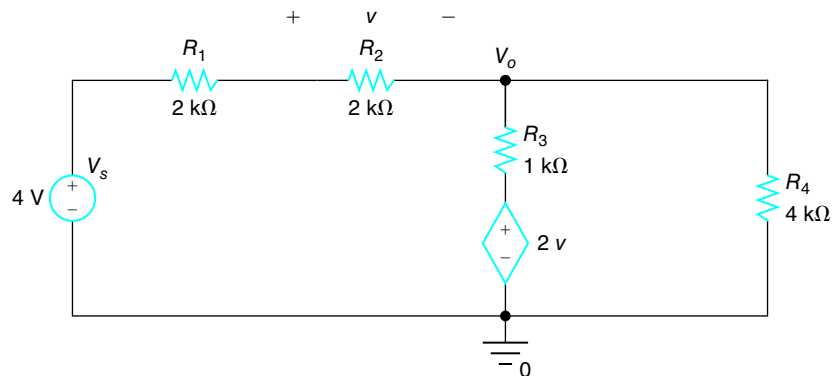
$I_s$  and  $R_1$  are transformed into a voltage source  $V_s$  and a series resistor  $R_1$ .



The voltage-controlled voltage source (VCVS) and  $R_3$  can be transformed into a voltage-controlled current source (VCCS) with current  $\frac{2v}{R_3}$  and a parallel resistor  $R_3$ , as shown in Figure 4.29.

FIGURE 4.29

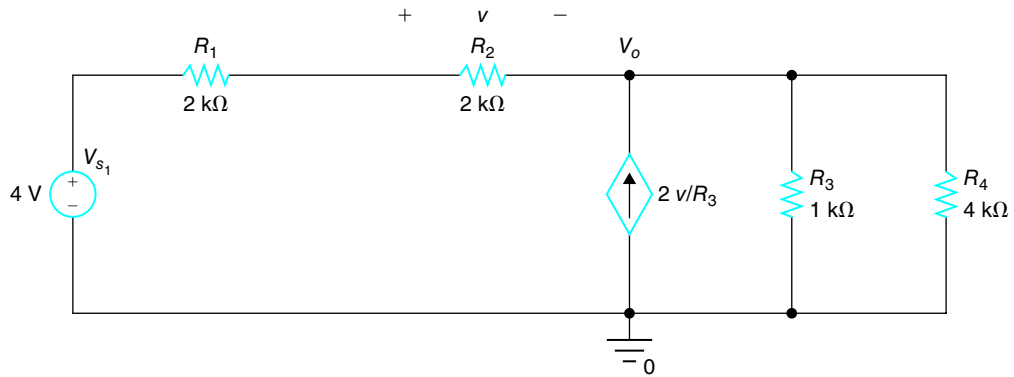A VCVS and  $R_3$  are transformed into a VCCS and a parallel resistor  $R_3$ .




Let  $R_a$  be the equivalent resistance of the parallel connection of  $R_3$  and  $R_4$ . Then, we have

$$R_a = R_3 \parallel R_4 = 1 \text{ k}\Omega \parallel 4 \text{ k}\Omega = 0.8 \text{ k}\Omega$$

FIGURE 4.30

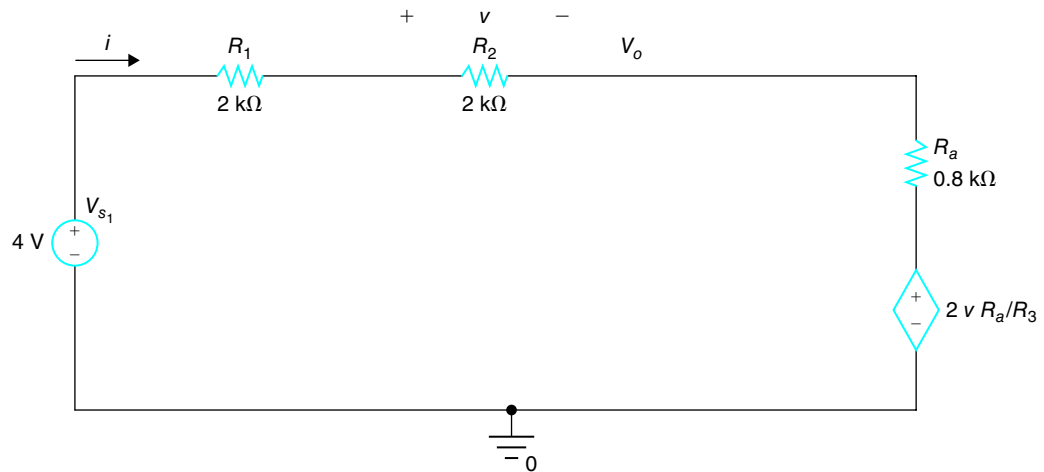A VCCS and  $R_a$  are transformed into a VCVS and a series resistor  $R_a$ .



The VCCS and a parallel resistor  $R_a$  can be transformed into a VCVS with voltage  $\frac{2vR_a}{R_3}$  and a series resistor  $R_a$ , as shown in Figure 4.30.

The original circuit is transformed into a single mesh. Let the mesh current be  $i$ . Then, the controlling voltage  $v$  is given by

$$v = R_2 i$$

Collecting the voltage drops around the mesh in the clockwise direction, we obtain

$$-R_1 I_s + R_1 i + R_2 i + R_a i + \frac{2R_2 R_a}{R_3} i = 0$$

Solving for  $i$ , we obtain

$$i = \frac{R_1 I_s}{R_1 + R_2 + R_a + \frac{2R_2 R_a}{R_3}} = \frac{4 \text{ V}}{2 \text{ k}\Omega + 2 \text{ k}\Omega + 0.8 \text{ k}\Omega + 3.2 \text{ k}\Omega} = 0.5 \text{ mA}$$

Voltage  $V_o$  is given by


$$V_o = R_a i + \frac{2R_2 R_a}{R_3} i = 2 \text{ V}$$

### EXAMPLE 4.4

Find voltage  $V_1$  using source transformation for the circuit shown in Figure 4.31.

**FIGURE 4.31**

Circuit for  
EXAMPLE 4.4.

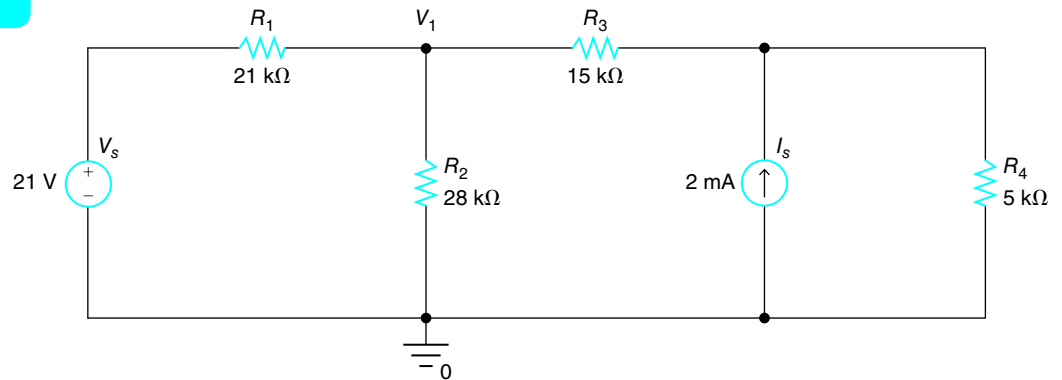


The voltage source  $V_s$  and a series resistor  $R_1$  can be transformed into a current source with the current:

$$I_{s_1} = \frac{V_s}{R_1} = \frac{21 \text{ V}}{21 \text{ k}\Omega} = 1 \text{ mA}$$

and a parallel resistor  $R_1$ , as shown in Figure 4.32.

**FIGURE 4.32**

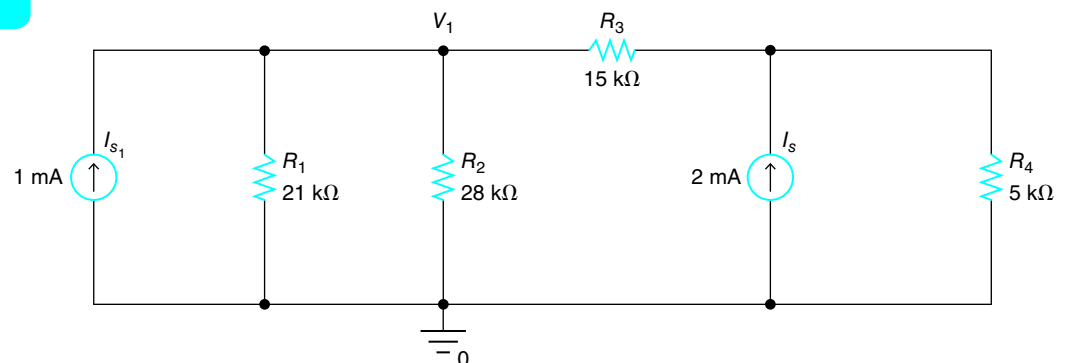The series connection  
of  $V_s$  and  $R_1$  is  
transformed into a  
parallel connection  
of  $I_{s_1}$  and  $R_1$ .



The equivalent resistance of parallel connection of  $R_1$  and  $R_2$  is given by

$$R_a = R_1 \parallel R_2 = 21 \text{ k}\Omega \parallel 28 \text{ k}\Omega = 12 \text{ k}\Omega$$


Figure 4.33 shows a circuit with  $I_{s_1}$  in parallel with  $R_a$ .

*continued*

Example 4.4 continued

**FIGURE 4.33**

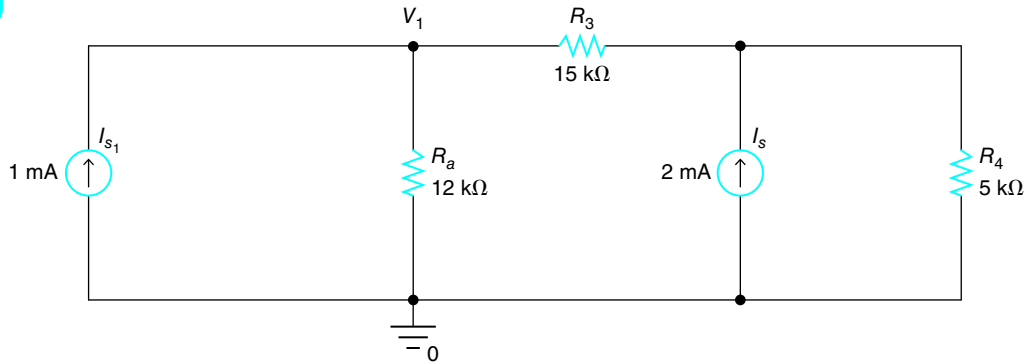A circuit with a parallel connection of  $I_{s1}$  and  $R_a$ .




The parallel connection of  $I_s$  and  $R_4$  can be transformed into a voltage source with the following voltage:

$$V_{s1} = R_4 \times I_s = 5 \text{ k}\Omega \times 2 \text{ mA} = 10 \text{ V}$$

and a series resistor  $R_4$ , as shown in Figure 4.34.

**FIGURE 4.34**

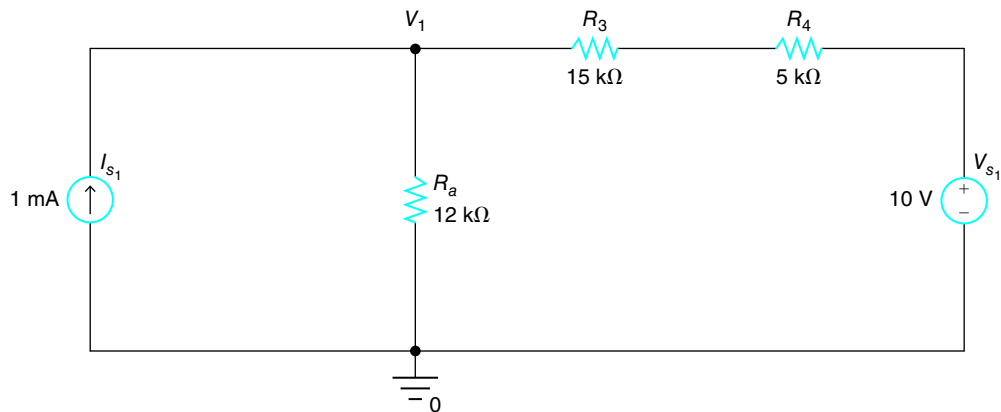The circuit in Figure 4.33 with a series connection of  $V_{s1}$  and  $R_4$ .



Let  $R_b$  be the equivalent resistance of the series connection of  $R_3$  and  $R_4$ . Then, we have

$$R_b = R_3 + R_4 = 20 \text{ k}\Omega$$

The series connection of  $V_{s1}$  and  $R_b$  can be transformed into a parallel connection of a current source with current

$$I_{s2} = \frac{V_{s1}}{R_b} = \frac{10 \text{ V}}{20 \text{ k}\Omega} = 0.5 \text{ mA}$$

and a parallel resistor  $R_b$ , as shown in Figure 4.35.

Let  $R_c$  be the equivalent resistance of the parallel connection on  $R_a$  and  $R_b$ . Then, we have


$$R_c = R_a \parallel R_b = 12 \text{ k}\Omega \parallel 20 \text{ k}\Omega = 7.5 \text{ k}\Omega$$

continued


Example 4.4 continued

**FIGURE 4.35**

The circuit in Figure 4.35 with a parallel connection of  $I_{s2}$  and  $R_b$ .

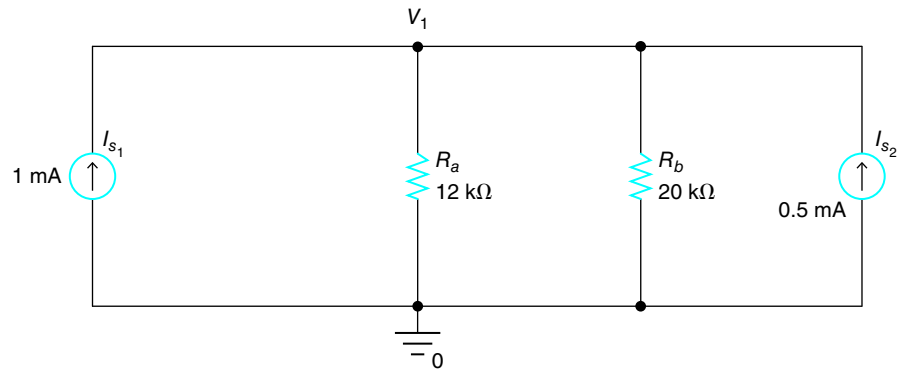**FIGURE 4.36**

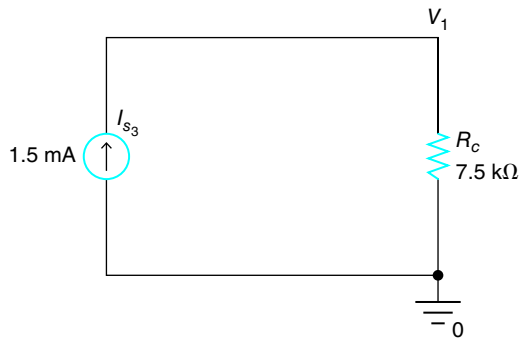A circuit with a parallel connection of  $I_{s3}$  and  $R_c$ .



The two current sources can be combined into a single current source with the current given by

$$I_{s3} = I_{s1} + I_{s2} = 1 \text{ mA} + 0.5 \text{ mA} = 1.5 \text{ mA}$$

The circuit with a current source  $I_{s3}$  and a parallel resistor  $R_c$  is shown in Figure 4.36.

Voltage  $V_1$  is given by


$$V_1 = R_c \times I_{s3} = 7.5 \text{ k}\Omega \times 1.5 \text{ mA} = 11.25 \text{ V}$$

## Exercise 4.4

Find voltage  $V_1$  using source transformation for the circuit shown in Figure 4.37.

**FIGURE 4.37**

Circuit for EXERCISE 4.4.

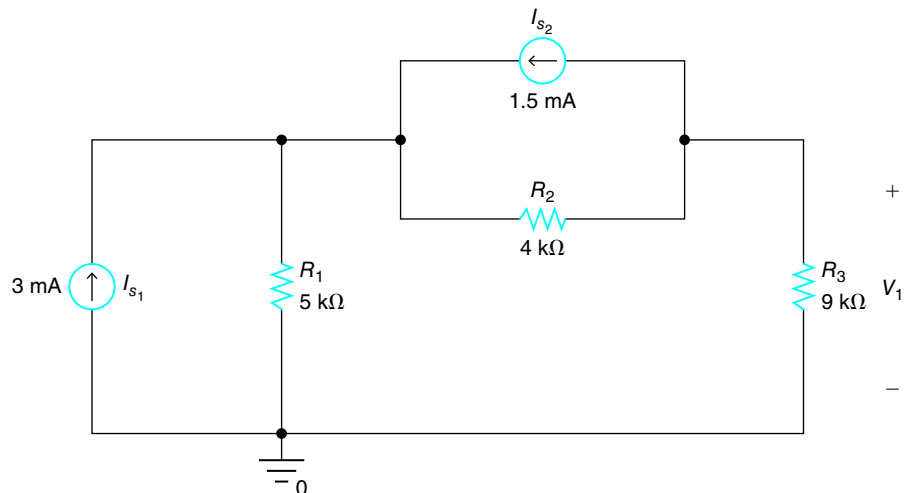


**Answer:**  
 $V_1 = 4.5 \text{ V}.$

## EXAMPLE 4.5

Find voltage  $V$  and current  $I$  using source transformation for the circuit shown in Figure 4.38.

FIGURE 4.38


Circuit for  
EXAMPLE 4.5.

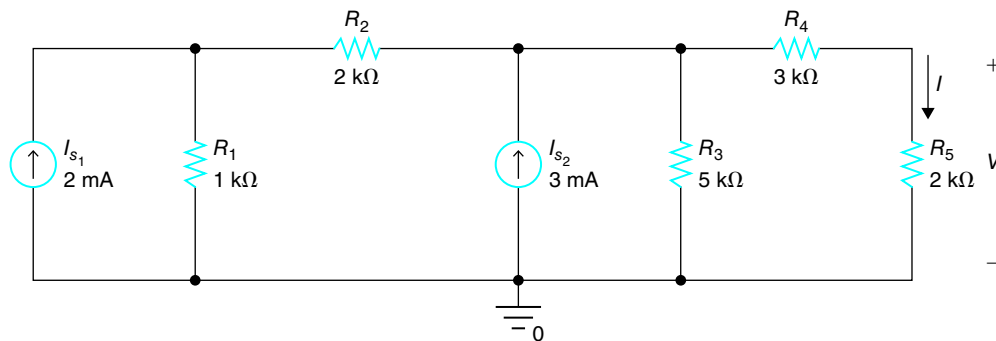

Current source  $I_{s1}$  and resistor  $R_1$  can be transformed into a voltage source with voltage  $V_{s1} = R_1 I_{s1} = 1 \text{ k}\Omega \times 2 \text{ mA} = 2 \text{ V}$  in series with a resistor  $R_1$  with resistance  $1 \text{ k}\Omega$ , as shown in Figure 4.39.

FIGURE 4.39

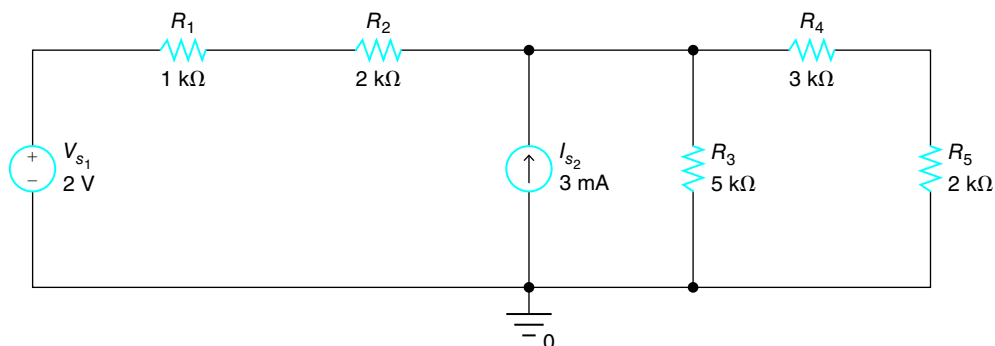
The circuit  
in Figure 4.38 with  $I_{s1}$   
and  $R_1$  replaced  
by  $V_{s1}$  and  $R_1$ .



The equivalent resistance of  $R_1$  and  $R_2$  is given by  $R_6 = R_1 + R_2 = 3 \text{ k}\Omega$ . Figure 4.40 shows the circuit with  $R_6$ .

FIGURE 4.40

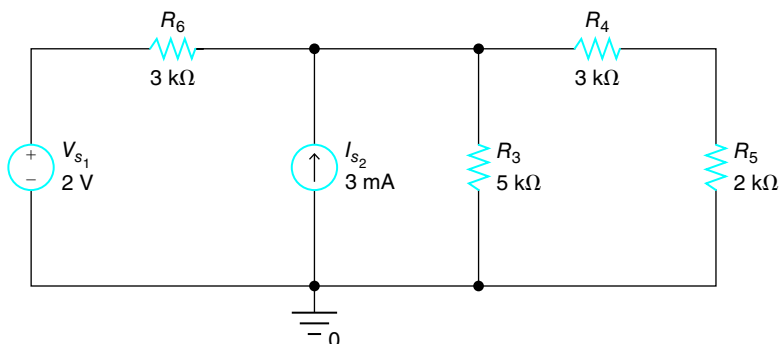The circuit in  
Figure 4.39 with  
 $R_6 = R_1 + R_2$ .




The voltage source  $V_{s1}$  and  $R_6$  can be transformed into a current source with current  $2/3 \text{ mA}$  and a resistor  $R_6$ , as shown in Figure 4.41.

*continued*

Example 4.5 continued

**FIGURE 4.41**

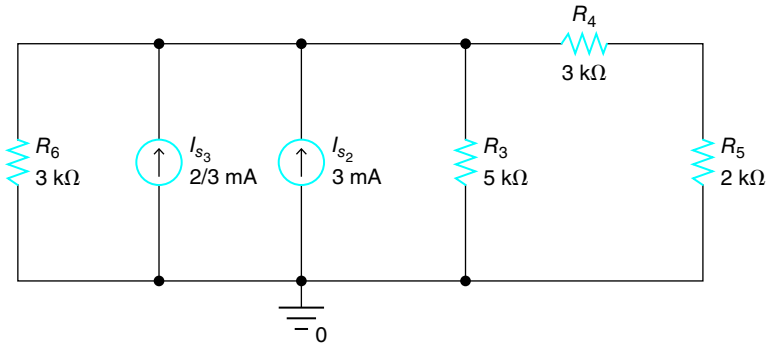
The circuit from Figure 4.40 with  $I_{s_3}$  in parallel with  $R_6$ .



The current sources  $I_{s_2}$  and  $I_{s_3}$  are in parallel and can be combined into a single current source  $I_{s_4}$  with  $2/3 + 3 = 11/3$  mA. The two parallel resistors  $R_3$  and  $R_6$  can be combined into a single resistor  $R_7$  with  $3||5 = 15/8$  kΩ. The circuit shown in Figure 4.41 simplifies to the one shown in Figure 4.42.

**FIGURE 4.42**

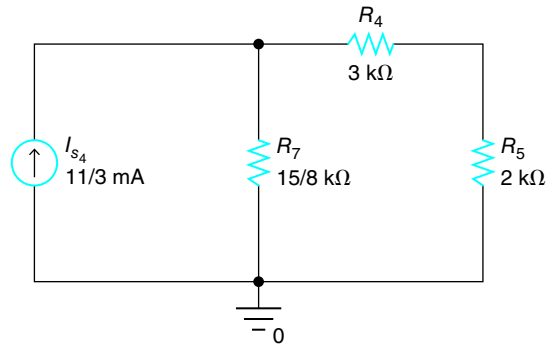The circuit from Figure 4.41 with  $I_{s_4}$  in parallel with  $R_7$ .



The current source  $I_{s_4}$  and the parallel resistor  $R_7$  can be transformed into a voltage source  $V_{s_2}$  with voltage  $(11/3 \text{ mA}) \times (15/8 \text{ kΩ}) = 55/8$  V and the series resistor  $R_7$ , as shown in Figure 4.43.

The equivalent resistance of  $R_7$ ,  $R_4$ , and  $R_5$  is

$$R = R_7 + R_4 + R_5 = \frac{55}{8} \text{ kΩ}$$

Thus, the current  $I$  through the circuit shown in Figure 4.43 is given by


$$I = \frac{V_{s_2}}{R} = 1 \text{ mA}$$

The voltage  $V$  across  $R_5$  is given by

$$V = R_5 I = 2 \text{ kΩ} \times 1 \text{ mA} = 2 \text{ V}$$

**FIGURE 4.43**


The circuit from Figure 4.42 with  $V_{s_2}$  in series with  $R_7$ .

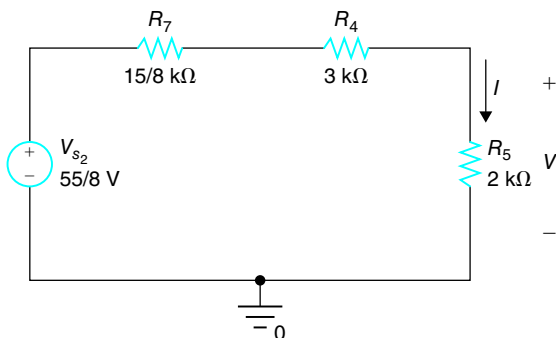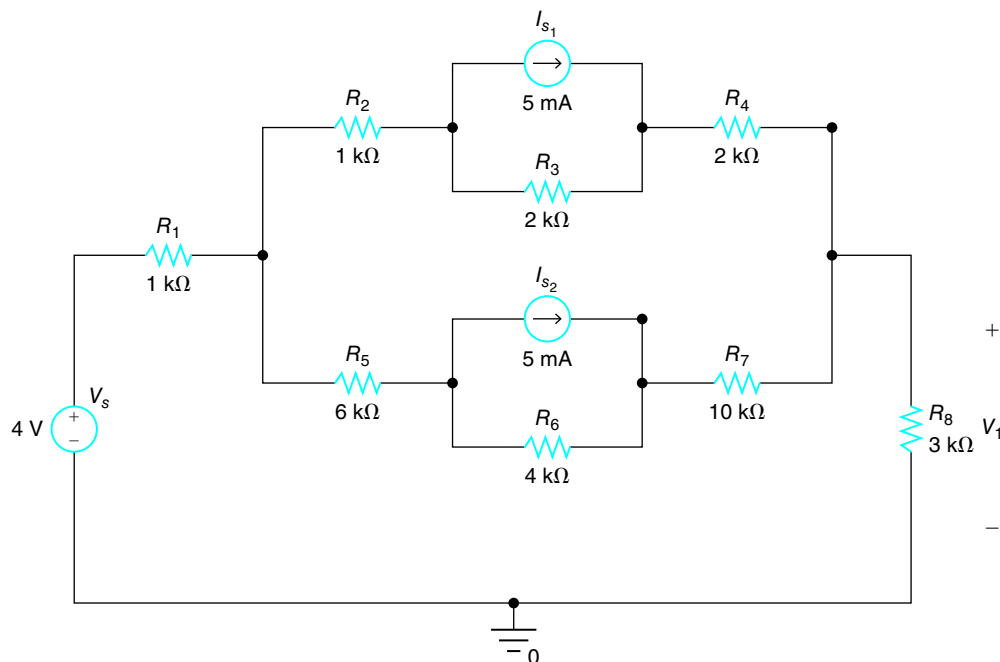

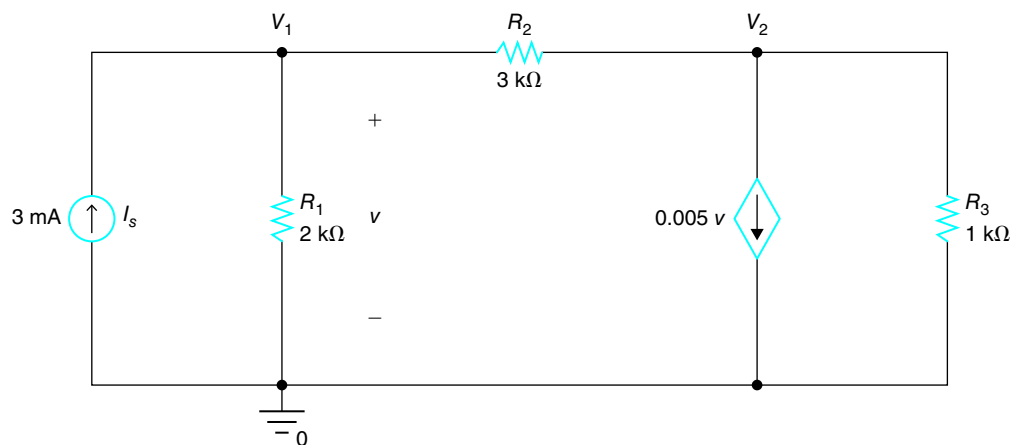


**Exercise 4.5**Find voltage  $V_1$  using source transformation for the circuit shown in Figure 4.44.**FIGURE 4.44**

Circuit for EXERCISE 4.5.

**Answer:**  
 $V_1 = 6 \text{ V}.$ **EXAMPLE 4.6**Find voltage  $V_1$  using source transformation for the circuit shown in Figure 4.45.**FIGURE 4.45**

Circuit for EXAMPLE 4.6.

*continued*

Example 4.6 continued


The VCCS and the parallel resistor  $R_3$  can be transformed into a VCVS with voltage

$$0.005v \times 1000 = 5v$$

and a series resistor  $R_3$ , as shown in Figure 4.46.

**FIGURE 4.46**

The circuit in Figure 4.45 with VCVS.

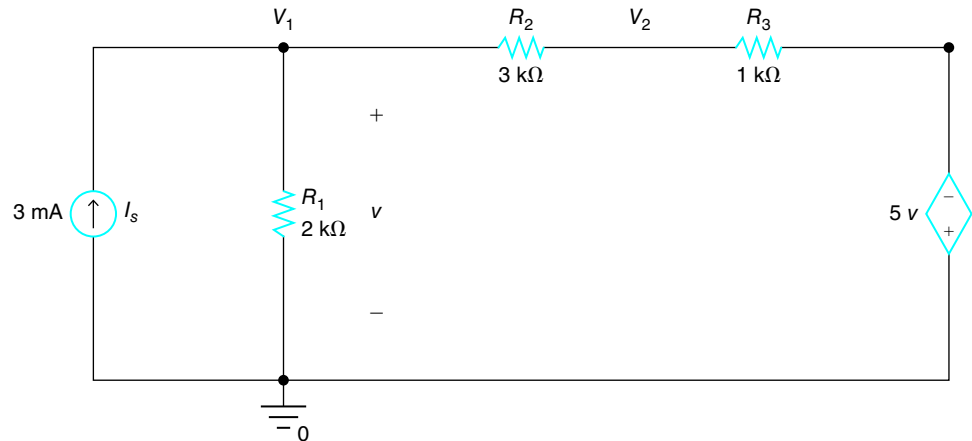

Let  $R_4$  be the sum of  $R_2$  and  $R_3$ . Then, we have

$$R_4 = R_2 + R_3 = 4 \text{ k}\Omega$$


The VCVS and the series resistor  $R_4$  can be transformed into a VCCS with current

$$\frac{-5v}{4000} = -0.00125v$$

and a parallel resistor  $R_4$ , as shown in Figure 4.47.

**FIGURE 4.47**

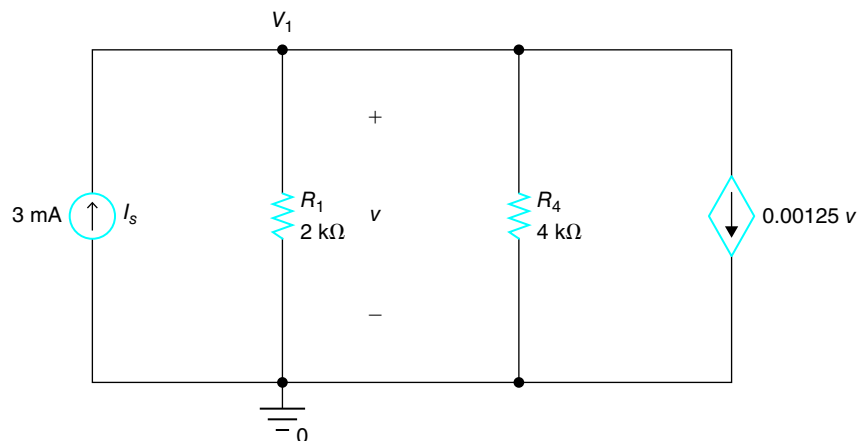The circuit in Figure 4.46 with two current sources in parallel and two resistors in parallel.



The sum of currents from the two current sources is given by

$$0.003 - 0.00125v$$

continued


Example 4.6 continued

and the equivalent resistance  $R_{eq}$  of the parallel connection of  $R_1$  and  $R_4$  is given by

$$R_{eq} = R_1 \parallel R_4 = \frac{R_1 \times R_4}{R_1 + R_4} = \frac{2000 \times 4000}{2000 + 4000} = \frac{8000}{6} = 1.3333 \text{ k}\Omega$$

**FIGURE 4.48**

The final reduced circuit.

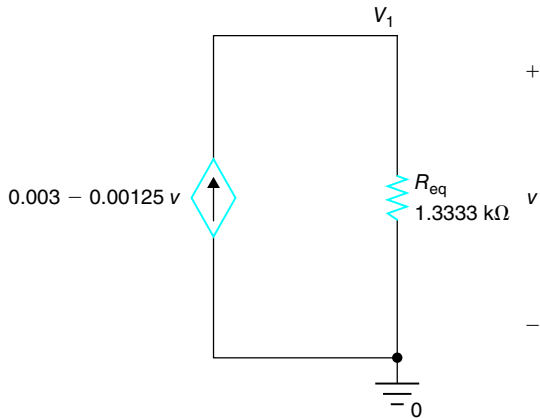

The circuit shown in Figure 4.47 reduces to the one shown in Figure 4.48.

The voltage  $v$ , which is  $V_1$ , is given by, from Ohm's law,


$$v = (0.003 - 0.00125v) \times 1333.3333 = 4 - 1.6667v$$

Solving for  $v$ , we obtain

$$v = V_1 = \frac{4}{2.66667} \text{ V} = 1.5 \text{ V.}$$

**Exercise 4.6**Find voltage  $v$  using the source transformation for the circuit shown in Figure 4.49.**FIGURE 4.49**

Circuit for EXERCISE 4.6.

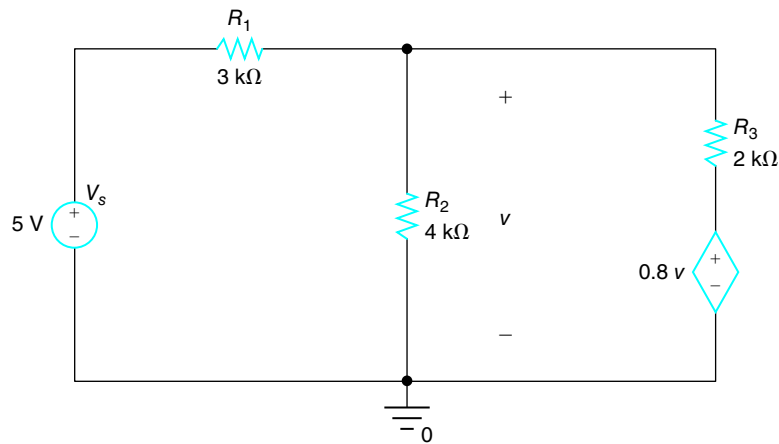**Answer:**


$$v = 2.4390 \text{ V.}$$

**4.4 Thévenin's Theorem**


A circuit consisting of a voltage source  $V_{th}$  and a series resistor  $R_{th}$ , representing the original circuit looking from a pair of terminals, is called a **Thévenin equivalent circuit**. The voltage  $V_{th}$  is called **Thévenin equivalent voltage**, and the resistance  $R_{th}$  is called **Thévenin equivalent resistance**, as shown in Figure 4.50.

**FIGURE 4.50**

A Thévenin equivalent circuit.

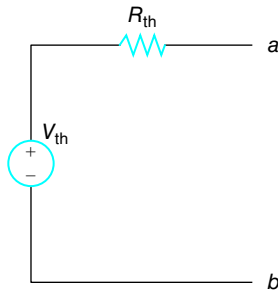**FIGURE 4.51**

Short-circuit current.

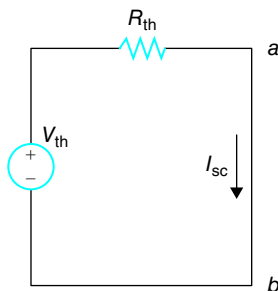

The Thévenin equivalent circuit can be used to simplify the circuit. When a load resistor is connected between terminals  $a$  and  $b$ , we can find the effects of the circuit on the load from the Thévenin equivalent circuit. We do not need all the details of the original circuit to find the voltage, current, and power on the load.

Let the voltage across terminals  $a$  and  $b$  of the Thévenin equivalent circuit be  $V_{oc}$ . This voltage is called *open-circuit voltage* because terminals  $a$  and  $b$  are open (with an infinite resistance between  $a$  and  $b$ ). No current flows on the Thévenin equivalent resistor  $R_{th}$ . Thus,

$$V_{oc} = V_{th}$$

If the terminals  $a$  and  $b$  are short-circuited, as shown in Figure 4.51, the current through the short circuit is given by

$$I_{sc} = \frac{V_{th}}{R_{th}} = \frac{V_{oc}}{R_{th}}$$

If we solve this equation for  $R_{th}$ , we have

$$R_{th} = \frac{V_{oc}}{I_{sc}}$$

This equation can be used to find the Thévenin equivalent resistance  $R_{th}$  from the original circuit.

#### 4.4.1 FINDING THE THÉVENIN EQUIVALENT VOLTAGE $V_{th}$

Given a circuit and terminals  $a$  and  $b$ , we can find the Thévenin equivalent voltage  $V_{th}$  with respect to terminals  $a$  and  $b$  by finding the open-circuit voltage  $V_{oc}$  across terminals  $a$  and  $b$ . The open-circuit voltage  $V_{oc}$  can be found by utilizing circuit analysis methods such as the voltage divider rule, current divider rule, superposition principle, nodal analysis, and mesh analysis. The Thévenin equivalent voltage  $V_{th}$  is found from the original circuit without any changes.

#### 4.4.2 FINDING THE THÉVENIN EQUIVALENT RESISTANCE $R_{th}$

Given a circuit and terminals  $a$  and  $b$ , we can find the Thévenin equivalent resistance  $R_{th}$  with respect to terminals  $a$  and  $b$  by using one of the three methods listed next.

##### Method 1

Deactivate all the independent sources by short-circuiting voltage sources and open-circuiting current sources. Find the equivalent resistance looking into the circuit from terminals  $a$  and  $b$ . This equivalent resistance is the Thévenin equivalent resistance  $R_{th}$ . This method can be used if the circuit does not contain dependent sources.

##### Method 2

Connect terminals  $a$  and  $b$  by wire (short-circuit). Find the short-circuit current  $I_{sc}$  by utilizing circuit analysis methods such as nodal analysis and mesh analysis. The Thévenin equivalent resistance  $R_{th}$  is given by

$$R_{th} = \frac{V_{oc}}{I_{sc}}$$

##### Method 3


Deactivate all the independent sources by open-circuiting current sources and short-circuiting voltage sources. Apply a test voltage of 1 V (or any other value) between terminals  $a$  and  $b$  with terminal  $a$  connected to the positive terminal of the test voltage. Measure

the current flowing out of the positive terminal of the test voltage source. The Thévenin equivalent resistance  $R_{th}$  is given by the ratio of the test voltage to the current flowing out of the positive terminal of the test voltage source. A test current can be used instead of the test voltage. Apply a test current between terminals  $a$  and  $b$  after deactivating the independent sources, and measure the voltage across  $a$  and  $b$  of the test current source. The Thévenin equivalent resistance  $R_{th}$  is the ratio of the voltage across  $a$  and  $b$  to the test current.

Consider a circuit shown in Figure 4.52. We are interested in finding the Thévenin equivalent voltage  $V_{th}$  and the Thévenin equivalent resistance  $R_{th}$  between terminals  $a$  and  $b$ . The Thévenin equivalent voltage  $V_{th}$  is the open-circuit voltage  $V_{oc}$  between terminals  $a$  and  $b$ . The open-circuit voltage is the voltage across the resistor  $R_4$ , which is labeled  $V_2$  in the circuit shown in Figure 4.52.

**FIGURE 4.52**

A circuit with a pair of terminals.

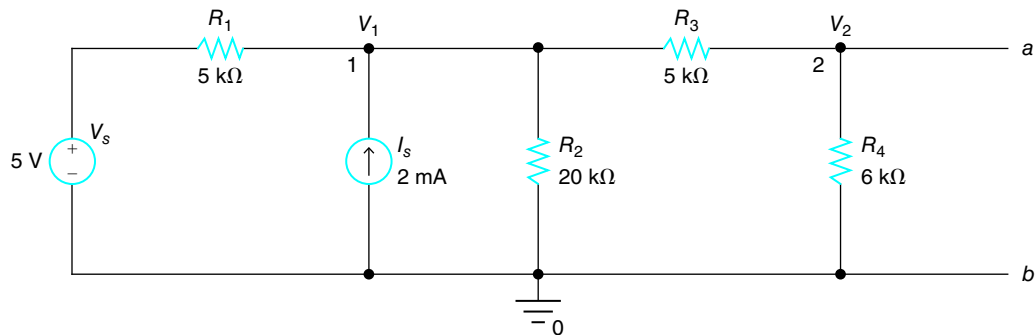

Summing the currents leaving node 1, we obtain

$$\frac{V_1 - 5}{5000} - 0.002 + \frac{V_1}{20,000} + \frac{V_1 - V_2}{5000} = 0$$

Multiplication by 20,000 yields

$$4V_1 - 20 - 40 + V_1 + 4V_1 - 4V_2 = 0$$

which can be rearranged as

$$9V_1 - 4V_2 = 60 \quad (4.22)$$

Summing the currents leaving node 2, we obtain

$$\frac{V_2 - V_1}{5000} + \frac{V_2}{6000} = 0$$

Multiplication by 30,000 yields

$$6V_2 - 6V_1 + 5V_2 = 0$$

which can be rearranged as

$$6V_1 = 11V_2$$

or

$$V_1 = \frac{11}{6}V_2 \quad (4.23)$$

Substituting Equation (4.23) into Equation (4.22), we obtain

$$9\frac{11}{6}V_2 - 4V_2 = \frac{75}{6}V_2 = 60$$

Thus, we have

$$V_2 = 4.8 \text{ V}$$


Since  $V_2$  is the open-circuit voltage between terminals  $a$  and  $b$ , it is the Thévenin equivalent voltage  $V_{th}$ . Thus, we have

$$V_{th} = V_{oc} = 4.8 \text{ V}$$

We will try all three methods to find the Thévenin equivalent resistance  $R_{th}$ . In method 1, we deactivate all independent sources and find the equivalent resistance looking into the circuit from terminals  $a$  and  $b$ . Figure 4.53 shows the circuit shown in Figure 4.52 with the voltage source short-circuited and current source open-circuited.

**FIGURE 4.53**

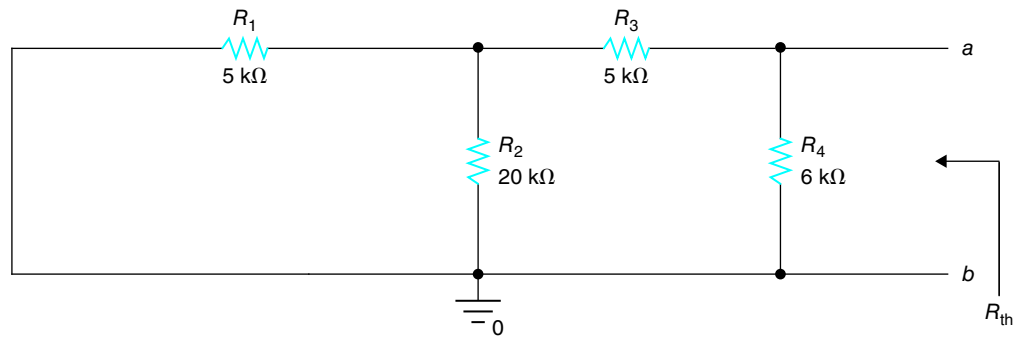The circuit from Figure 4.52 with its sources deactivated.



The equivalent resistance of the parallel connection of  $R_1$  and  $R_2$  is

$$R_a = R_1 \parallel R_2 = 4 \text{ k}\Omega$$

The equivalent resistance of the series connection of  $R_3$  and  $R_a$  is

$$R_b = R_3 + R_a = R_3 + (R_1 \parallel R_2) = 5 \text{ k}\Omega + 4 \text{ k}\Omega = 9 \text{ k}\Omega$$

The Thévenin equivalent resistance,  $R_{th}$ , is the equivalent resistance of parallel connection of  $R_b$  and  $R_4$ . Thus, we have

$$R_{th} = R_b \parallel R_4 = 9 \text{ k}\Omega \parallel 6 \text{ k}\Omega = 3.6 \text{ k}\Omega$$


In method 2, we find the open-circuit voltage  $V_{oc}$  and the short-circuit current  $I_{sc}$ . The Thévenin equivalent resistance between terminals  $a$  and  $b$  is the ratio of  $V_{oc}$  to  $I_{sc}$ . The open-circuit voltage is found to be

$$V_{oc} = V_2 = 4.8 \text{ V}$$

To find the short-circuit current, we connect terminals  $a$  and  $b$  by a wire without changing the rest of the circuit, as shown in Figure 4.54.

**FIGURE 4.54**

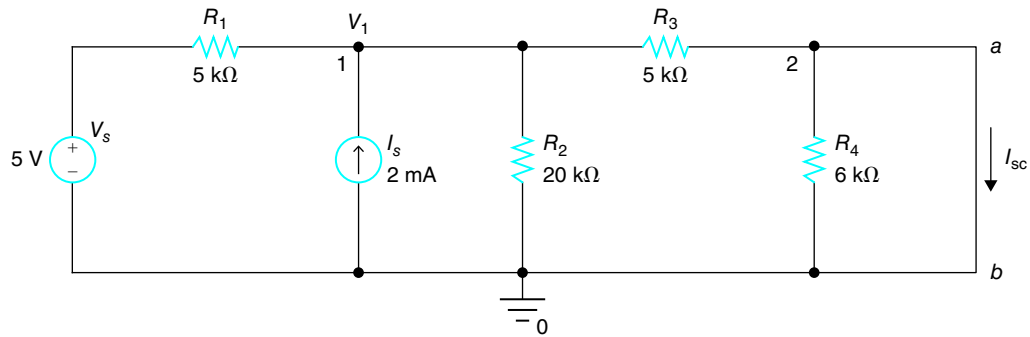A circuit with a short-circuit between  $a$  and  $b$ .



Notice that node 2 is a ground and no current flows through  $R_4$ . The short-circuit current  $I_{sc}$  is the current through  $R_3$  from left to right ( $\rightarrow$ ). Summing the currents leaving node 1, we obtain

$$\frac{V_1 - 5}{5000} - 0.002 + \frac{V_1}{20,000} + \frac{V_1}{5000} = 0$$

Multiplication by 20,000 yields

$$4V_1 - 20 - 40 + V_1 + 4V_1 = 0$$

which can be revised as

$$9V_1 = 60$$

The node voltage at node 1 is given by

$$V_1 = \frac{60}{9} = \frac{20}{3} \text{ V}$$

The current through  $R_3$ , which is also  $I_{sc}$ , is given by

$$I_{sc} = \frac{V_1}{R_3} = \frac{\frac{20}{3} \text{ V}}{5 \text{ k}\Omega} = \frac{4}{3} \text{ mA}$$

The Thévenin equivalent resistance is given by

$$R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{4.8 \text{ V}}{\frac{4}{3} \text{ mA}} = 3.6 \text{ k}\Omega$$


In method 3, we deactivate all independent sources and apply a test voltage across terminals  $a$  and  $b$ . The Thévenin equivalent resistance is the ratio of the test voltage to the current flowing out of the positive terminal of the test voltage. Figure 4.55 shows a circuit with a test voltage source  $V_t$  after deactivating independent sources.

Notice that  $R_1 \parallel R_2 = 4 \text{ k}\Omega$  and  $R_3 + (R_1 \parallel R_2) = 9 \text{ k}\Omega$ . The current through  $R_3$  is

$$I_{R_3} = \frac{V_t}{R_3 + (R_1 \parallel R_2)} = \frac{1 \text{ V}}{9 \text{ k}\Omega} = \frac{1}{9} \text{ mA}$$

**FIGURE 4.55**

Circuit with test voltage.

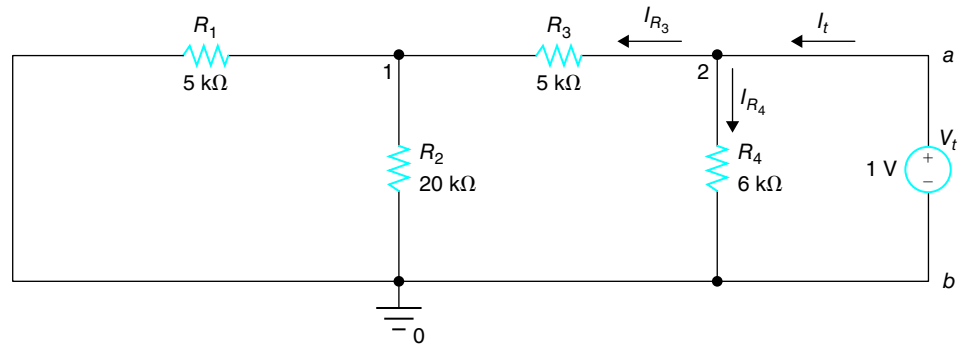

The current through  $R_4$  is

$$I_{R_4} = \frac{V_t}{R_4} = \frac{1 \text{ V}}{6 \text{ k}\Omega} = \frac{1}{6} \text{ mA}$$

The total current flowing out of the positive terminal of the test voltage source is given by

$$I_t = I_{R_3} + I_{R_4} = \frac{1}{9} \text{ mA} + \frac{1}{6} \text{ mA} = \frac{5}{18} \text{ mA}$$


The Thévenin equivalent resistance is given by

$$R_{th} = \frac{V_t}{I_t} = \frac{1 \text{ V}}{\frac{5}{18} \text{ mA}} = \frac{18}{5} \text{ k}\Omega = 3.6 \text{ k}\Omega$$

In method 3, instead of a test voltage source, a test current source can be applied after deactivating the independent sources. Figure 4.56 shows a circuit with a test current source  $I_t$  after deactivating independent sources.

**FIGURE 4.56**

Circuit with a test current.

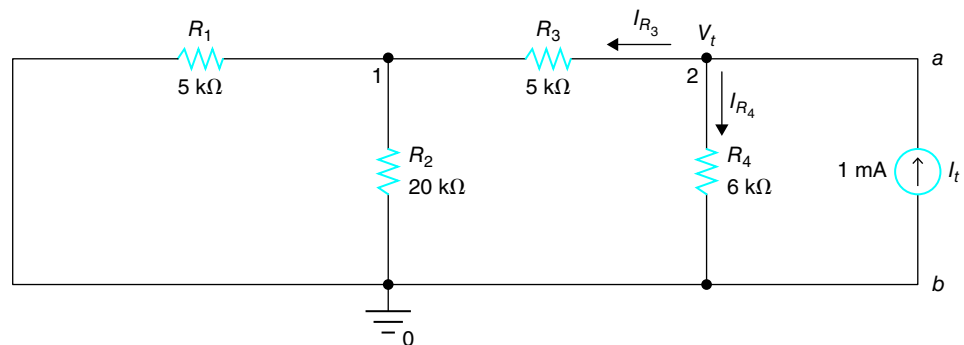

Notice that  $R_1 \parallel R_2 = 4 \text{ k}\Omega$  and  $R_3 + (R_1 \parallel R_2) = 9 \text{ k}\Omega$ . The current through  $R_4$ ,  $I_{R_4}$ , can be obtained by applying the current divider rule:

$$I_{R_4} = I_t \times \frac{9 \text{ k}\Omega}{9 \text{ k}\Omega + 6 \text{ k}\Omega} = 1 \text{ mA} \times \frac{9}{15} = \frac{9}{15} \text{ mA}$$


The voltage across  $R_4$ , which is also the voltage across the test current source, is given by

$$V_t = R_4 I_{R_4} = 6 \text{ k}\Omega \times \frac{9}{15} \text{ mA} = \frac{54}{15} \text{ V} = 3.6 \text{ V}$$



**FIGURE 4.57**

The Thévenin equivalent circuit.

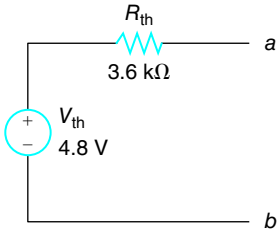

The Thévenin equivalent resistance is given by


$$R_{th} = \frac{V_t}{I_t} = \frac{3.6 \text{ V}}{1 \text{ mA}} = 3.6 \text{ k}\Omega$$

The Thévenin equivalent circuit is shown in Figure 4.57.

A circuit with VCCS is shown in Figure 4.58. We are interested in finding the Thévenin equivalent voltage  $V_{th}$  and the Thévenin equivalent resistance  $R_{th}$  between terminals  $a$  and  $b$ . The Thévenin equivalent voltage  $V_{th}$  is the open-circuit voltage  $V_{oc}$  between terminals  $a$  and  $b$ . The open-circuit voltage is the voltage across the resistor  $R_4$ , which is labeled  $V_2$  in the circuit shown in Figure 4.58. Notice that the controlling voltage  $v$  is equal to  $V_1$ .

**FIGURE 4.58**

A circuit with VCCS.

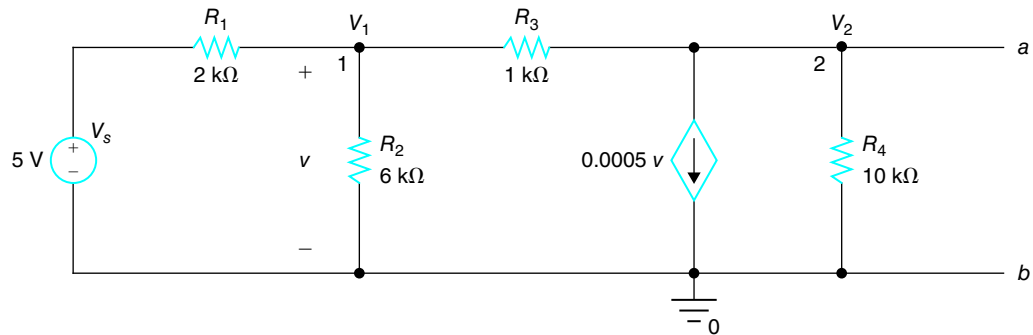

Summing the currents leaving node 1, we obtain

$$\frac{V_1 - 5}{2000} + \frac{V_1}{6000} + \frac{V_1 - V_2}{1000} = 0$$

Multiplication by 6000 yields

$$3V_1 - 15 + V_1 + 6V_1 - 6V_2 = 0,$$

which can be revised as

$$10V_1 - 6V_2 = 15 \quad (4.24)$$

Summing the currents leaving node 2, we obtain

$$\frac{V_2 - V_1}{1000} + 0.0005V_1 + \frac{V_2}{10,000} = 0$$

Multiplication by 10,000 yields

$$10V_2 - 10V_1 + 5V_1 + V_2 = 0$$

which can be revised as

$$5V_1 = 11V_2$$

or

$$V_1 = \frac{11}{5}V_2 = 2.2V_2 \quad (4.25)$$

Substituting Equation (4.25) into Equation (4.24), we obtain

$$10 \times 2.2V_2 - 6V_2 = 16V_2 = 15$$

Thus, we have

$$V_2 = \frac{15}{16} \text{ V} = 0.9375 \text{ V}$$

Since  $V_2$  is the open-circuit voltage between terminals  $a$  and  $b$ , it is the Thévenin equivalent voltage  $V_{th}$ . Thus, we have

$$V_{th} = 0.9375 \text{ V}$$


Since the circuit contains a dependent source, method 1 cannot be used to find the Thévenin equivalent resistance  $R_{th}$ . We will try method 2 and method 3. In method 2, we find the open-circuit voltage  $V_{oc}$  and the short-circuit current  $I_{sc}$ . The Thévenin equivalent resistance between terminals  $a$  and  $b$  is the ratio of  $V_{oc}$  to  $I_{sc}$ . The open-circuit voltage is found to be

$$V_{oc} = V_2 = 0.9375 \text{ V}$$

To find the short-circuit current, we connect terminals  $a$  and  $b$  by a wire without changing the rest of the circuit, as shown in Figure 4.59.

**FIGURE 4.59**

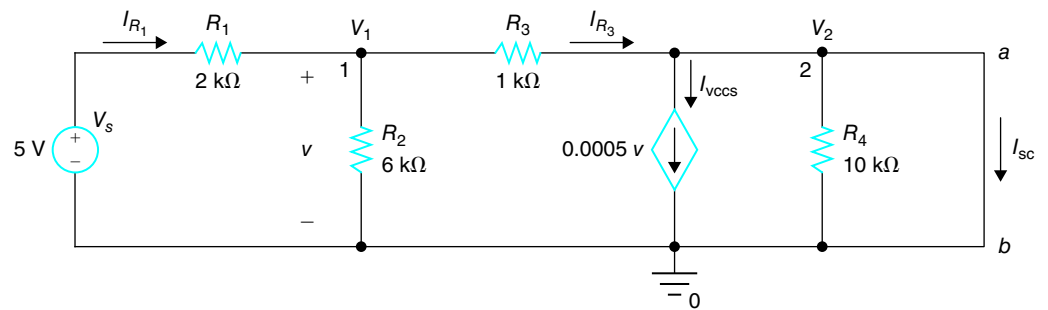A circuit with a short circuit between  $a$  and  $b$ .



Notice that node 2 is a ground and no current flows through  $R_4$ . The short-circuit current  $I_{sc}$  is the current through  $R_3$ ,  $I_{R_3}$ , minus the current through VCCS. The equivalent resistance of the parallel connection of  $R_2$  and  $R_3$  is given by

$$R_2 \parallel R_3 = \frac{6}{7} \text{ k}\Omega = 0.857143 \text{ k}\Omega$$

The total resistance seen from the voltage source  $V_s$  is given by

$$R_1 + (R_2 \parallel R_3) = 2 \text{ k}\Omega + \frac{6}{7} \text{ k}\Omega = \frac{20}{7} \text{ k}\Omega = 2.857143 \text{ k}\Omega$$

The current through  $R_1$  is given by

$$I_{R_1} = \frac{V_s}{R_1 + (R_2 \parallel R_3)} = \frac{5 \text{ V}}{\frac{20}{7} \text{ k}\Omega} = \frac{35}{20} \text{ mA} = 1.75 \text{ mA}$$

Voltage  $V_1$  is given by

$$V_1 = V_s - R_1 \times I_{R_1} = 5 \text{ V} - 1.75 \text{ mA} \times 2 \text{ k}\Omega = 1.5 \text{ V}$$

Since the controlling voltage  $v$  is identical to  $V_1$ , we have

$$v = V_1 = 1.5 \text{ V}$$

The current through  $R_3$  is given by

$$I_{R_3} = \frac{V_1}{R_3} = \frac{1.5 \text{ V}}{1 \text{ k}\Omega} = 1.5 \text{ mA}$$

The current through VCCS is given by

$$I_{VCCS} = 0.0005 \times V_1 = 0.0005 \times 1.5 \text{ A} = 0.75 \text{ mA}$$

The short-circuit current is the difference of  $I_{R_3}$  and  $I_{VCCS}$ . Thus, we have

$$I_{sc} = I_{R_3} - I_{VCCS} = 1.5 \text{ mA} - 0.75 \text{ mA} = 0.75 \text{ mA}$$


The Thévenin equivalent resistance is given by

$$R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{0.9375 \text{ V}}{0.75 \text{ mA}} = 1.25 \text{ k}\Omega$$

In method 3, we deactivate the independent voltage source and apply a test voltage across terminals  $a$  and  $b$ . The Thévenin equivalent resistance is the ratio of the test voltage to the current flowing out of the positive terminal of the test voltage source. Figure 4.60 shows a circuit with test voltage source  $V_t$  after deactivating the independent source.

**FIGURE 4.60**

A circuit with test voltage.

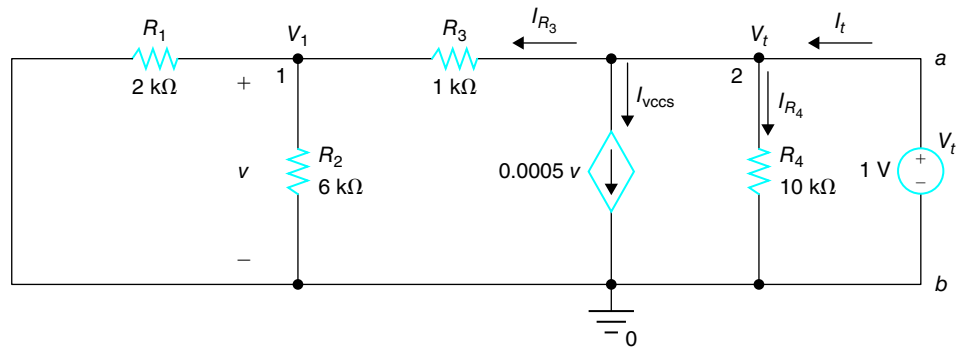

Notice that  $R_1 \parallel R_2 = 1.5 \text{ k}\Omega$  and  $R_3 + (R_1 \parallel R_2) = 2.5 \text{ k}\Omega$ . The current through  $R_3$  is

$$I_{R_3} = \frac{V_t}{R_3 + (R_1 \parallel R_2)} = \frac{1 \text{ V}}{2.5 \text{ k}\Omega} = 0.4 \text{ mA}$$

The voltage at node 1 is given by

$$V_1 = v = V_t - R_3 \times I_{R_3} = 1 \text{ V} - 1 \text{ k}\Omega \times 0.4 \text{ mA} = 1 \text{ V} - 0.4 \text{ V} = 0.6 \text{ V}$$

The current through the VCCS is given by

$$I_{VCCS} = 0.0005v = 0.0005 \times 0.6 \text{ V} = 0.0003 \text{ A} = 0.3 \text{ mA}$$

The current through  $R_4$  is

$$I_{R_4} = \frac{V_t}{R_4} = \frac{1 \text{ V}}{10 \text{ k}\Omega} = 0.1 \text{ mA}$$

The total current flowing out of the positive terminal of the test voltage source is given by

$$I_t = I_{R_3} + I_{V_{CCS}} + I_{R_4} = 0.4 \text{ mA} + 0.3 \text{ mA} + 0.1 \text{ mA} = 0.8 \text{ mA}$$


The Thévenin equivalent resistance is given by

$$R_{th} = \frac{V_t}{I_t} = \frac{1 \text{ V}}{0.8 \text{ mA}} = 1.25 \text{ k}\Omega$$

In method 3, instead of test voltage, a test current can be applied after deactivating the independent voltage source. Figure 4.61 shows a circuit with test current source  $I_t$  after deactivating the independent voltage source.

**FIGURE 4.61**

A circuit with a test current.

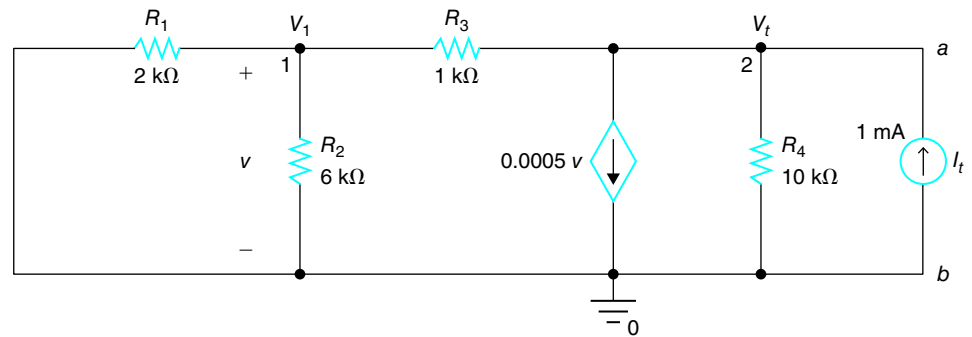

Summing the currents leaving node 1, we obtain

$$\frac{V_1}{2000} + \frac{V_1}{6000} + \frac{V_1 - V_t}{1000} = 0$$

Multiplication by 6000 yields

$$3V_1 + V_1 + 6V_1 - 6V_t = 0$$

which can be revised as

$$10V_1 - 6V_t = 0$$

Solving for  $V_1$ , we get

$$V_1 = 0.6V_t \quad (4.26)$$

Summing the currents leaving node 2, we obtain

$$\frac{V_t - V_1}{1000} + 0.0005V_1 + \frac{V_t}{10,000} - 0.001 = 0$$

Multiplication by 10,000 yields

$$10V_t - 10V_1 + 5V_1 + V_t - 10 = 0$$

which can be revised as

$$-5V_1 + 11V_t = 10 \quad (4.27)$$

Substitution of Equation (4.26) into Equation (4.27) yields

$$-5(0.6V_t) + 11V_t = 8V_t = 10$$

Thus, we have

$$V_t = \frac{10}{8} \text{ V} = 1.25 \text{ V}$$


The Thévenin equivalent resistance is given by

$$R_{th} = \frac{V_t}{I_t} = \frac{1.25 \text{ V}}{1 \text{ mA}} = 1.25 \text{ k}\Omega$$

A Thévenin equivalent circuit is shown in Figure 4.62.

**FIGURE 4.62**

Thévenin equivalent circuit.

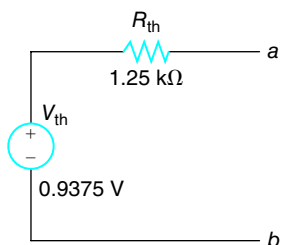


### EXAMPLE 4.7

Find the Thévenin equivalent voltage and the Thévenin equivalent resistance between  $a$  and  $b$  in the circuit shown in Figure 4.63.

**FIGURE 4.63**

Circuit for  
EXAMPLE 4.7.

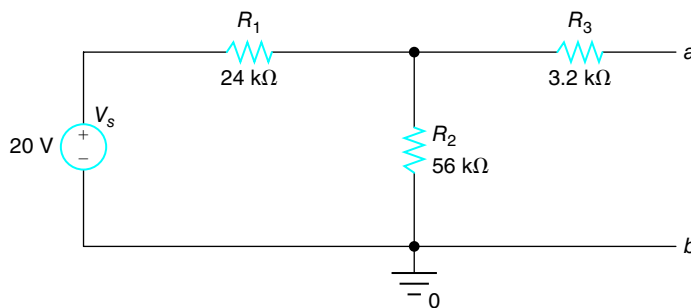


Since  $a$  and  $b$  is an open circuit, resistance between  $a$  and  $b$  is infinite. There is no current flowing through  $R_3$ . Therefore, there is no voltage drop across  $R_3$ . The open-circuit voltage between  $a$  and  $b$  is identical to the voltage across  $R_2$ . From the voltage divider rule, we have

$$V_{th} = V_{oc} = V_s \times \frac{R_2}{R_1 + R_2} = 20 \text{ V} \times \frac{56 \text{ k}\Omega}{24 \text{ k}\Omega + 56 \text{ k}\Omega} = 14 \text{ V}$$

To find the Thévenin equivalent resistance, we deactivate the voltage source by short-circuiting it, as shown in Figure 4.64.

**FIGURE 4.64**

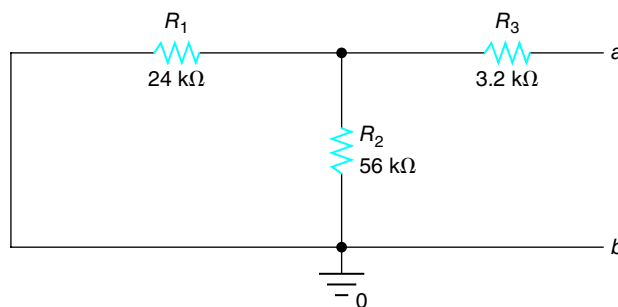Circuit in Figure 4.63  
after deactivating the  
voltage source.




*continued*

Example 4.7 continued

**FIGURE 4.65**

The Thévenin equivalent circuit.

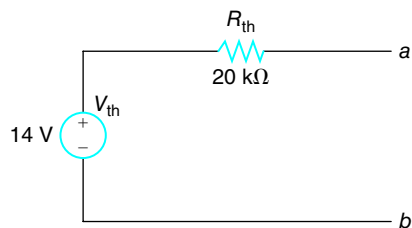
The equivalent resistance to the left of  $a$  and  $b$  is given by

$$R_{th} = R_3 + (R_1 \parallel R_2) = R_3 + \frac{R_1 \times R_2}{R_1 + R_2} = 3.2 \text{ k}\Omega + \frac{24 \text{ k}\Omega \times 56 \text{ k}\Omega}{24 \text{ k}\Omega + 56 \text{ k}\Omega} \\ = 3.2 \text{ k}\Omega + 16.8 \text{ k}\Omega = 20 \text{ k}\Omega$$

When the circuit is replaced by a Thévenin equivalent circuit, the original circuit shown in Figure 4.63 becomes the circuit shown in Figure 4.65.

**Exercise 4.7**Find the Thévenin equivalent circuit between  $a$  and  $b$  in the circuit shown in Figure 4.66.**FIGURE 4.66**


Circuit for EXERCISE 4.7.

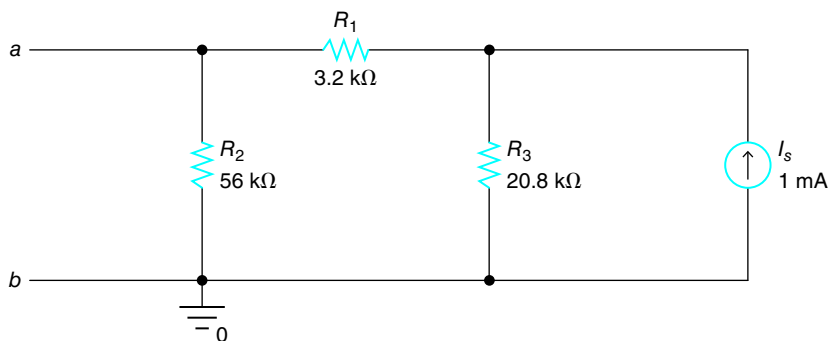**Answer:**

$$V_{th} = 14.56 \text{ V}, R_{th} = 16.8 \text{ k}\Omega.$$

**EXAMPLE 4.8**Find the Thévenin equivalent voltage and the Thévenin equivalent resistance between  $a$  and  $b$  in the circuit shown in Figure 4.67.**FIGURE 4.67**

Circuit for EXAMPLE 4.8.

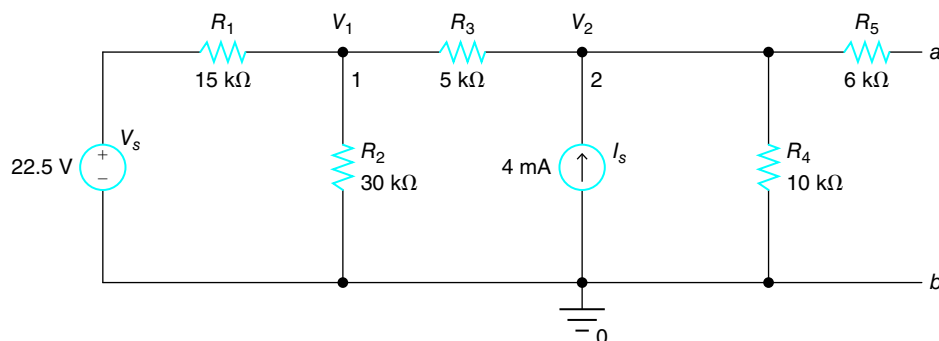


continued

Example 4.8 continued

Since no current flows through  $R_5$ , the Thévenin equivalent voltage is the voltage across  $R_4$ , which is labeled  $V_2$  in the circuit shown in Figure 4.67. The superposition principle will be applied to find the Thévenin equivalent voltage. When the current source is deactivated, the circuit reduces to the one shown in Figure 4.68.

**FIGURE 4.68**

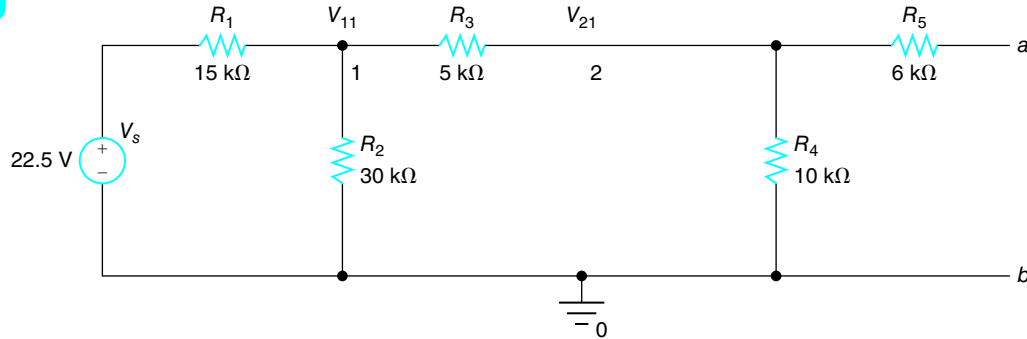The circuit shown in Figure 4.67 with  $I_s$  deactivated.



The equivalent resistance of the parallel connection of  $R_2$  and  $R_3 + R_4$  is given by

$$R_2 \parallel (R_3 + R_4) = 30 \text{ k}\Omega \parallel 15 \text{ k}\Omega = 10 \text{ k}\Omega$$

Application of the voltage divider rule results in

$$V_{11} = V_s \times \frac{R_2 \parallel (R_3 + R_4)}{R_1 + [R_2 \parallel (R_3 + R_4)]} = 22.5 \text{ V} \times \frac{10 \text{ k}\Omega}{15 \text{ k}\Omega + 10 \text{ k}\Omega} = 9 \text{ V}$$


Application of the voltage divider rule to  $R_3$  and  $R_4$  results in

$$V_{21} = V_{11} \times \frac{R_4}{R_3 + R_4} = 9 \text{ V} \times \frac{10 \text{ k}\Omega}{5 \text{ k}\Omega + 10 \text{ k}\Omega} = 6 \text{ V}$$

When the voltage source is deactivated, the circuit shown in Figure 4.67 reduces to the one shown in Figure 4.69.

**FIGURE 4.69**

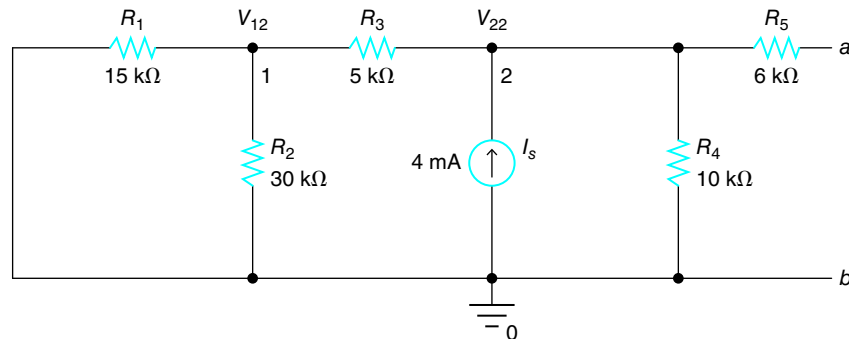The circuit shown in Figure 4.67 with  $V_s$  deactivated.



Let  $R_a$  be the equivalent resistance of  $R_3 + (R_1 \parallel R_2)$ . Then, we have

$$R_a = R_3 + (R_1 \parallel R_2) = 5 \text{ k}\Omega + (15 \text{ k}\Omega \parallel 30 \text{ k}\Omega) = 5 \text{ k}\Omega + 10 \text{ k}\Omega = 15 \text{ k}\Omega$$

continued

Example 4.8 continued

From the current divider rule, the current through  $R_4$  is given by

$$I_{R_4} = I_s \times \frac{R_a}{R_a + R_4} = 4 \text{ mA} \times \frac{15 \text{ k}\Omega}{15 \text{ k}\Omega + 10 \text{ k}\Omega} = 2.4 \text{ mA}$$

The voltage across  $R_4$  is given by

$$V_{22} = R_4 \times I_{R_4} = 10 \text{ k}\Omega \times 2.4 \text{ mA} = 24 \text{ V}$$


The open-circuit voltage, which is the Thévenin equivalent voltage, is the sum of  $V_{21}$  and  $V_{22}$ :

$$V_{th} = V_{oc} = V_2 = V_{21} + V_{22} = 6 \text{ V} + 24 \text{ V} = 30 \text{ V}$$

To find the Thévenin equivalent resistance  $R_{th}$ , we deactivate the sources by short-circuiting the voltage source and open-circuiting the current source, as shown in Figure 4.70.

**FIGURE 4.70**

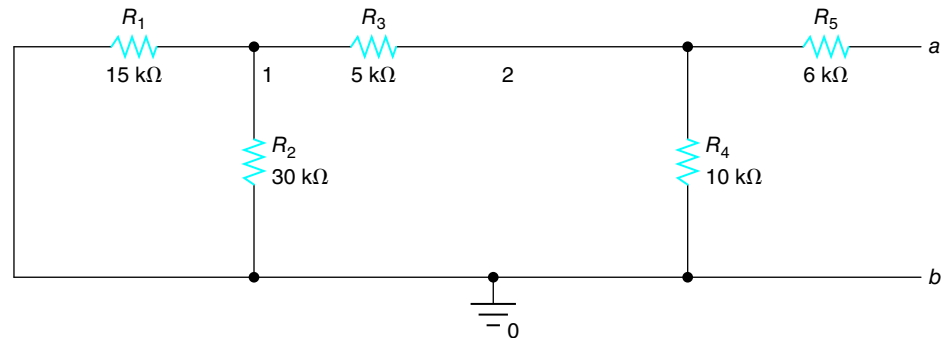The circuit shown in Figure 4.67 after deactivating the sources.



We find the equivalent resistance starting from the left side of the circuit and moving toward terminals  $a$  and  $b$ . The equivalent resistance of the parallel connection of  $R_1$  and  $R_2$  is given by

$$R_1 \parallel R_2 = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{15 \text{ k}\Omega \times 30 \text{ k}\Omega}{15 \text{ k}\Omega + 30 \text{ k}\Omega} = \frac{30 \text{ k}\Omega}{1 + 2} = 10 \text{ k}\Omega$$

$R_1 \parallel R_2$  is in series with  $R_3$ . Thus, we have

$$(R_1 \parallel R_2) + R_3 = 10 \text{ k}\Omega + 5 \text{ k}\Omega = 15 \text{ k}\Omega.$$

$(R_1 \parallel R_2) + R_3$  is in parallel with  $R_4$ . Thus, we have

$$[(R_1 \parallel R_2) + R_3] \parallel R_4 = \frac{15 \text{ k}\Omega \times 10 \text{ k}\Omega}{15 \text{ k}\Omega + 10 \text{ k}\Omega} = \frac{30 \text{ k}\Omega}{5} = 6 \text{ k}\Omega$$


The Thévenin equivalent resistance is the sum of  $6 \text{ k}\Omega$  and  $R_5$ ; i.e.,

$$R_{th} = 6 \text{ k}\Omega + 6 \text{ k}\Omega = 12 \text{ k}\Omega$$

The Thévenin equivalent circuit is shown in Figure 4.71.

**FIGURE 4.71**

The Thévenin equivalent circuit.

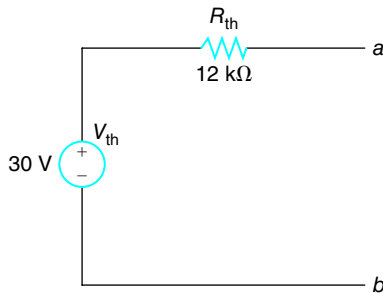




**Exercise 4.8**

Find the Thévenin equivalent voltage and the Thévenin equivalent resistance between  $a$  and  $b$  in the circuit shown in Figure 4.72.

**FIGURE 4.72**

Circuit for  
EXERCISE 4.8.

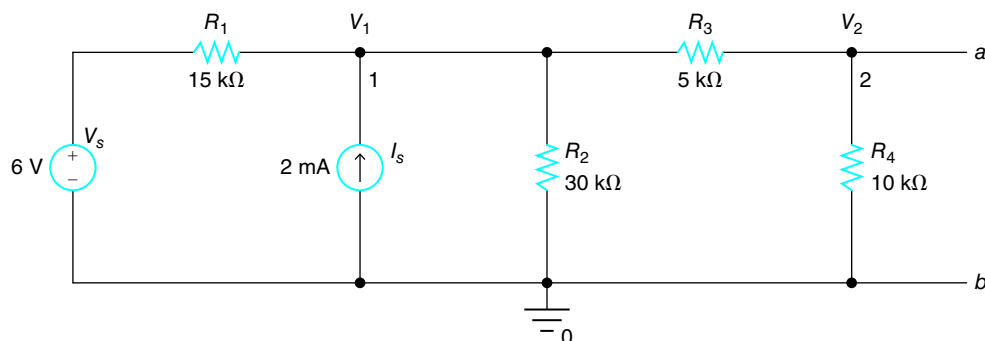

**Answer:**


$$V_{th} = 9.6 \text{ V}, R_{th} = 6 \text{ k}\Omega.$$

**EXAMPLE 4.9**

Find the Thévenin equivalent circuit between terminals  $a$  and  $b$  for the circuit shown in Figure 4.73.

**FIGURE 4.73**

Circuit for  
EXAMPLE 4.9.

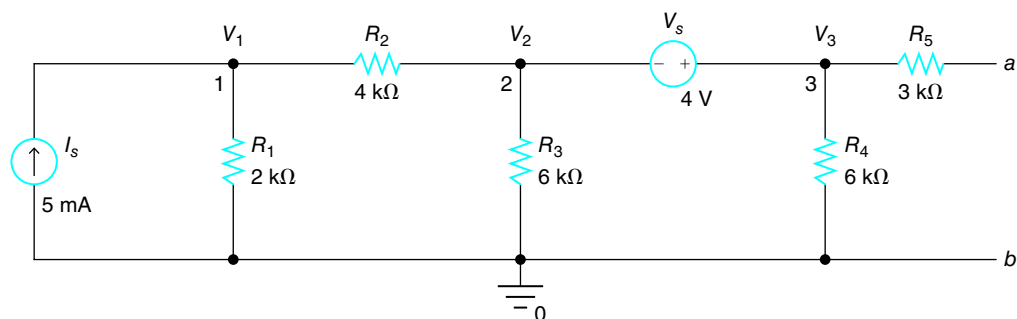

Voltage  $V_3$  at node 3 is 4 V higher than voltage  $V_2$  at node 2. Thus, we have

$$V_3 = V_2 + 4 \quad (4.28)$$

Summing the currents away from node 1, we get

$$-5 \times 10^{-3} + \frac{V_1}{2000} + \frac{V_1 - V_2}{4000} = 0 \quad (4.29)$$

Multiplication of Equation (4.29) by 4000 yields

$$2V_1 + V_1 - V_2 = 20$$

which reduces to

$$3V_1 - V_2 = 20 \quad (4.30)$$

*continued*

Example 4.9 continued

Summing the currents away from nodes 2 and 3 (i.e., the supernode, as discussed in Chapter 3), we have

$$\frac{V_2 - V_1}{4000} + \frac{V_2}{6000} + \frac{V_3}{6000} = 0 \quad (4.31)$$

Since one end of  $R_5$  is open, there is no current through  $R_5$ . Thus, the voltage drop across  $R_5$  is zero. Substitution of Equation (4.28) into Equation (4.31) results in

$$\frac{V_2 - V_1}{4000} + \frac{V_2}{6000} + \frac{V_2 + 4}{6000} = 0 \quad (4.32)$$

Multiplication of Equation (4.32) by 12,000 yields

$$3V_2 - 3V_1 + 2V_2 + 2V_2 + 8 = 0$$

which reduces to

$$-3V_1 + 7V_2 = -8 \quad (4.33)$$

Summing Equations (4.30) and (4.33) results in

$$6V_2 = 12$$


Thus,  $V_2 = 2$  V. Substituting this into Equation (4.30), we get  $V_1 = 22/3$  V = 7.3333 V. The Thévenin voltage is  $V_3$ , which is the sum of  $V_2$  and 4 V from the voltage source  $V_s$ . Thus,

$$V_{th} = V_3 = V_2 + 4 \text{ V} = 2 \text{ V} + 4 \text{ V} = 6 \text{ V}$$

In method 2 of finding the Thévenin equivalent resistance, the terminals  $a$  and  $b$  are short-circuited, as shown in Figure 4.74.

**FIGURE 4.74**

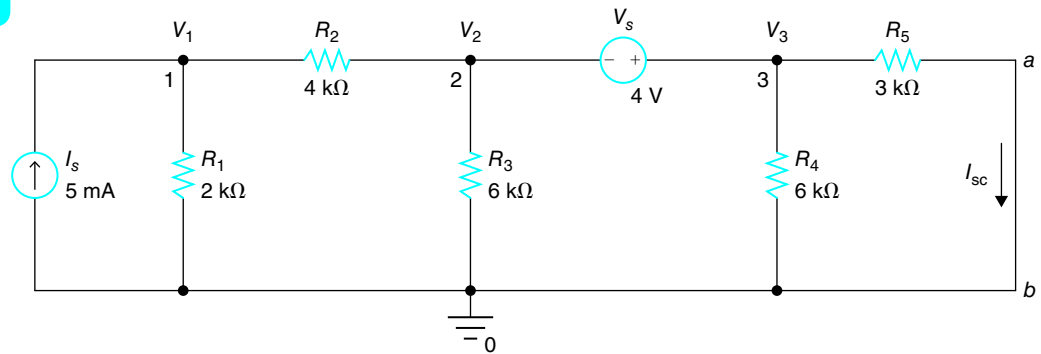Terminals  $a$  and  $b$  are short-circuited.



To find the short-circuit current  $I_{sc}$  for the circuit shown in Figure 4.46, we modify Equation (4.32) to include the current through the resistor  $R_5$ :

$$\frac{V_2 - V_1}{4000} + \frac{V_2}{6000} + \frac{V_3}{6000} + \frac{V_3}{3000} = 0 \quad (4.34)$$

Substitution of Equation (4.28) into Equation (4.34) yields

$$\frac{V_2 - V_1}{4000} + \frac{V_2}{6000} + \frac{V_2 + 4}{6000} + \frac{V_2 + 4}{3000} = 0 \quad (4.35)$$

Multiplying Equation (4.35) by 12,000, we get

$$3V_2 - 3V_1 + 2V_2 + 2V_2 + 8 + 4V_2 + 16 = 0$$

continued

Example 4.9 continued

which can be simplified to

$$-3V_1 + 11V_2 = -24 \quad (4.36)$$

Summing Equations (4.30) and (4.36) yields

$$10V_2 = -4$$

from which we get  $V_2 = -0.4$  V. Thus,  $V_3 = V_2 + 4 = 3.6$  V. The short-circuit current is given by

$$I_{sc} = \frac{V_3}{R_3} = \frac{3.6 \text{ V}}{3 \text{ k}\Omega} = 1.2 \text{ mA}$$

Thus, the Thévenin equivalent resistance is given by


$$R_{th} = \frac{V_{th}}{I_{sc}} = \frac{6 \text{ V}}{1.2 \text{ mA}} = 5 \text{ k}\Omega$$

The Thévenin equivalent circuit between terminals  $a$  and  $b$  is shown in Figure 4.75.


The Thévenin equivalent resistance can also be found using method 1. If current source  $I_s$  and voltage source  $V_s$  are deactivated (i.e., open-circuit the current source and short-circuit the voltage source) from the circuit shown in Figure 4.73, we obtain the circuit shown in Figure 4.76.

**FIGURE 4.75**

The Thévenin equivalent circuit.

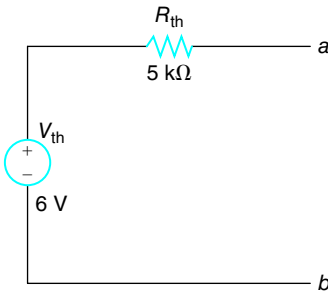**FIGURE 4.76**

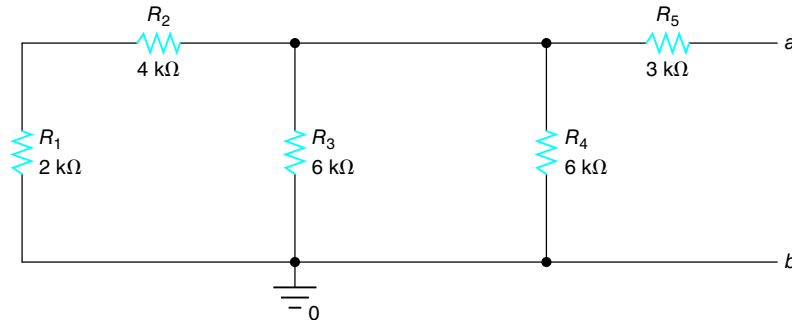Circuit shown in Figure 4.73 with the sources deactivated.



The equivalent resistance of the series connection of  $R_1$  and  $R_2$  is  $2 \text{ k}\Omega + 4 \text{ k}\Omega = 6 \text{ k}\Omega$ . The equivalent resistance of the parallel connection of  $R_1 + R_2$  and  $R_3$  is given by  $6 \text{ k}\Omega \parallel 6 \text{ k}\Omega = 3 \text{ k}\Omega$ . The equivalent resistance of this result ( $3 \text{ k}\Omega$ ) and  $R_4$  is  $3 \text{ k}\Omega \parallel 6 \text{ k}\Omega = 18 \text{ k}\Omega / 9 = 2 \text{ k}\Omega$ . The series connection of this result ( $2 \text{ k}\Omega$ ) and  $R_5$  yields  $2 \text{ k}\Omega + 3 \text{ k}\Omega = 5 \text{ k}\Omega$ . Thus, the Thévenin equivalent resistance is  $5 \text{ k}\Omega$ .

The Thévenin equivalent resistance can also be found using method 3. If a test voltage source with voltage of 1 V is applied between terminals  $a$  and  $b$  of the circuit shown in Figure 4.73 after deactivating sources, we obtain the circuit shown in Figure 4.77.

Summing the currents away from node 1 of the circuit shown in Figure 4.77, we obtain

$$\frac{V_1}{2000 + 4000} + \frac{V_1}{6000} + \frac{V_1}{6000} + \frac{V_1 - 1}{3000} = 0 \quad (4.37)$$

Multiplication of Equation (4.37) by 6000 results in


$$5V_1 = 2 \quad (4.38)$$

continued

Example 4.9 continued

**FIGURE 4.77**

Circuit with a test voltage.

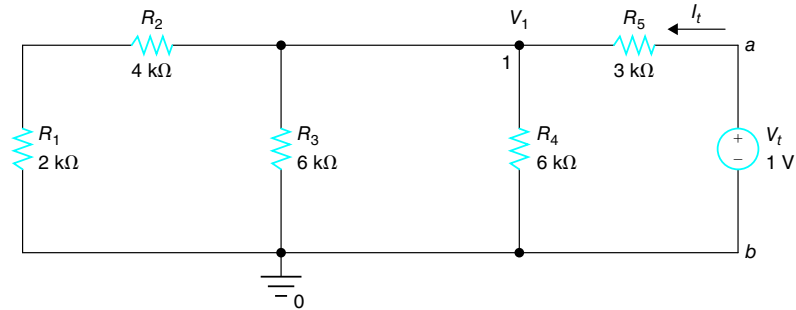

The solution of Equation (4.38) is  $V_1 = 2/5 \text{ V} = 0.4 \text{ V}$ . Current  $I_t$  is given by

$$I_t = \frac{V_t - V_1}{R_5} = \frac{1 \text{ V} - \frac{2}{5} \text{ V}}{3000} = \frac{1}{5} \text{ mA} = 0.2 \text{ mA}$$

Thus, the Thévenin equivalent resistance is given by

$$R_{th} = \frac{V_t}{I_t} = \frac{1 \text{ V}}{\frac{1}{5} \text{ mA}} = 5 \text{ k}\Omega$$

**MATLAB**

```
%EXAMPLE 4.9
%Function P.m should be in the same folder as this file.
clear all;
Is=5e-3;Vs=4;R1=2000;R2=4000;R3=6000;R4=6000;R5=3000;Vt=1;
syms V1 V2 V3 Va Vb Vc Vd
%Voc = Vth
[V1,V2,V3]=solve(V3==V2+Vs,...
-Is+V1/R1+(V1-V2)/R2,...
(V2-V1)/R2+V2/R3+V3/R4);
Vth=V3;
%Method 2: Rth2 = Voc/Isc = Vth/Isc
[Va,Vb,Vc]=solve(Vc==Vb+Vs,...
-Is+Va/R1+(Va-Vb)/R2,...
(Vb-Va)/R2+Vb/R3+Vc/R4+Vc/R5);
Isc=Vc/R5;
Rth2=Vth/Isc;
%Method 1: Rth1 = Req
Rth1=R5+P([R4,R3,R2+R1]);
%Method 3: Rth3 = Vt/It (test voltage)
Vd=solve(Vd/(R2+R1)+Vd/R3+Vd/R4+(Vd-Vt)/R5);
It=(Vt-Vd)/R5;
Rth3=Vt/It;
%Display results
V1=vpa(V1,7)
V2=vpa(V2,7)
V3=vpa(V3,7)
Va=vpa(Va,7)
Vb=vpa(Vb,7)
Vc=vpa(Vc,7)
Isc=vpa(Isc,7)
Vd=vpa(Vd,7)
```

continued

Example 4.9 continued


MATLAB continued

```

It=vpa(It,7)
Vth=vpa(Vth,10)
Rth2=vpa(Rth3,10)
Rth1=vpa(Rth1,10)
Rth3=vpa(Rth3,10)

Answers:
V1 =
7.333333
V2 =
2.0
V3 =
6.0
Va =
6.533333
Vb =
-0.4
Vc =
3.6
Isc =
0.0012
Vd =
0.4
It =
0.0002
Vth =
6.0
Rth2 =
5000.0
Rth1 =
5000.0
Rth3 =
5000.0

```

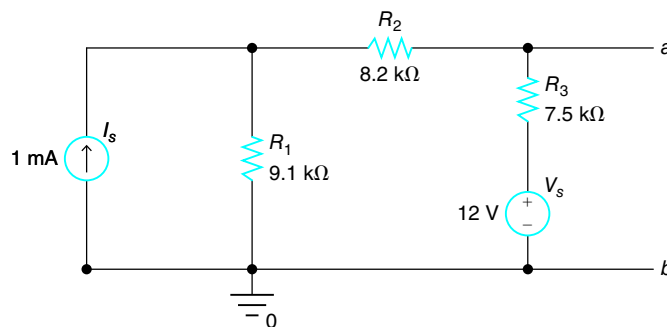**Exercise 4.9**Find the Thévenin equivalent circuit between terminals  $a$  and  $b$  for the circuit shown in Figure 4.78.**FIGURE 4.78**Circuit for  
EXERCISE 4.9.**Answer:**


$$V_{th} = 11.1230 \text{ V}, R_{th} = 5.2319 \text{ k}\Omega.$$

### EXAMPLE 4.10

Find the Thévenin equivalent circuit between terminals  $a$  and  $b$  for the circuit shown in Figure 4.79.

**FIGURE 4.79**

Circuit with a CCCS.

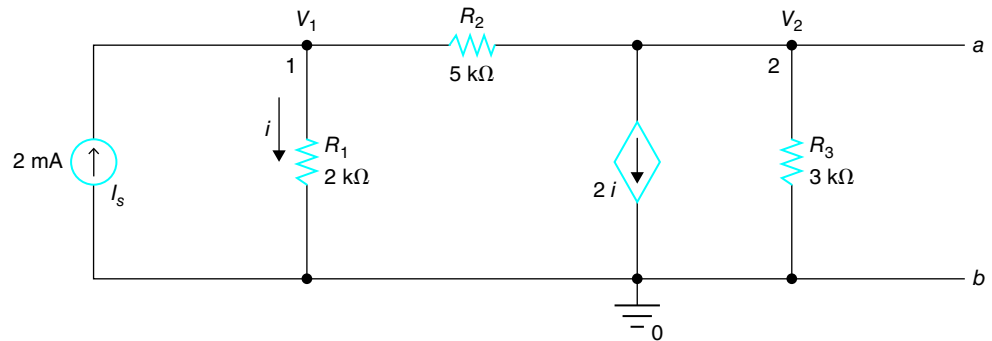

Notice that the open-circuit voltage between terminals  $a$  and  $b$  is the voltage across  $R_3$ , which is labeled  $V_2$  in the circuit shown in Figure 4.79. Summing the currents away from node 1, we obtain

$$-0.002 + \frac{V_1}{2000} + \frac{V_1 - V_2}{5000} = 0$$

Multiplication of this equation by 10,000 yields

$$-20 + 5V_1 + 2(V_1 - V_2) = 0$$

which can be simplified to

$$7V_1 - 2V_2 = 20 \quad (4.39)$$

Summing the currents away from node 2, we obtain

$$\frac{V_2 - V_1}{5000} + 2\frac{V_1}{2000} + \frac{V_2}{3000} = 0$$

Multiplication by 30,000 yields

$$6V_2 - 6V_1 + 30V_1 + 10V_2 = 0$$

which can be simplified to

$$24V_1 + 16V_2 = 0 \quad (4.40)$$

Solving Equation (4.40) for  $V_1$ , we have

$$V_1 = -\frac{2}{3}V_2$$

Substituting this into Equation (4.39), we obtain

$$7V_1 - 2V_2 = 7\left(-\frac{2}{3}V_2\right) - 2V_2 = -\frac{20}{3}V_2 = 20$$

*continued*

Example 4.10 continued


Thus,  $V_2 = V_{oc} = -3$  V. The Thévenin equivalent voltage is the open-circuit voltage between  $a$  and  $b$ , which is  $V_2$ . Therefore,

$$V_{th} = V_{oc} = -3 \text{ V}$$

To find the Thévenin equivalent resistance, we first use method 2. The terminals  $a$  and  $b$  are short-circuited without changing the rest of the circuit, as shown in Figure 4.80.

**FIGURE 4.80**

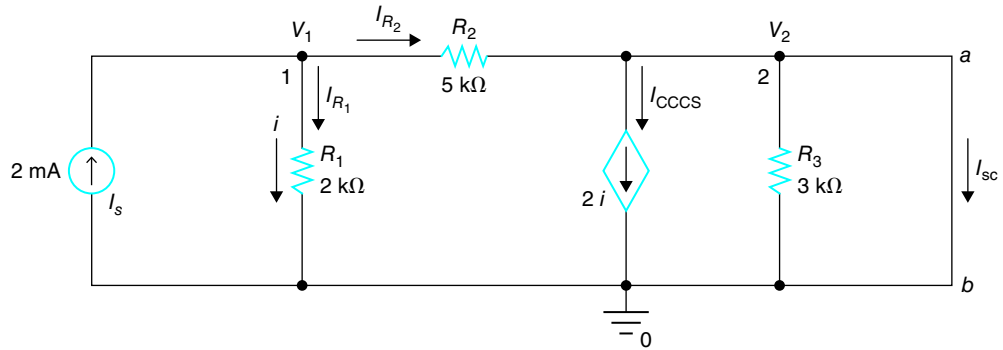A circuit with terminals  $a$  and  $b$  short-circuited.



Notice that node 2 is connected to ground and no current flows through  $R_3$ . From the current divider rule, the current through  $R_1$  is given by

$$I_{R_1} = i = I_s \times \frac{R_2}{R_1 + R_2} = 2 \text{ mA} \times \frac{5 \text{ k}\Omega}{2 \text{ k}\Omega + 5 \text{ k}\Omega} = \frac{10}{7} \text{ mA}$$

Similarly, the current through  $R_2$  is given by

$$I_{R_2} = I_s \times \frac{R_1}{R_1 + R_2} = 2 \text{ mA} \times \frac{2 \text{ k}\Omega}{2 \text{ k}\Omega + 5 \text{ k}\Omega} = \frac{4}{7} \text{ mA}$$

The current through a current-controlled current source (CCCS) is given by

$$I_{CCCS} = 2i = 2I_{R_1} = \frac{20}{7} \text{ mA}$$

Applying KCL at node 2, we obtain

$$I_{R_2} = I_{CCCS} + I_{sc}$$

Solving for  $I_{sc}$ , we have

$$I_{sc} = I_{R_2} - I_{CCCS} = \frac{4}{7} \text{ mA} - \frac{20}{7} \text{ mA} = -\frac{16}{7} \text{ mA} = -2.2857 \text{ mA}$$

The Thévenin equivalent resistance is the ratio of the open-circuit voltage to the short-circuit current. Thus, we have

$$R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{-3 \text{ V}}{-\frac{16}{7} \text{ mA}} = \frac{21}{16} \text{ k}\Omega = 1.3125 \text{ k}\Omega$$


continued

Example 4.10 continued

The Thévenin equivalent resistance can also be found using method 3. After deactivating the current source by removing it from the circuit, a test voltage is applied to the circuit from terminals  $a$  and  $b$ , as shown in Figure 4.81.

**FIGURE 4.81**

A circuit with a test voltage source.

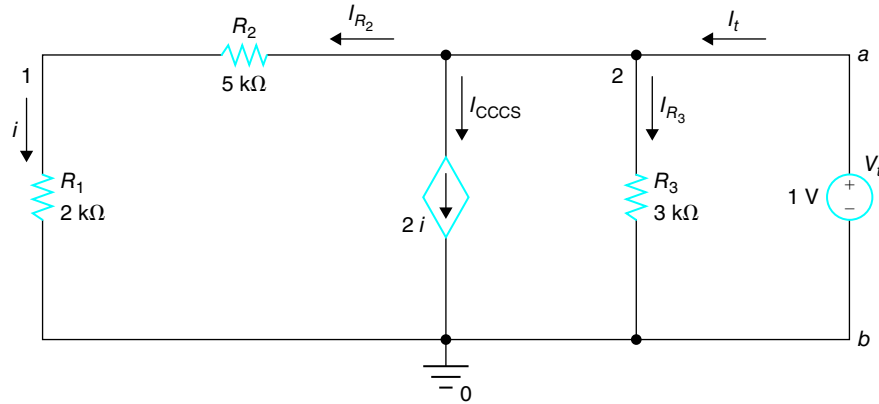

The test voltage  $V_t$  is applied across  $R_3$  and  $R_2 - R_1$ . The current through  $R_2 - R_1$ , which is also the controlling current, is given by

$$I_{R_2} = i = \frac{V_t}{R_2 + R_1} = \frac{1 \text{ V}}{7 \text{ k}\Omega} = \frac{1}{7} \text{ mA}$$

The current through  $R_3$  is given by

$$I_{R_3} = \frac{V_t}{R_3} = \frac{1 \text{ V}}{3 \text{ k}\Omega} = \frac{1}{3} \text{ mA}$$

The current through CCCS is twice the controlling current  $i$ . Thus,

$$I_{CCCS} = 2i = 2I_{R_2} = \frac{2}{7} \text{ mA}$$

The total current flowing out of the positive terminal of the test voltage source is given by

$$I_t = I_{R_2} + I_{CCCS} + I_{R_3} = \frac{1}{7} \text{ mA} + \frac{2}{7} \text{ mA} + \frac{1}{3} \text{ mA} = \frac{16}{21} \text{ mA} = 0.7619 \text{ mA}$$

The Thévenin equivalent resistance is the ratio of  $V_t$  to  $I_t$ :

$$R_{th} = \frac{V_t}{I_t} = \frac{1 \text{ V}}{\frac{16}{21} \text{ mA}} = \frac{21}{16} \text{ k}\Omega = 1.3125 \text{ k}\Omega$$

After deactivating the current source, instead of a test voltage source, a test current source can be applied to the circuit from terminals  $a$  and  $b$ , as shown in Figure 4.82.

Summing the currents leaving node 2, we obtain

$$\frac{V_t}{7000} + \frac{2V_t}{7000} + \frac{V_t}{3000} - 0.001 = 0$$

Multiplication by 21,000 yields

$$3V_t + 6V_t + 7V_t = 21$$

continued



Example 4.10 continued

FIGURE 4.82

A circuit with a test current source.

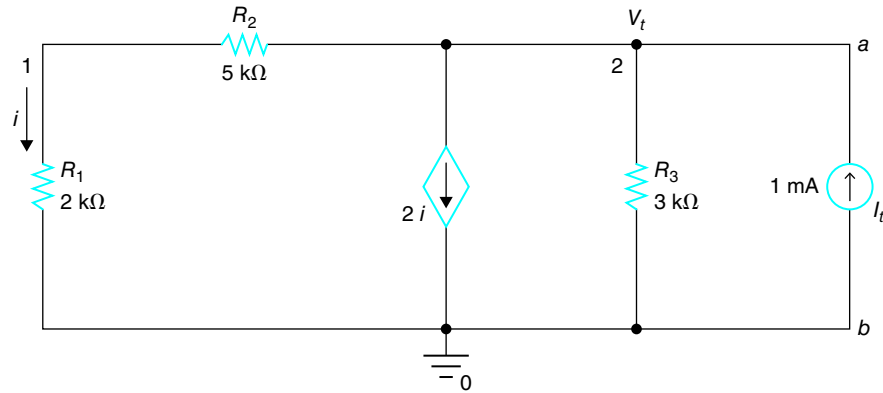
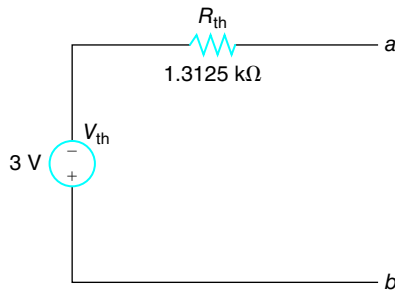


FIGURE 4.83

The Thévenin equivalent circuit.

Solving for  $V_t$ , we obtain

$$V_t = \frac{21}{16} \text{ V} = 1.3125 \text{ V}$$

The Thévenin equivalent resistance is the ratio of  $V_t$  to  $I_t$ :

$$R_{th} = \frac{V_t}{I_t} = \frac{\frac{21}{16} \text{ V}}{1 \text{ mA}} = \frac{21}{16} \text{ k}\Omega = 1.3125 \text{ k}\Omega$$

The Thévenin equivalent circuit is shown in Figure 4.83.

## MATLAB

```
%EXAMPLE 4.10
clear all;
Is=2e-3;R1=2000;R2=5000;R3=3000;ki=2;Vta=1;Itb=1e-3;
syms V1 V2 Va Vtb
%Voc = Vth
[V1,V2]=solve(-Is+V1/R1+(V1-V2)/R2,(V2-V1)/R2+ki*V1/R1+V2/R3);
Vth=V2;
%Method 2: Rth2 = Voc/Isc
Va=solve(-Is+Va/R1+Va/R2);
Isc=Va/R2-ki*Va/R1;
Rth2=Vth/Isc;
%Method 3: Rth3a = Vta/Ita (test voltage)
IR2=Vta/(R2+R1);
Icccs=ki*IR2;
IR3=Vta/R3;
Ita=IR2+Icccs+IR3;
Rth3a=Vta/Ita;
Rth3a=vpa(Rth3a,10);
%Method 3: Rth3b = Vtb/Itb (test current)
Vtb=solve(Vtb/(R2+R1)+ki*Vtb/(R2+R1)+Vtb/R3-Itb);
Rth3b=Vtb/Itb;
Rth3b=vpa(Rth3b,10);
%Display results
V1=vpa(V1,7)
V2=vpa(V2,7)
Va=vpa(Va,7)
```

continued

Example 4.10 continued

MATLAB continued

```

Isc=vpa(Isc,7)
Ita=vpa(Ita,7)
Vtb=vpa(Vtb,7)
Vth=vpa(Vth,10)
Rth2=vpa(Rth2,10)
Rth3a=vpa(Rth3a,10)
Rth3b=vpa(Rth3b,10)


```

Answers:

```

V1 =
2.0
V2 =
-3.0
Va =
2.857143
Isc =
-0.002285714
Ita =
0.0007619048
Vtb =
1.3125
Vth =
-3.0
Rth2 =
1312.5
Rth3a =
1312.5
Rth3b =
1312.5

```

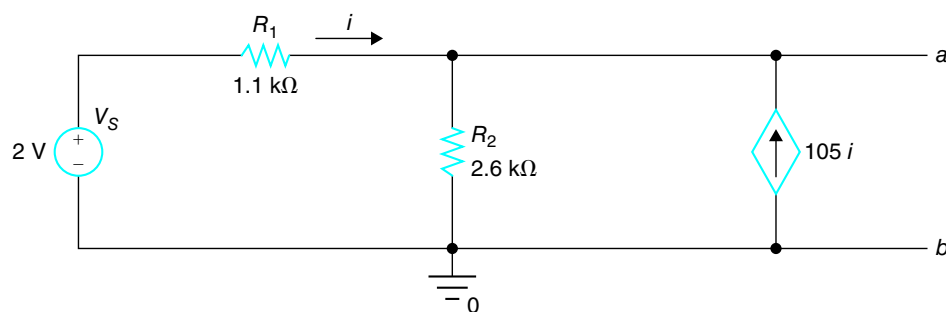**Exercise 4.10**Find the Thévenin equivalent circuit between terminals  $a$  and  $b$  for the circuit shown in Figure 4.84.**FIGURE 4.84**Circuit for  
EXERCISE 4.10.**Answer:**


$$V_{th} = 1.9920 \text{ V}, R_{th} = 10.3361 \text{ } \Omega.$$

## EXAMPLE 4.11

Find the Thévenin equivalent circuit between terminals  $a$  and  $b$  for the circuit shown in Figure 4.85.

FIGURE 4.85

Circuit for  
EXAMPLE 4.11.

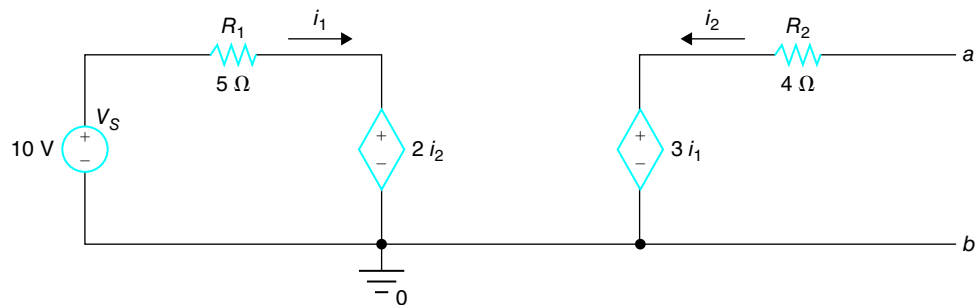

Since current  $i_2$  equals zero, the voltage across the CCVS on the left side of the circuit is zero. Current  $i_1$  is given by

$$i_1 = \frac{V_s}{R_1} = \frac{10 \text{ V}}{5 \Omega} = 2 \text{ A}$$


The Thévenin voltage is the voltage across the CCVS on the right side of the circuit. Thus,

$$V_{\text{th}} = 3i_1 = 3 \times 2 \text{ V} = 6 \text{ V}$$

To find the Thévenin resistance, we deactivate the voltage source by short-circuiting it, and then apply a test voltage  $V_t$  of 1 V across  $a$  and  $b$ , as shown in Figure 4.86.

FIGURE 4.86

A circuit with a  
test voltage.

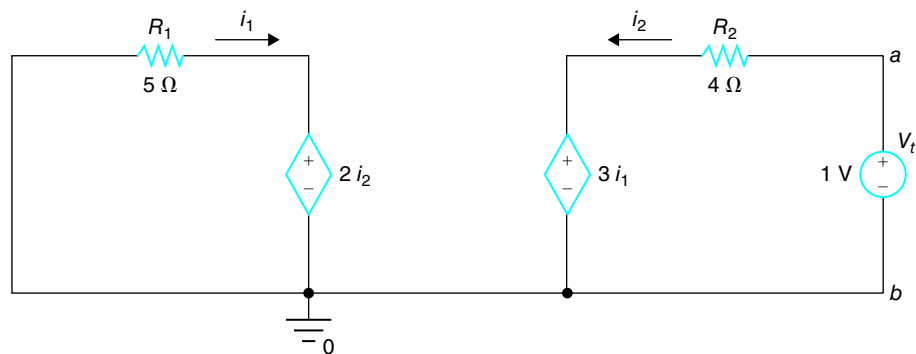

Collecting the voltage drops around the mesh on the left side in the clockwise direction, we obtain

$$5i_1 + 2i_2 = 0$$

Solving for  $i_1$ , we get

$$i_1 = \frac{-2i_2}{5} = -0.4i_2 \quad (4.41)$$

continued

Example 4.11 continued

Collecting the voltage drops around the mesh on the right side in the clockwise direction, we obtain

$$-3i_1 - 4i_2 + 1 = 0 \quad (4.42)$$

Substitution of Equation (4.41) into Equation (4.42) yields

$$1.2i_2 - 4i_2 + 1 = 0$$

Solving for  $i_2$ , we get

$$i_2 = \frac{1}{2.8} \text{ A} = 0.3571 \text{ A}$$


The Thévenin equivalent resistance is given by

$$R_{\text{th}} = \frac{V_t}{i_2} = \frac{1 \text{ V}}{\frac{1}{2.8} \text{ A}} = 2.8 \Omega$$

The Thévenin equivalent circuit is shown in Figure 4.87.

FIGURE 4.87

The Thévenin equivalent circuit.

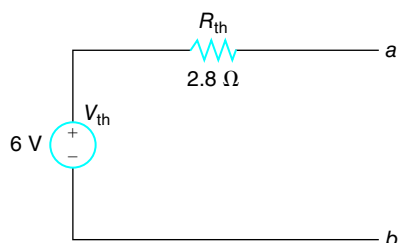


### Exercise 4.11

Find the Thévenin equivalent circuit between terminals  $a$  and  $b$  for the circuit shown in Figure 4.88.

FIGURE 4.88

Circuit for EXERCISE 4.11.

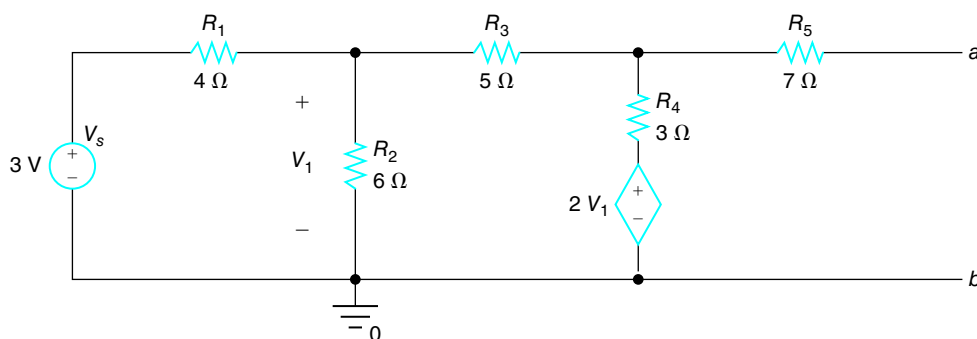

**Answer:**


$$V_{\text{th}} = 4.1786 \text{ V}, R_{\text{th}} = 10.9643 \Omega.$$

### EXAMPLE 4.12

Find the Thévenin equivalent circuit between terminals  $a$  and  $b$  for the circuit shown in Figure 4.89.

*continued*

Example 4.12 continued

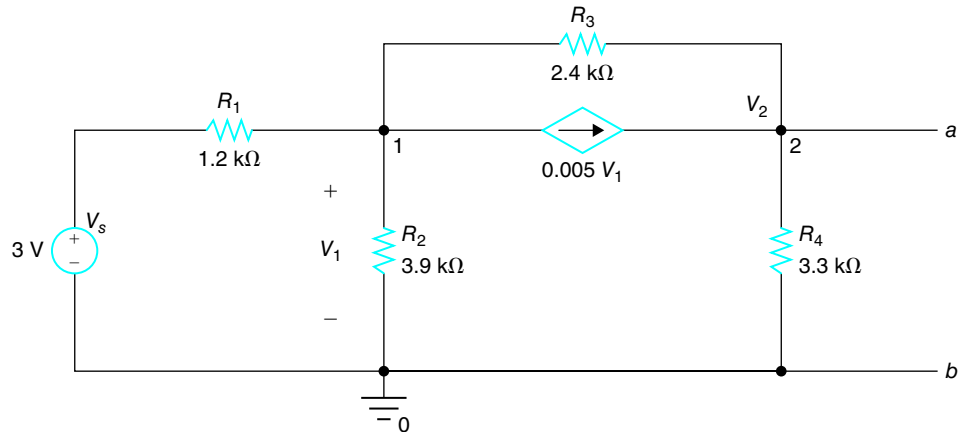**FIGURE 4.89**Circuit for  
EXAMPLE 4.12.

The Thévenin equivalent circuit between terminals  $a$  and  $b$  can be found by finding the open-circuit voltage  $V_{oc}$  and the short-circuit current  $I_{sc}$ . The open-circuit voltage  $V_{oc}$  is  $V_2$ , which is the voltage across  $R_4$  in the circuit shown in Figure 4.89. Summing the currents leaving node 1, we obtain

$$\frac{V_1 - V_s}{R_1} + \frac{V_1}{R_2} + \frac{V_1 - V_2}{R_3} + g_m V_1 = 0 \quad (4.43)$$

which can be rearranged as

$$\left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + g_m \right) V_1 - \frac{1}{R_3} V_2 = \frac{V_s}{R_1}$$

Substituting the component values, we get

$$\left( \frac{1}{1200} + \frac{1}{3900} + \frac{1}{2400} + 0.005 \right) V_1 - \frac{1}{2400} V_2 = \frac{3}{1200}$$

which can be simplified to

$$6.50641 \times 10^{-3} V_1 - 4.16667 \times 10^{-4} V_2 = 2.5 \times 10^{-3}$$

Multiplication by 1000 yields

$$6.50641 V_1 - 0.416667 V_2 = 2.5 \quad (4.44)$$

Summing the currents leaving node 2, we obtain

$$\frac{V_2 - V_1}{R_3} - g_m V_1 + \frac{V_2}{R_4} = 0 \quad (4.45)$$

which can be revised as

$$-\left( \frac{1}{R_3} + g_m \right) V_1 + \left( \frac{1}{R_3} + \frac{1}{R_4} \right) V_2 = 0$$

Substituting the component values, we get

$$-\left( \frac{1}{2400} + 0.005 \right) V_1 + \left( \frac{1}{2400} + \frac{1}{3300} \right) V_2 = 0$$

continued

Example 4.12 continued

which can be simplified to

$$-5.416667 \times 10^{-3}V_1 + 7.19697 \times 10^{-4}V_2 = 0$$

Multiplication by 1000 yields

$$-5.416667V_1 + 0.719697V_2 = 0 \quad (4.46)$$

Solving Equation (4.46) for  $V_2$ , we obtain

$$V_2 = \frac{5.416667}{0.719697}V_1 = 7.526317V_1$$

Substituting  $V_2$  into Equation (4.44), we get

$$6.50641V_1 - 0.416667(7.526317V_1) = 2.5$$

Thus,


$$V_1 = \frac{2.5}{6.50641 - 0.416667 \times 7.526317} = 0.74174 \text{ V}$$

$$V_2 = 7.526317V_1 = 5.5826 \text{ V}$$

Alternatively, application of Cramer's rule to Equations (4.44) and (4.46) yields

$$V_1 = \frac{\begin{vmatrix} 2.5 & -0.416667 \\ 0 & 0.719697 \end{vmatrix}}{\begin{vmatrix} 6.50641 & -0.416667 \\ -5.416667 & 0.719697 \end{vmatrix}} = \frac{1.7992}{2.4257} = 0.74174 \text{ V}$$

$$V_2 = \frac{\begin{vmatrix} 6.50641 & 2.5 \\ -5.416667 & 0 \end{vmatrix}}{\begin{vmatrix} 6.50641 & -0.416667 \\ -5.416667 & 0.719697 \end{vmatrix}} = \frac{13.541667}{2.4257} = 5.5826 \text{ V}$$

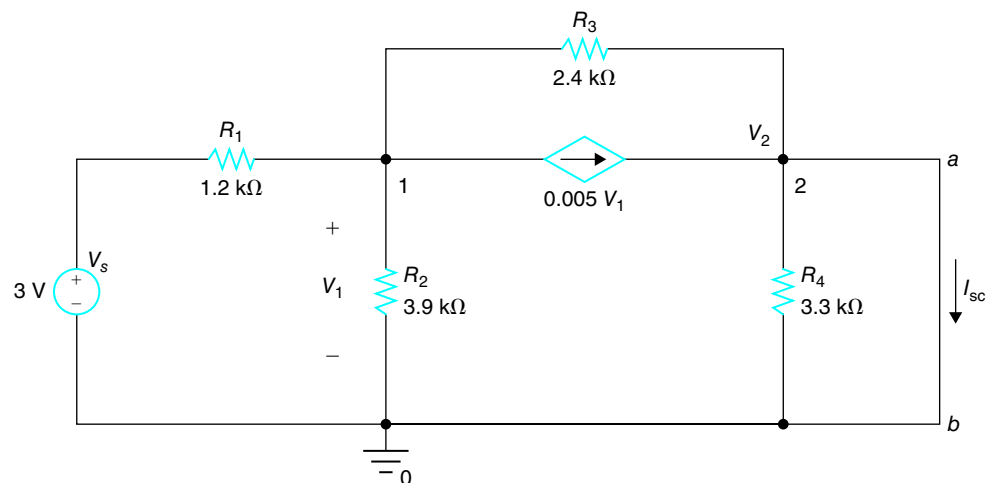To find the short-circuit current, we short-circuit  $a$  and  $b$ , as shown in Figure 4.90.**FIGURE 4.90**The circuit from Figure 4.89 with  $a$  and  $b$  short-circuited.

continued

Example 4.12 continued

Notice that node 2 is connected to ground and no current flows through  $R_4$ . Summing the currents leaving node 1 of the circuit shown in Figure 4.90, we obtain

$$\frac{V_1 - V_s}{R_1} + \frac{V_1}{R_2} + \frac{V_1}{R_3} + g_m V_1 = 0$$

which can be rearranged as

$$\left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + g_m \right) V_1 = \frac{V_s}{R_1}$$

Thus, we obtain

$$V_1 = \frac{\frac{V_s}{R_1}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + g_m} = \frac{\frac{3}{1200}}{\frac{1}{1200} + \frac{1}{3900} + \frac{1}{2400} + 0.005} = 0.38423645 \text{ V}$$

The short-circuit current is given by

$$\begin{aligned} I_{sc} &= \frac{V_1}{R_3} + g_m V_1 = V_1 \left( \frac{1}{R_3} + g_m \right) \\ &= 0.38423645 \left( \frac{1}{2400} + 0.005 \right) = 2.0813 \text{ mA} \end{aligned}$$


The Thévenin equivalent resistance is given by

$$R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{5.5826 \text{ V}}{2.6823 \text{ mA}} = 2.6823 \text{ k}\Omega$$

The Thévenin equivalent circuit is shown in Figure 4.91.

FIGURE 4.91

The Thévenin equivalent circuit.

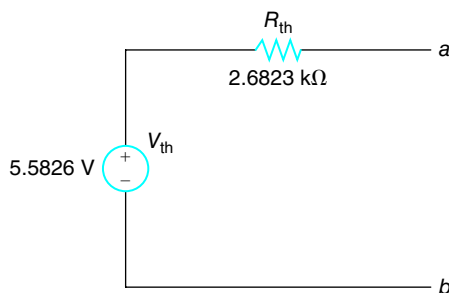

## MATLAB

```
%EXAMPLE 4.12
clear all;
Vs=3;R1=1200;R2=3900;R3=2400;R4=3300;gm=0.005;
syms V1 V2 Va Vb
%Voc = Vth
[V1,V2]=solve((V1-Vs)/R1+V1/R2+(V1-V2)/R3+gm*V1,...
(V2-V1)/R3-gm*V1+V2/R4,V1,V2);
Vth=V2;
%Method 2: Rth = Voc/Isc
Va=solve((Va-Vs)/R1+Va/R2+(Va-0)/R3+gm*Va,Va);
Isc=Va/R3+gm*Va;
Rth=Vth/Isc;
%Display results
V1=vpa(V1,8)
V2=vpa(V2,8)
Va=vpa(Va,8)
Isc=vpa(Isc,8)
Vth=vpa(Vth,8)
Rth=vpa(Rth,8)

Answers:
V1 =
0.74174174
```

continued

Example 4.12 continued  
MATLAB continued


```
V2 =
5.5825826
Va =
0.38423645
Isc =
0.0020812808
Vth =
5.5825826
Rth =
2682.2823
```

### Exercise 4.12

Find the Thévenin equivalent circuit between terminals  $a$  and  $b$  for the circuit shown in Figure 4.92.

FIGURE 4.92

Circuit for  
EXERCISE 4.12.

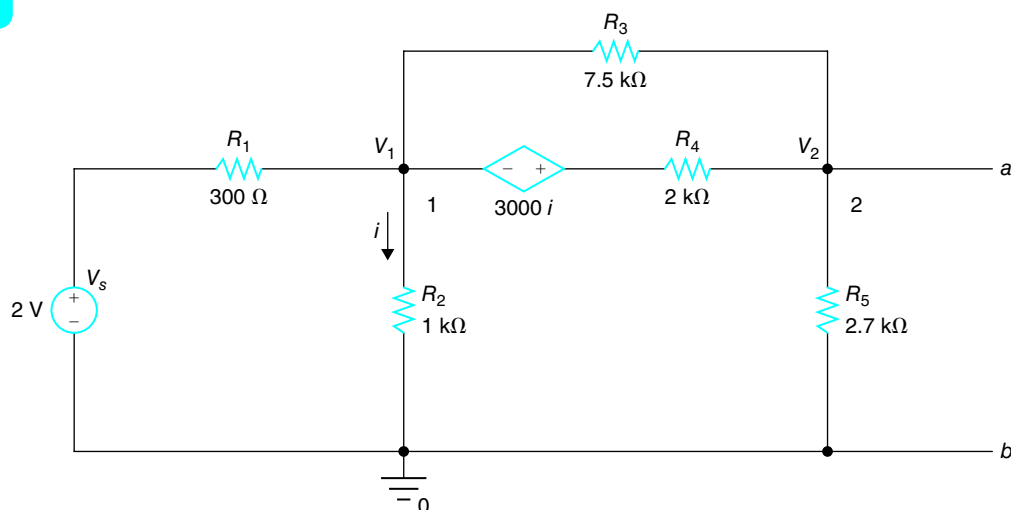


**Answer:**

$V_{th} = 2.7672 \text{ V}$ ,  $R_{th} = 1.2582 \text{ k}\Omega$ .

## 4.5 Norton's Theorem

FIGURE 4.93

A Norton equivalent circuit.

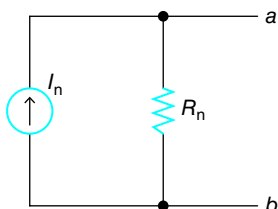

A circuit looking from terminals  $a$  and  $b$  can be replaced by a current source with current  $I_n$  and a parallel resistor with resistance  $R_n$ , as shown in Figure 4.93. This equivalent circuit consisting of a current source and a parallel resistor is called **Norton equivalent circuit**. The current  $I_n$  is called **Norton equivalent current** and the resistance  $R_n$  is called **Norton equivalent resistance**.


The Norton equivalent circuit can be used to simplify a circuit. When a load resistor is connected between terminals  $a$  and  $b$ , we can find the effects of the circuit on the load from the Norton equivalent circuit. We do not need all the details of the original circuit to find the voltage, current, and power on the load.

When the terminals  $a$  and  $b$  are short-circuited in the Norton equivalent circuit, as shown in Figure 4.94, the short-circuit current  $I_{sc}$  is equal to  $I_n$  from the current divider rule. Thus, the Norton equivalent current can be obtained by finding the short-circuit current.



FIGURE 4.94

Short-circuit current.

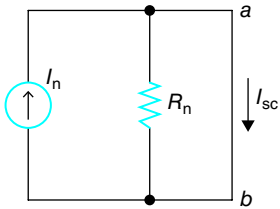

### 4.5.1 FINDING THE NORTON EQUIVALENT CURRENT $I_n$

Given a circuit and terminals  $a$  and  $b$ , we can find the Norton equivalent current  $I_n$  with respect to terminals  $a$  and  $b$  by finding the short-circuit current  $I_{sc}$  between terminals  $a$  and  $b$ . The short-circuit current  $I_{sc}$  can be found by utilizing circuit analysis methods such as the voltage divider rule, current divider rule, superposition principle, nodal analysis, and mesh analysis. The Norton equivalent current  $I_n$  is found from the original circuit by connecting a wire between  $a$  and  $b$  without any changes for the rest of the circuit.

### 4.5.2 FINDING THE NORTON EQUIVALENT RESISTANCE $R_n$

The Norton equivalent resistance can be obtained by applying the three methods used to find the Thévenin equivalent resistance. These three methods are listed next.

#### Method 1

Deactivate all the independent sources by short-circuiting the voltage sources and open-circuiting the current sources. Find the equivalent resistance looking into the circuit from terminals  $a$  and  $b$ . This equivalent resistance is the Norton equivalent resistance  $R_n$ . This method can be used if the circuit does not contain dependent sources.

#### Method 2

Find the open-circuit voltage  $V_{oc}$  and the short-circuit current  $I_{sc}$  between terminals  $a$  and  $b$ . The Norton equivalent resistance  $R_n$  is given by

$$R_n = \frac{V_{oc}}{I_{sc}}$$

#### Method 3


Deactivate all the independent sources by open-circuiting current sources and short-circuiting voltage sources. Apply a test voltage of 1 V (or any other value) between terminals  $a$  and  $b$  with terminal  $a$  connected to the positive terminal of the test voltage. Measure the current flowing out of the positive terminal of the test voltage source. The Norton equivalent resistance  $R_n$  is given by the ratio of the test voltage to the current flowing out of the positive terminal of the test voltage source. A test current can be used instead of a test voltage. Apply a test current between terminals  $a$  and  $b$  after deactivating the independent sources and measure the voltage across  $a$  and  $b$  of the test current source. The Norton equivalent resistance  $R_n$  is the ratio of the voltage across  $a$  and  $b$  to the test current.

### 4.5.3 RELATION BETWEEN THE THÉVENIN EQUIVALENT CIRCUIT AND THE NORTON EQUIVALENT CIRCUIT

Application of source transformation to the Norton equivalent circuit shown in Figure 4.95(a) yields the Thévenin equivalent circuit shown in Figure 4.95(b). Notice that the Thévenin equivalent voltage is  $V_{th} = I_n R_n$  and the Thévenin equivalent resistance is  $R_{th} = R_n$ . The source transformation does not change the resistance value. Application of source transformation to the Thévenin equivalent circuit shown in Figure 4.96(a) yields the Norton equivalent


FIGURE 4.95

Transformation from Norton equivalent circuit to Thévenin equivalent circuit.

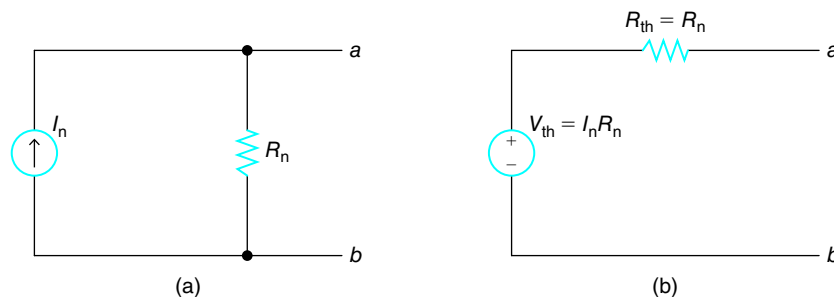

**FIGURE 4.96**

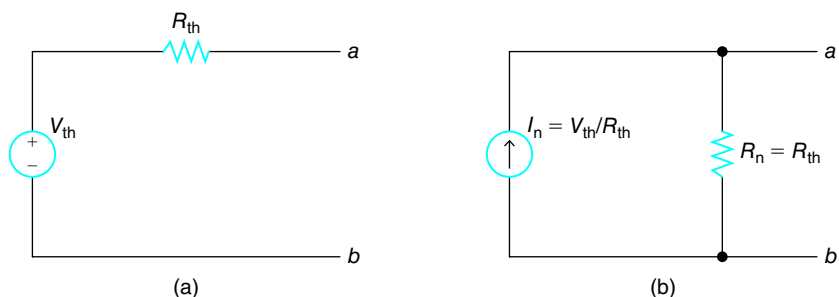Transformation from Thévenin equivalent circuit to Norton equivalent circuit.




circuit, as shown in Figure 4.96(b). Notice that the Norton equivalent current is  $I_n = V_{th}/R_{th}$  and the Norton equivalent resistance is  $R_n = R_{th}$ . The source transformation does not change the resistance value.

Consider the circuit shown in Figure 4.97. We are interested in finding a Norton equivalent circuit looking into the circuit from terminals  $a$  and  $b$ .

**FIGURE 4.97**


A circuit with two sources.

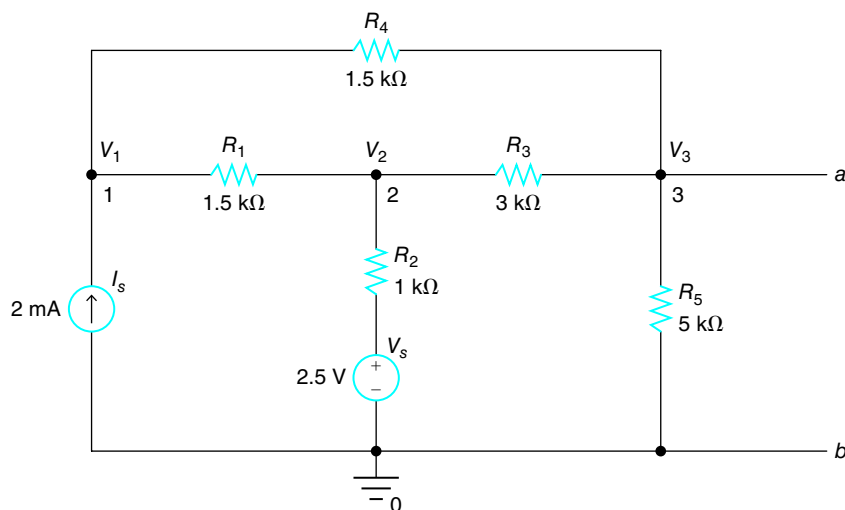

To find the short-circuit current, we short-circuit  $a$  and  $b$ , as shown in Figure 4.98. Node 3 is a ground, and no current flows through  $R_5$ .

**FIGURE 4.98**


A circuit with  $a$  and  $b$  shorted.

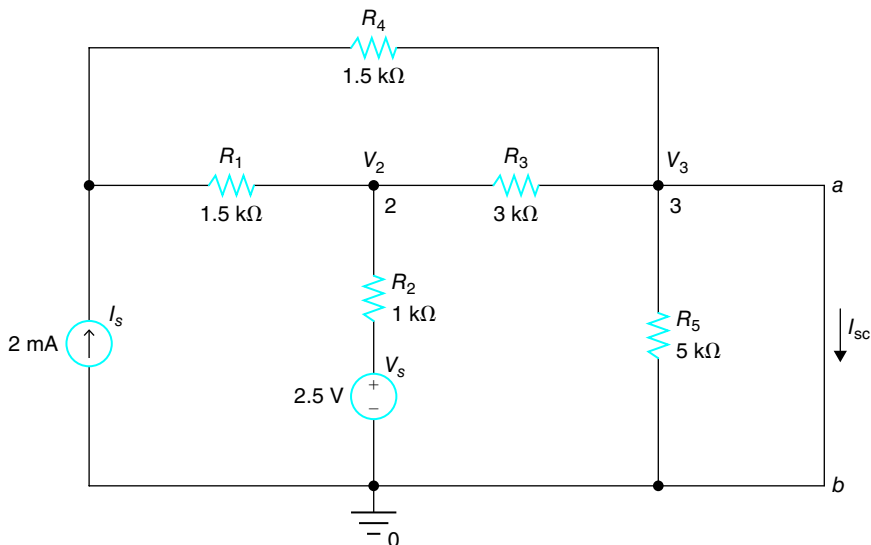

We can find the short-circuit current using the superposition principle. First, we deactivate the voltage source by short-circuiting it, as shown in Figure 4.99.

**FIGURE 4.99**

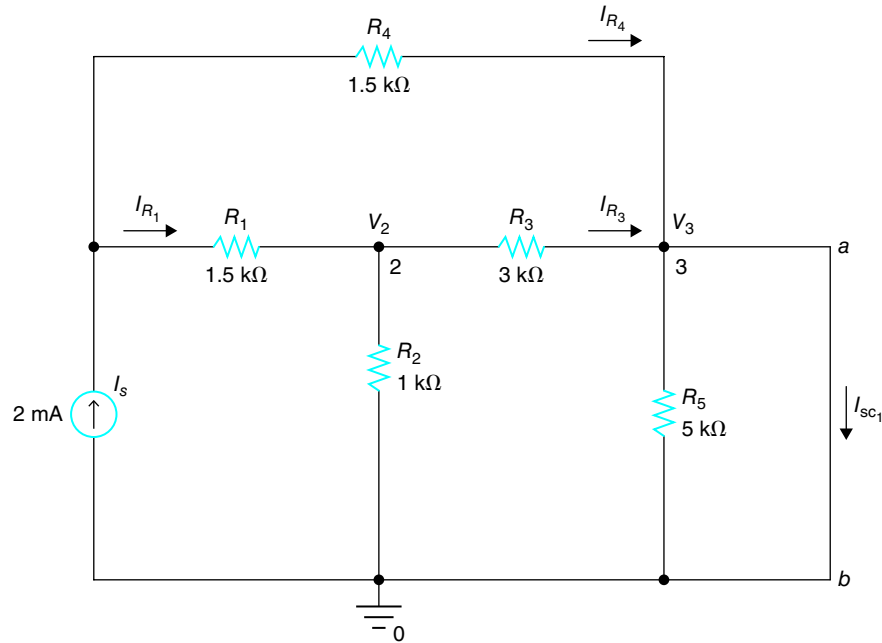A circuit with the voltage source deactivated.



Notice that  $R_2$  and  $R_3$  are connected in parallel. Let  $R_a$  be the equivalent resistance of  $R_1 + (R_2 \parallel R_3)$ . Then, we have

$$R_a = R_1 + (R_2 \parallel R_3) = 1.5 \text{ k}\Omega + (1 \text{ k}\Omega \parallel 3 \text{ k}\Omega) = 1.5 \text{ k}\Omega + 0.75 \text{ k}\Omega = 2.25 \text{ k}\Omega$$

Application of the current divider rule yields

$$I_{R_4} = I_s \times \frac{R_a}{R_a + R_4} = 2 \text{ mA} \times \frac{2.25 \text{ k}\Omega}{2.25 \text{ k}\Omega + 1.5 \text{ k}\Omega} = 1.2 \text{ mA}$$

The current through  $R_1$  is given by

$$I_{R_1} = I_s - I_{R_4} = 2 \text{ mA} - 1.2 \text{ mA} = 0.8 \text{ mA}$$

Application of the current divider rule to  $R_2$  and  $R_3$  yields

$$I_{R_3} = I_{R_1} \times \frac{R_2}{R_2 + R_3} = 0.8 \text{ mA} \times \frac{1 \text{ k}\Omega}{1 \text{ k}\Omega + 3 \text{ k}\Omega} = 0.2 \text{ mA}$$

The short-circuit current is given by

$$I_{sc1} = I_{R_4} + I_{R_3} = 1.2 \text{ mA} + 0.2 \text{ mA} = 1.4 \text{ mA}$$


Now, we deactivate the current source by open-circuiting it, as shown in Figure 4.100.

Let  $R_b$  be the equivalent resistance of parallel connection of  $R_1 + R_4$  and  $R_3$ . Then, we have

$$R_b = (R_1 + R_4) \parallel R_3 = 3 \text{ k}\Omega \parallel 3 \text{ k}\Omega = 1.5 \text{ k}\Omega$$

**FIGURE 4.100**

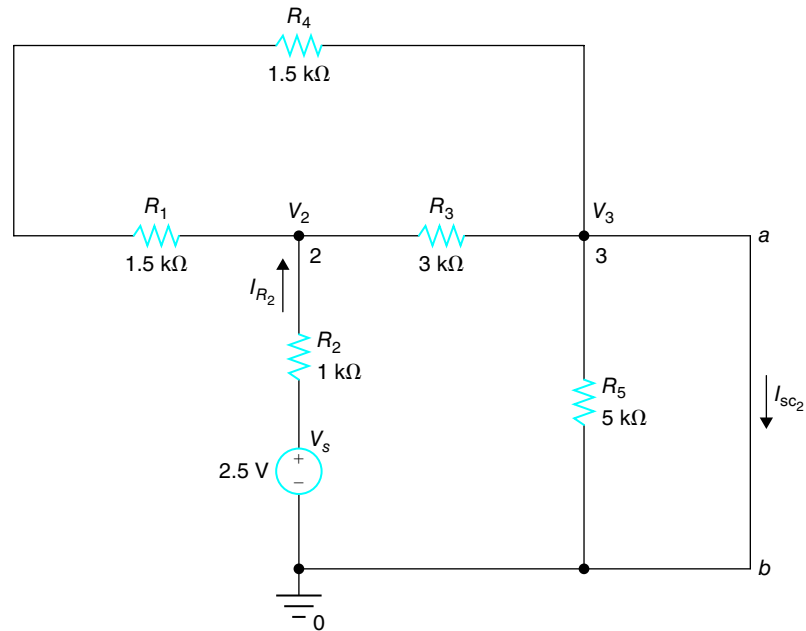Circuit with the current source deactivated.



The total resistance seen from the voltage source is  $R_2 + R_b$ . Thus, the current through  $R_2$ , which is also the short-circuit current, is given by

$$I_{R_2} = I_{sc_2} = \frac{V_s}{R_2 + R_b} = \frac{2.5 \text{ V}}{1 \text{ k}\Omega + 1.5 \text{ k}\Omega} = 1 \text{ mA}$$


The total short-circuit current from the two sources is

$$I_{sc} = I_{sc_1} + I_{sc_2} = 1.4 \text{ mA} + 1 \text{ mA} = 2.4 \text{ mA}$$

To find the Norton equivalent resistance, we deactivate the two sources in the circuit shown in Figure 4.97 to obtain the circuit shown in Figure 4.101.


**FIGURE 4.101**

The circuit from Figure 4.97 with sources deactivated.

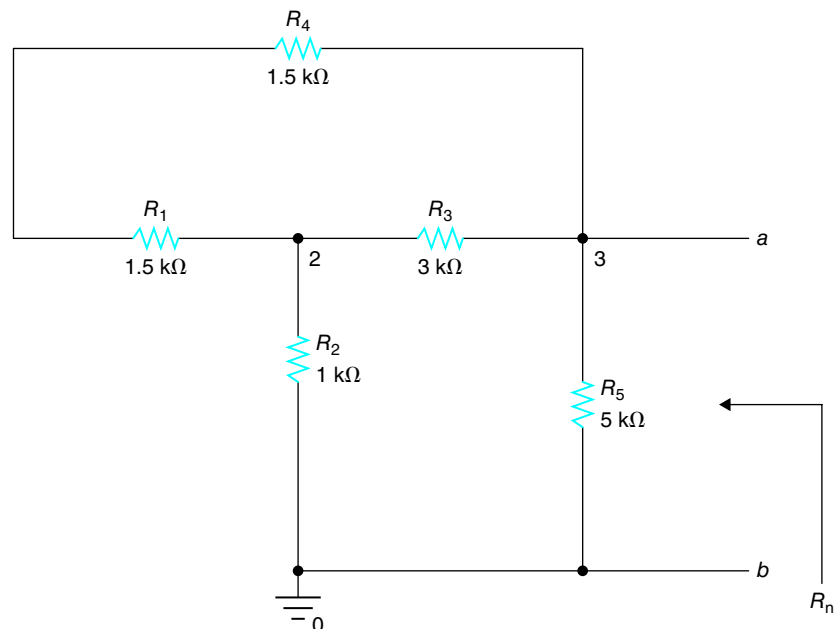

**FIGURE 4.102**

Norton equivalent circuit.

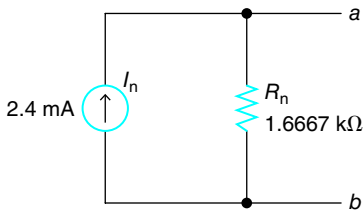

The Norton equivalent resistance is given by the parallel connection of  $R_5$  and  $R_b + R_2$ , where  $R_b = (R_1 + R_4) \parallel R_3 = 1.5 \text{ k}\Omega$ . Thus, we have

$$R_n = R_5 \parallel (R_b + R_2) = 5 \text{ k}\Omega \parallel 2.5 \text{ k}\Omega = 1.6667 \text{ k}\Omega.$$



The Norton equivalent circuit is shown in Figure 4.102.

Consider a circuit with a CCVS shown in Figure 4.103. We are interested in finding the Norton equivalent circuit between terminals  $a$  and  $b$ .

To find the Norton equivalent current, we short-circuit terminals  $a$  and  $b$ , as shown in Figure 4.104. Notice that node 2 is connected to ground, and the current through  $R_4$  is zero.

**FIGURE 4.103**

A circuit with CCVS.

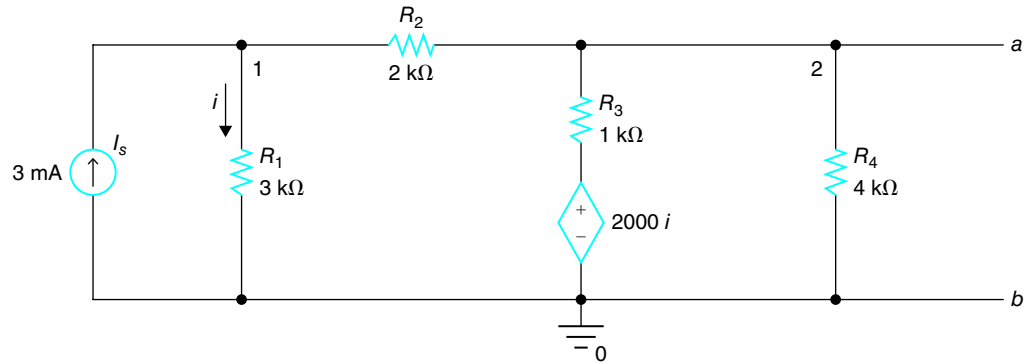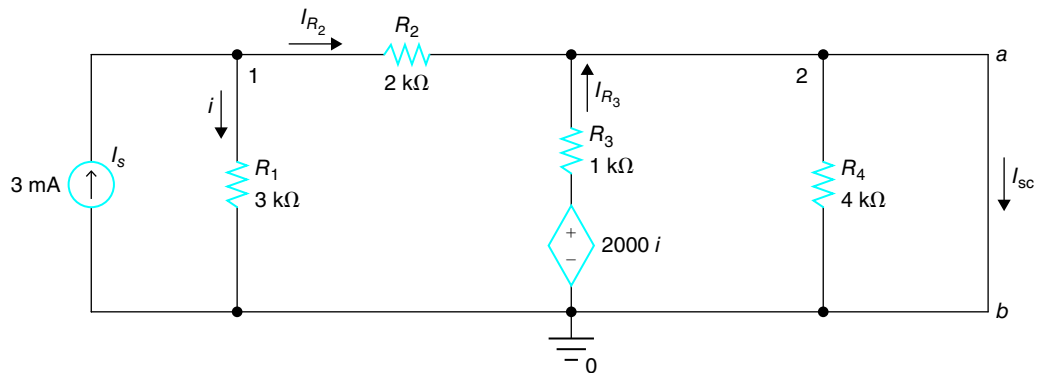**FIGURE 4.104**A circuit with  $a$  and  $b$  short-circuited.

From the current divider rule, the current through  $R_2$  is given by

$$I_{R_2} = I_s \times \frac{R_1}{R_1 + R_2} = 3 \text{ mA} \times \frac{3 \text{ k}\Omega}{3 \text{ k}\Omega + 2 \text{ k}\Omega} = 1.8 \text{ mA}$$

From KCL, the current through  $R_1$  is given by

$$i = I_s - I_{R_2} = 3 \text{ mA} - 1.8 \text{ mA} = 1.2 \text{ mA}$$

The voltage across the CCVS is

$$V_{CCVS} = 2000i = 2000(\text{V/A}) \times 1.2 \text{ mA} = 2.4 \text{ V}$$

The current through  $R_3$  is

$$I_{R_3} = \frac{V_{CCVS}}{R_3} = \frac{2.4 \text{ V}}{1 \text{ k}\Omega} = 2.4 \text{ mA}$$


The short-circuit current is the sum of  $I_{R_2}$  and  $I_{R_3}$ :

$$I_{sc} = I_n = I_{R_2} + I_{R_3} = 1.8 \text{ mA} + 2.4 \text{ mA} = 4.2 \text{ mA}$$

To find the Norton equivalent resistance, after deactivating the current source, we apply a test voltage to the circuit at the terminals  $a$  and  $b$ , as shown in Figure 4.105.

**FIGURE 4.105**

A circuit with a test voltage source.

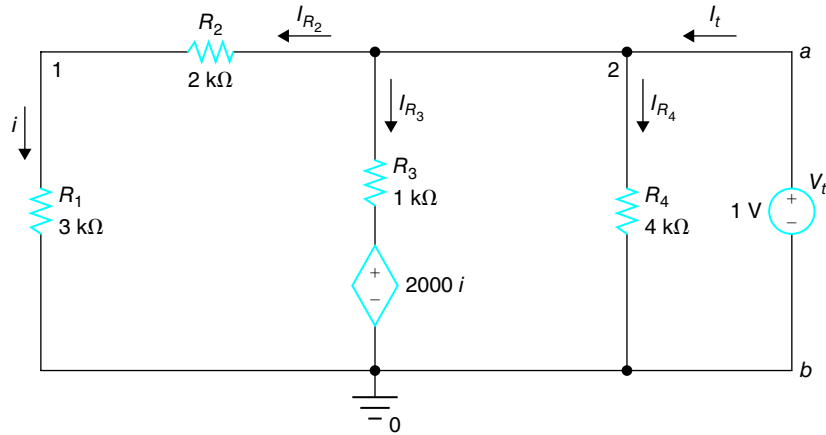

The current through  $R_2$ , which is also the controlling current  $i$ , is given by

$$I_{R_2} = i = \frac{V_t}{R_2 + R_1} = \frac{1 \text{ V}}{2 \text{ k}\Omega + 3 \text{ k}\Omega} = 0.2 \text{ mA}$$

The voltage of the CCVS is given by

$$V_{CCVS} = 2000i = 2000(\text{V/A}) \times 0.2 \text{ mA} = 0.4 \text{ V}$$

The current through  $R_3$  is given by


$$I_{R_3} = \frac{V_t - V_{CCVS}}{R_3} = \frac{1 \text{ V} - 0.4 \text{ V}}{1 \text{ k}\Omega} = 0.6 \text{ mA}$$

The current through  $R_4$  is given by

$$I_{R_4} = \frac{V_t}{R_4} = \frac{1 \text{ V}}{4 \text{ k}\Omega} = 0.25 \text{ mA}$$

**FIGURE 4.106**

Norton equivalent circuit.

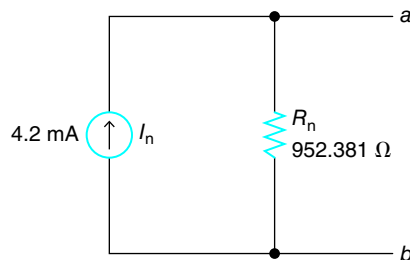

The total current flowing out of the positive terminal of the test voltage source is given by

$$I_t = I_{R_2} + I_{R_3} + I_{R_4} = 0.2 \text{ mA} + 0.6 \text{ mA} + 0.25 \text{ mA} = 1.05 \text{ mA}$$

The Norton equivalent resistance is the ratio of  $V_t$  to  $I_t$ :

$$R_n = \frac{V_t}{I_t} = \frac{1 \text{ V}}{1.05 \text{ mA}} = 952.381 \Omega$$


The Norton equivalent circuit is shown in Figure 4.106.

## EXAMPLE 4.13

Find the Norton equivalent circuit between terminals  $a$  and  $b$  for the circuit shown in Figure 4.107.

FIGURE 4.107


Circuit for  
EXAMPLE 4.13.

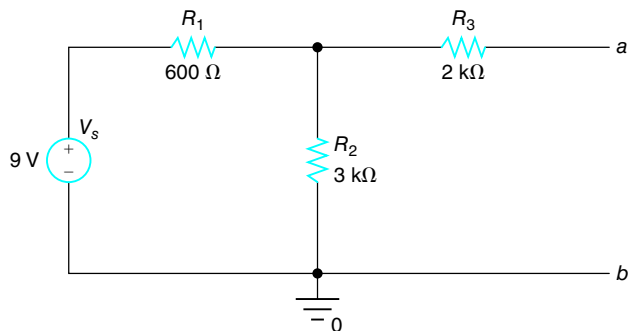

To find the Norton equivalent current,  $a$  and  $b$  are short-circuited, as shown in Figure 4.108.

FIGURE 4.108

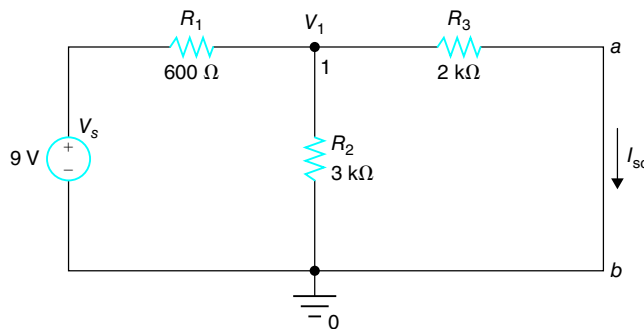Circuit shown in  
Figure 4.107 with  
 $a$  and  $b$  shorted.



Let  $R_a$  be the equivalent resistance of the parallel connection of  $R_2$  and  $R_3$ . Then, we get

$$R_a = R_2 \parallel R_3 = \frac{R_2 \times R_3}{R_2 + R_3} = \frac{3 \text{ k}\Omega \times 2 \text{ k}\Omega}{3 \text{ k}\Omega + 2 \text{ k}\Omega} = \frac{6}{5} \text{ k}\Omega = 1.2 \text{ k}\Omega$$

Application of the voltage divider rule yields

$$V_1 = V_s \times \frac{R_a}{R_1 + R_a} = 9 \text{ V} \times \frac{1.2}{0.6 + 1.2} = 9 \text{ V} \times \frac{1.2}{1.8} = 6 \text{ V}$$

The short-circuit current  $I_{sc}$ , which is the Norton equivalent current, is the current through  $R_3$ . Thus, we have

$$I_n = I_{sc} = \frac{V_1}{R_3} = \frac{6 \text{ V}}{2 \text{ k}\Omega} = 3 \text{ mA}$$

To find the Norton equivalent resistance,  $R_n$ , we deactivate the voltage source by short-circuiting it, as shown in Figure 4.109, and find the equivalent resistance seen from terminals  $a$  and  $b$ . The Norton equivalent resistance is given by


*continued*

Example 4.13 continued

$$\begin{aligned} R_n &= R_3 + (R_1 \parallel R_2) = 2 \text{ k}\Omega + (0.6 \text{ k}\Omega \parallel 3 \text{ k}\Omega) = 2 \text{ k}\Omega + \frac{0.6 \times 3}{0.6 + 3} \text{ k}\Omega \\ &= 2 \text{ k}\Omega + \frac{1.8}{3.6} \text{ k}\Omega = 2.5 \text{ k}\Omega \end{aligned}$$

**FIGURE 4.109**

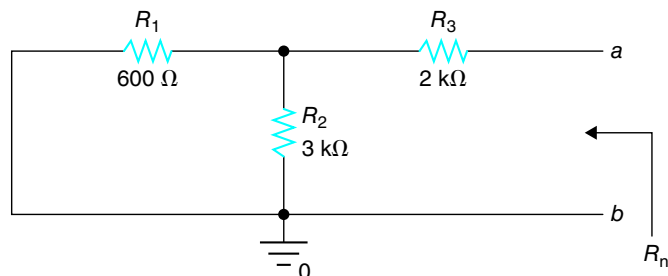
The circuit shown in Figure 4.107 after deactivating the voltage source.



The Norton equivalent circuit is shown in Figure 4.110.

**FIGURE 4.110**

The Norton equivalent circuit.

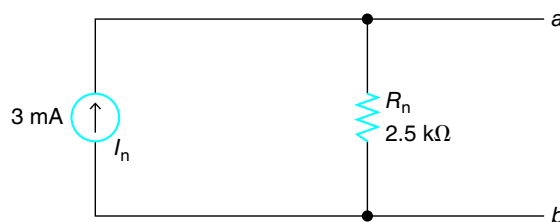


### Exercise 4.13

Find the Norton equivalent current  $I_n$  and the Norton equivalent resistance  $R_n$  between terminals  $a$  and  $b$  for the circuit shown in Figure 4.111.

**FIGURE 4.111**

Circuit for EXERCISE 4.13.

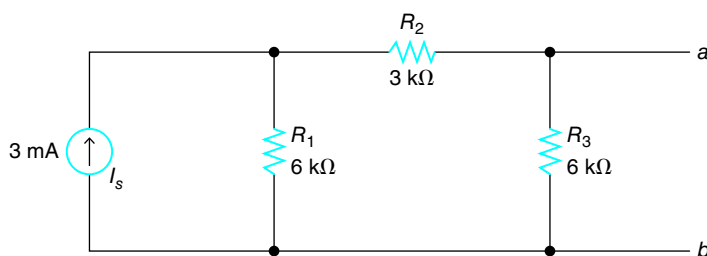

**Answer:**

$$I_n = 2 \text{ mA}, R_n = 3.6 \text{ k}\Omega.$$


### EXAMPLE 4.14

Find the Norton equivalent circuit between terminals  $a$  and  $b$  for the circuit shown in Figure 4.112.


*continued*



Example 4.14 continued

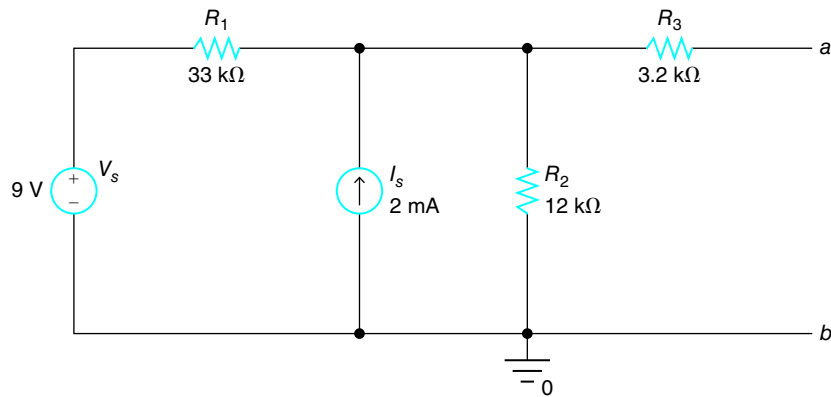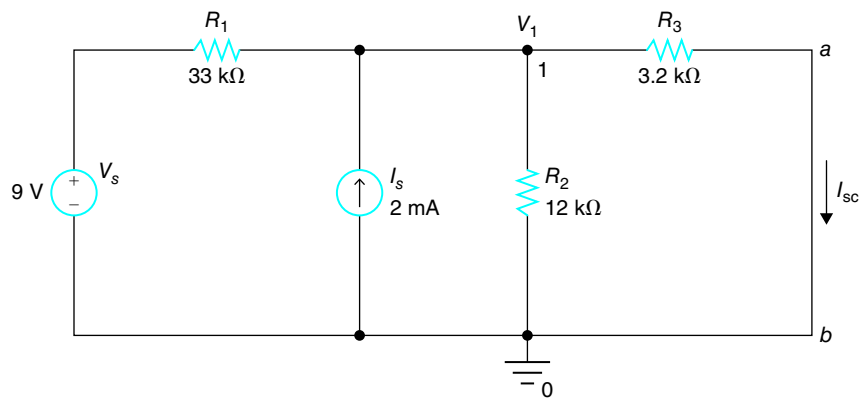**FIGURE 4.112**Circuit for  
EXAMPLE 4.14.

When terminals  $a$  and  $b$  are short-circuited, we obtain the circuit shown in Figure 4.113. The Norton equivalent current  $I_n$  is the short-circuit current  $I_{sc}$ . The short-circuit current  $I_{sc}$  is the current through  $R_3$ . Nodal analysis can be used to find voltage  $V_1$  at node 1.

**FIGURE 4.113**The circuit shown  
in Figure 4.112 with  
terminals  $a$  and  $b$   
short-circuited.

Summing the currents leaving node 1, we obtain

$$\frac{V_1 - 9}{33,000} - 0.002 + \frac{V_1}{12,000} + \frac{V_1}{3200} = 0$$

Multiplication by 33,000 yields

$$V_1 - 9 - 66 + 2.75V_1 + 10.3125V_1 = 0$$

which can be simplified to

$$14.0625V_1 = 75$$

Thus, we have

$$V_1 = \frac{75}{14.0625} = 5.3333 \text{ V}$$

The short-circuit current  $I_{sc}$  is found to be

$$I_n = I_{sc} = \frac{V_1}{R_3} = \frac{5.3333 \text{ V}}{3200 \Omega} = 1.6667 \text{ mA}$$


continued

Example 4.14 continued

To find the Norton equivalent resistance  $R_n$ , we deactivate the voltage source by short-circuiting it and deactivate the current source by open-circuiting it, as shown in Figure 4.114.


**FIGURE 4.114**

The circuit shown in Figure 4.113 with sources deactivated.

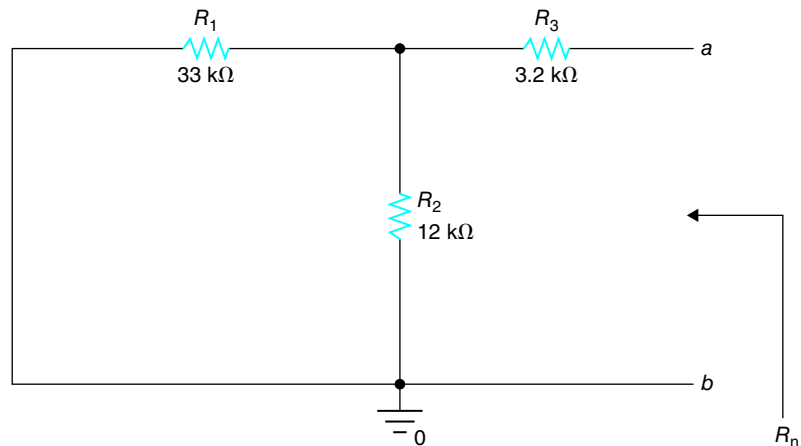

**FIGURE 4.115**

The Norton equivalent circuit.

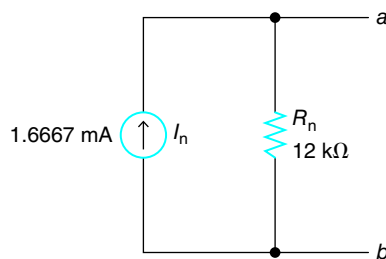

The Norton equivalent resistance  $R_n$  is the equivalent resistance of the circuit shown in Figure 4.114 from terminals  $a$  and  $b$ . Thus, we have

$$\begin{aligned} R_n &= R_3 + (R_1 \parallel R_2) = R_3 + \frac{R_1 \times R_2}{R_1 + R_2} = 3.2 \text{ k}\Omega + \frac{33 \text{ k}\Omega \times 12 \text{ k}\Omega}{33 \text{ k}\Omega + 12 \text{ k}\Omega} \\ &= 3.2 \text{ k}\Omega + \frac{396}{45} \text{ k}\Omega = 12 \text{ k}\Omega \end{aligned}$$


The Norton equivalent circuit is shown in Figure 4.115.

### Exercise 4.14

Find the Norton equivalent circuit between terminals  $a$  and  $b$  for the circuit shown in Figure 4.116.

**FIGURE 4.116**

Circuit for EXERCISE 4.14.

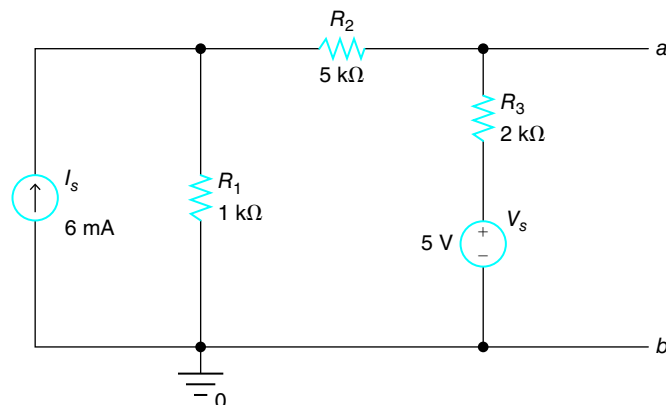

**Answer:**


$$I_n = 3.5 \text{ mA}, R_n = 1.5 \text{ k}\Omega.$$

## EXAMPLE 4.15

Find the Norton equivalent circuit between terminals  $a$  and  $b$  for the circuit shown in Figure 4.117.

FIGURE 4.117

Circuit for  
EXAMPLE 4.15.

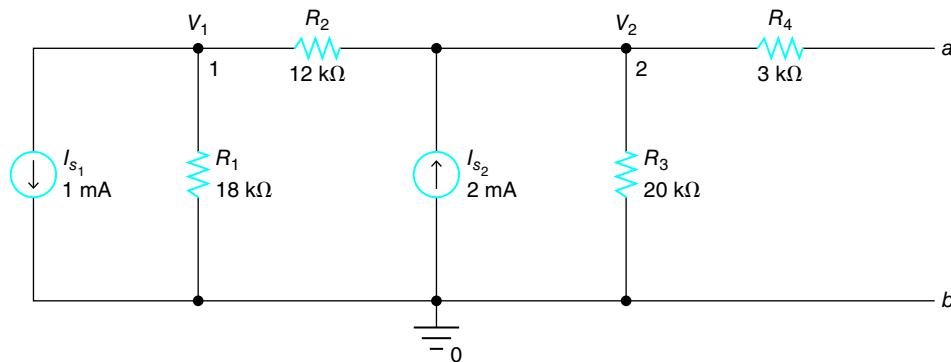

We will find the open-circuit voltage  $V_{oc}$  across  $a$  and  $b$ , and the short-circuit current  $I_{sc}$  through  $a$  and  $b$  to find the Norton equivalent circuit. Since no current flows through  $R_4$ , the open-circuit voltage is voltage  $V_2$  at node 2. Summing the currents leaving node 1, we obtain

$$0.001 + \frac{V_1}{18,000} + \frac{V_1 - V_2}{12,000} = 0$$

Multiplication by 36,000 yields

$$36 + 2V_1 + 3V_1 - 3V_2 = 0$$

which can be simplified to

$$5V_1 - 3V_2 = -36 \quad (4.47)$$

Summing the currents leaving node 2, we obtain

$$\frac{V_2 - V_1}{12,000} - 0.002 + \frac{V_2}{20,000} = 0$$

Multiplication by 60,000 yields

$$5V_2 - 5V_1 - 120 + 3V_2 = 0$$

which can be simplified to

$$-5V_1 + 8V_2 = 120 \quad (4.48)$$

Adding Equations (4.47) and (4.48), we obtain

$$5V_2 = 84$$

Thus, we have

$$V_2 = 16.8 \text{ V}$$

*continued*

Example 4.15 continued


The open-circuit voltage is  $V_2$ . Therefore,

$$V_{oc} = V_2 = 16.8 \text{ V}$$

To find the short-circuit current  $I_{sc}$ ,  $a$  and  $b$  are short-circuited, as shown in Figure 4.118.

**FIGURE 4.118**

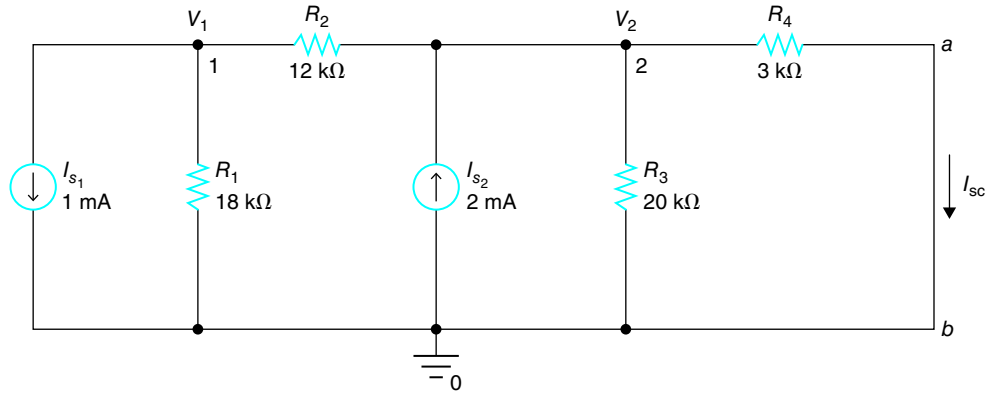Circuit with  $a$  and  $b$  short-circuited.



Equation (4.47) is still valid for the circuit shown in Figure 4.118. Summing the currents leaving node 2, we obtain

$$\frac{V_2 - V_1}{12,000} - 0.002 + \frac{V_2}{20,000} + \frac{V_2}{3000} = 0$$

Multiplication by 60,000 yields

$$5V_2 - 5V_1 - 120 + 3V_2 + 20V_2 = 0,$$

which can be simplified to

$$-5V_1 + 28V_2 = 120 \quad (4.49)$$

Adding Equations (4.47) and (4.49), we obtain

$$25V_2 = 84$$

Thus, we have

$$V_2 = 3.36 \text{ V}$$

The short-circuit current is the current through  $R_4$ . Thus, we have

$$I_{sc} = \frac{V_2}{R_4} = \frac{3.36 \text{ V}}{3 \text{ k}\Omega} = 1.12 \text{ mA}$$


The Norton equivalent resistance is given by

$$R_n = \frac{V_{oc}}{I_{sc}} = \frac{16.8 \text{ V}}{1.12 \text{ mA}} = 15 \text{ k}\Omega$$

The Norton equivalent circuit is shown in Figure 4.119.


**FIGURE 4.119**

The Norton equivalent circuit.

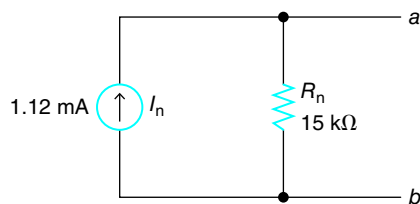

**Exercise 4.15**Find the Norton equivalent circuit between terminals  $a$  and  $b$  for the circuit shown in Figure 4.120.**FIGURE 4.120**


Circuit for EXERCISE 4.15.

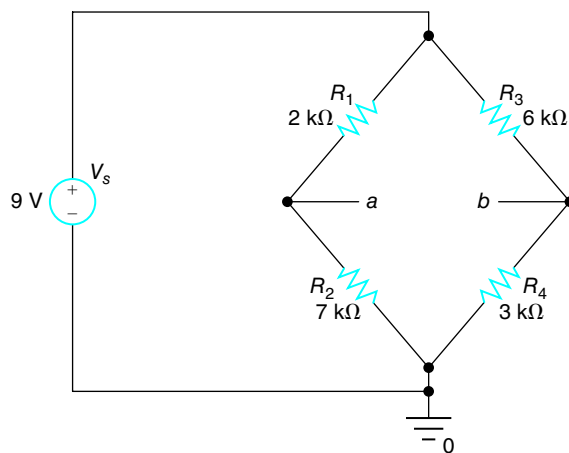**Answer:**

$$I_n = 1.125 \text{ mA}, R_n = 3.5556 \text{ k}\Omega.$$

**EXAMPLE 4.16**Find the Norton equivalent circuit between terminals  $a$  and  $b$  for the circuit shown in Figure 4.121. Assume that  $g_m = 3 \text{ (mA/V)}$ .**FIGURE 4.121**

Circuit for EXAMPLE 4.16.

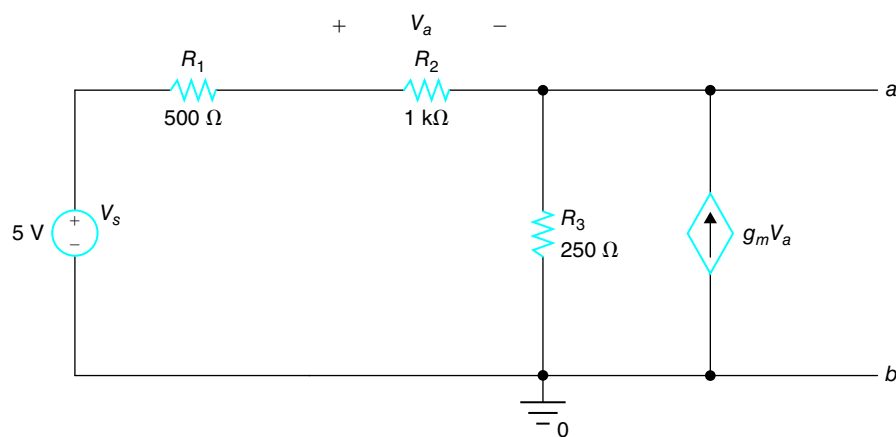

To find the Norton equivalent current, we short-circuit  $a$  and  $b$  in the circuit shown in Figure 4.121 to get the circuit shown in Figure 4.122.

The current  $I$  through  $R_1$  and  $R_2$  is given by


$$I = \frac{5 \text{ V}}{0.5 \text{ k}\Omega + 1 \text{ k}\Omega} = \frac{10}{3} \text{ mA}$$

*continued*

Example 4.16 continued

**FIGURE 4.122**

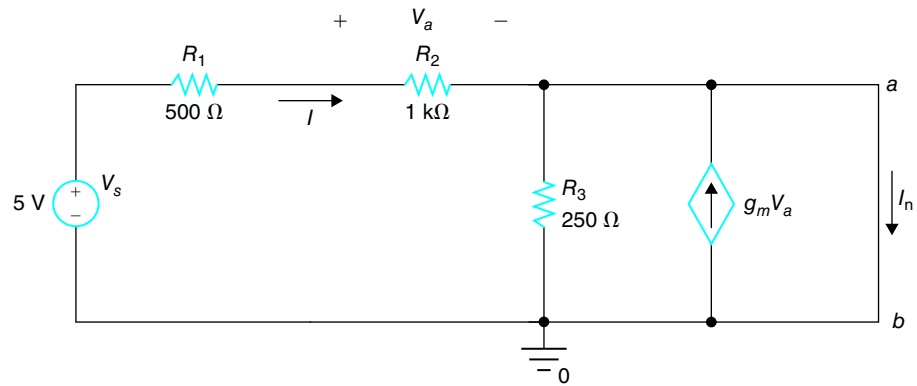The circuit from Figure 4.121 with  $a$  and  $b$  shorted.



The voltage  $V_a$  across  $R_2$  is given by

$$V_a = R_2 I = 1 \text{ k}\Omega \times \frac{10}{3} \text{ mA} = \frac{10}{3} \text{ V}$$

The current from the VCCS is

$$g_m V_a = 3 \left( \frac{\text{mA}}{\text{V}} \right) \times \frac{10}{3} (\text{V}) = \frac{30}{3} \text{ mA} = 10 \text{ mA}$$


According to the current divider rule, all the currents flowing into node  $a$  will flow out through the short circuit. In other words, there is no current through  $R_3$ . Thus, we have

$$I_n = I + g_m V_a = \frac{10}{3} \text{ mA} + \frac{30}{3} \text{ mA} = \frac{40}{3} \text{ mA} = 13.3333 \text{ mA}$$

To find the Norton equivalent resistance, we short-circuit the independent voltage source  $V_s$  and apply a test voltage of 1 V between terminals  $a$  and  $b$ , as shown in Figure 4.123.

**FIGURE 4.123**

Circuit with a test voltage.

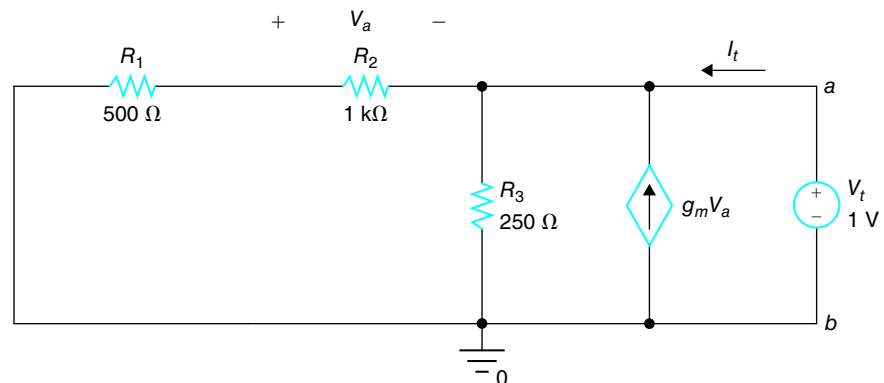

From the voltage divider rule, the voltage  $V_a$  of the circuit shown in Figure 4.123 is given by

$$V_a = -\frac{R_2}{R_2 + R_1} \times V_t = -\frac{1 \text{ k}\Omega}{1 \text{ k}\Omega + 0.5 \text{ k}\Omega} \times 1 = -\frac{2}{3} \text{ V}$$

continued

Example 4.16 continued

The current  $I_t$  flowing out of the test voltage source  $V_t$  is given by

$$I_t = -g_m V_a + \frac{V_t}{R_3} + \frac{V_t}{R_2 + R_1} = (-3 \text{ mA/V}) \times \left(-\frac{2}{3} \text{ V}\right) + \frac{1 \text{ V}}{0.25 \text{ k}\Omega} + \frac{1 \text{ V}}{1.5 \text{ k}\Omega} = \frac{20}{3} \text{ mA}$$


Thus, the Norton equivalent resistance is given by

$$R_n = \frac{V_t}{I_t} = \frac{1 \text{ V}}{\frac{20}{3} \text{ mA}} = \frac{3}{20} \text{ k}\Omega = 150 \Omega$$


The Norton equivalent circuit is shown in Figure 4.124.

**FIGURE 4.124**

The Norton equivalent circuit.

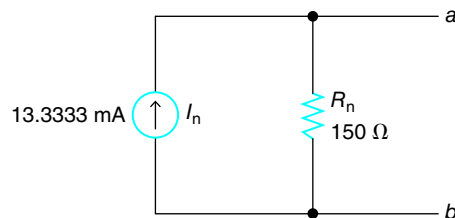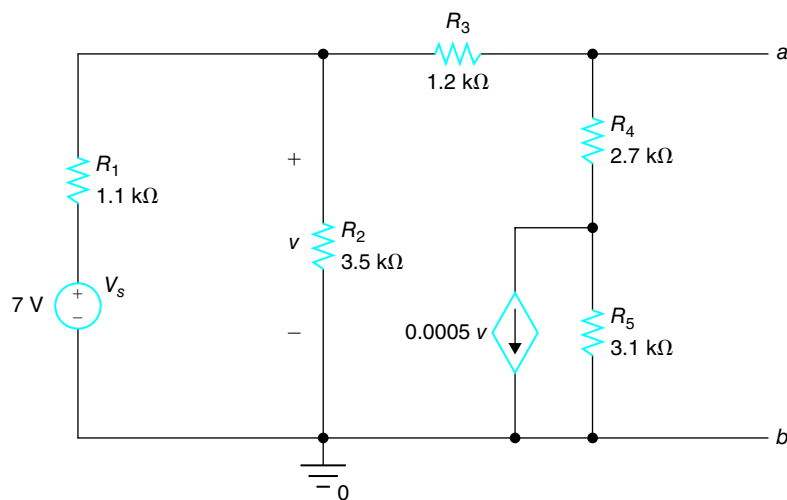**Exercise 4.16**Find the Norton equivalent circuit between terminals  $a$  and  $b$  for the circuit shown in Figure 4.125.**FIGURE 4.125**

Circuit for EXERCISE 4.16.

**Answer:**


$$I_n = 1.7762 \text{ mA}, R_n = 1.2934 \text{ k}\Omega$$

**EXAMPLE 4.17**

Find the Norton equivalent circuit between terminals  $a$  and  $b$  for the circuit shown in Figure 4.126.

**FIGURE 4.126**


Circuit for  
EXAMPLE 4.17.

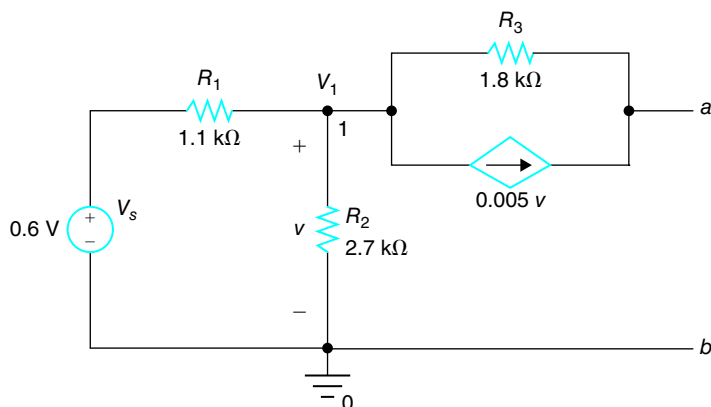

To find the Norton equivalent current, we short-circuit  $a$  and  $b$ , as shown in Figure 4.127, and find the current through the short circuit.

**FIGURE 4.127**

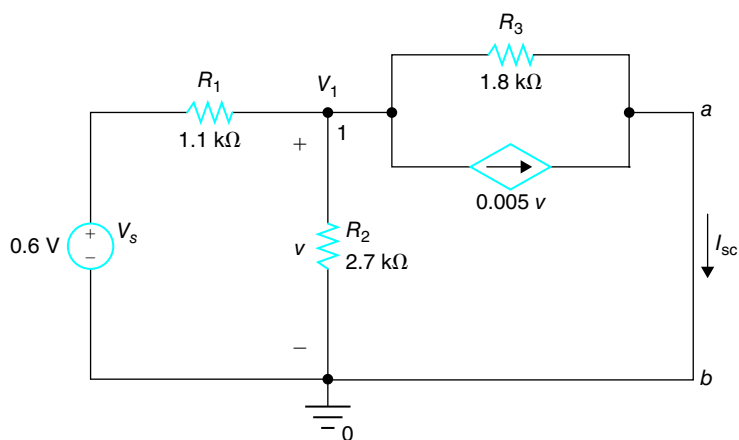Circuit shown in  
Figure 4.126 with  
 $a$  and  $b$  short-  
circuited.



Summing the currents leaving node 1, we obtain

$$\frac{V_1 - 0.6}{1100} + \frac{V_1}{2700} + \frac{V_1}{1800} + 0.005 \times V_1 = 0$$

which can be rearranged as

$$\left( \frac{1}{1100} + \frac{1}{2700} + \frac{1}{1800} + 0.005 \right) V_1 = \frac{0.6}{1100}$$

Thus, we have

$$V_1 = \frac{\frac{0.6}{1100}}{\frac{1}{1100} + \frac{1}{2700} + \frac{1}{1800} + 0.005} = 0.079803 \text{ V}$$

*continued*



Example 4.17 continued


The short-circuit current  $I_{sc}$ , which is the Norton equivalent current  $I_n$ , is given by

$$I_n = I_{sc} = \frac{V_1}{R_3} + 0.005 \times V_1 = \frac{0.079803}{1800} + 0.005 \times 0.079803 = 443.3498 \mu\text{A}$$

To find the Norton equivalent resistance  $R_n$ , we deactivate the voltage source  $V_s$  by short-circuiting it and then apply a test voltage  $V_t$  of 1 V between terminals  $a$  and  $b$ , as shown in Figure 4.128.

**FIGURE 4.128**

Circuit with a test voltage.

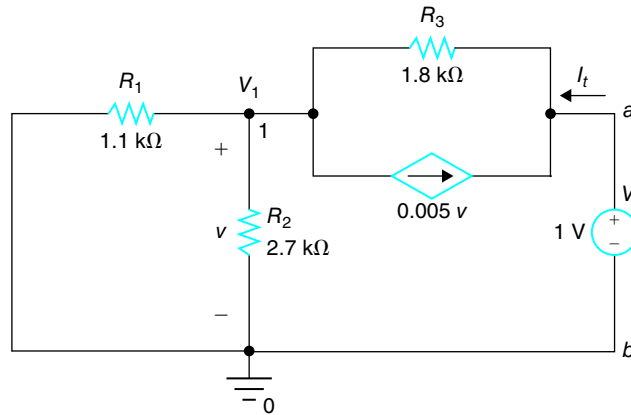

Summing the currents leaving node 1 of the circuit shown in Figure 4.128, we obtain

$$\frac{V_1}{1100} + \frac{V_1}{2700} + \frac{V_1 - 1}{1800} + 0.005 \times V_1 = 0$$

which can be rearranged as

$$\left( \frac{1}{1100} + \frac{1}{2700} + \frac{1}{1800} + 0.005 \right) V_1 = \frac{1}{1800}$$

Thus, we have

$$V_1 = \frac{\frac{1}{1800}}{\frac{1}{1100} + \frac{1}{2700} + \frac{1}{1800} + 0.005} = 0.0812808 \text{ V}$$

The current  $I_t$  flowing out of the positive terminal of the test voltage is given by

$$I_t = \frac{V_t - V_1}{R_3} - 0.005 \times V_1 = 103.9956 \mu\text{A}$$


The Norton equivalent resistance is given by

$$R_n = \frac{V_t}{I_t} = \frac{1 \text{ V}}{103.9956 \mu\text{A}} = 9.6158 \text{ k}\Omega$$

The Norton equivalent circuit is shown in Figure 4.129.

**FIGURE 4.129**

The Norton equivalent circuit.

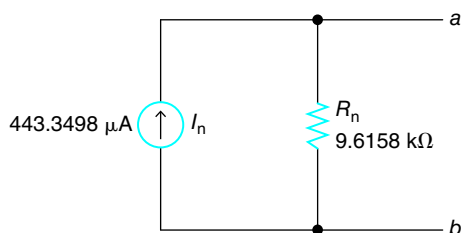


**Exercise 4.17**

Find the Norton equivalent circuit between terminals  $a$  and  $b$  for the circuit shown in Figure 4.130.

**FIGURE 4.130**

Circuit for  
EXERCISE 4.17.

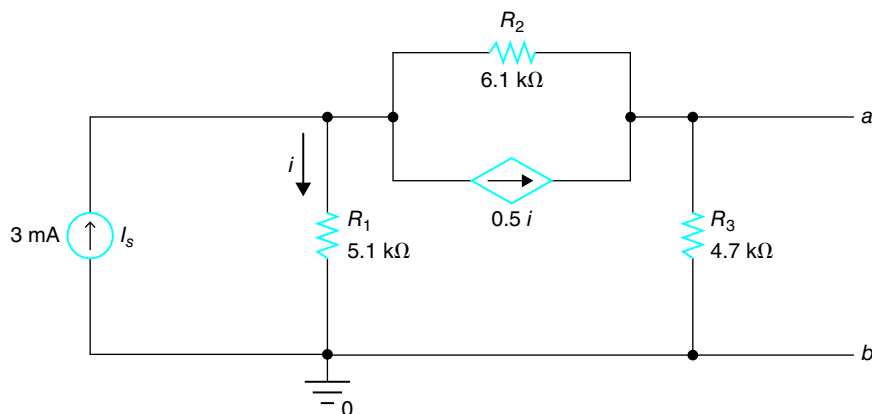

**Answer:**


$$I_n = 1.7158 \text{ mA}, R_n = 3.5343 \text{ k}\Omega$$

**EXAMPLE 4.18**

Find the Norton equivalent circuit between terminals  $a$  and  $b$  for the circuit shown in Figure 4.131.

**FIGURE 4.131**

Circuit for  
EXAMPLE 4.18.

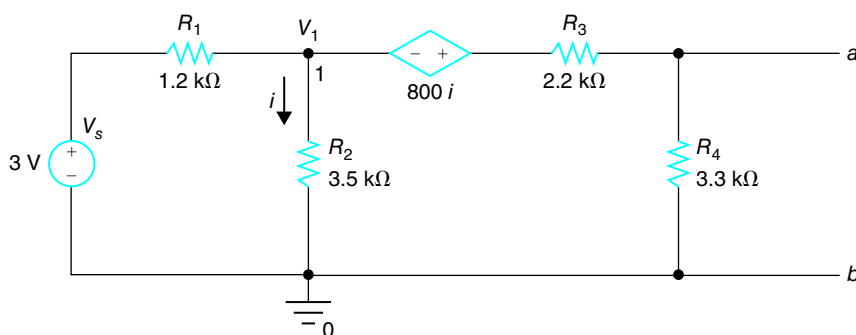

We can find the open-circuit voltage  $V_{oc}$  between  $a$  and  $b$ . The open-circuit voltage is the voltage across  $R_4$ . Summing the currents leaving node 1, we obtain

$$\frac{V_1 - 3}{1200} + \frac{V_1}{3500} + \frac{V_1 + 800 \times \frac{V_1}{3500}}{2200 + 3300} = 0$$

which can be rearranged as

$$\left( \frac{1}{1200} + \frac{1}{3500} + \frac{1 + \frac{800}{3500}}{5500} \right) V_1 = \frac{3}{1200}$$

*continued*

Example 4.18 continued


Thus, we have

$$V_1 = \frac{\frac{3}{1200}}{\frac{1}{1200} + \frac{1}{3500} + \frac{1 + \frac{800}{3500}}{5500}} = 1.8623 \text{ V}$$

The open-circuit voltage is given by

$$V_{oc} = \left( V_1 + 800 \times \frac{V_1}{3500} \right) \times \frac{R_4}{R_3 + R_4} = 1.8623 \times \left( 1 + \frac{800}{3500} \right) \times \frac{3300}{5500} = 1.3728 \text{ V}$$

The Norton equivalent current is the short-circuit current when  $a$  and  $b$  are short-circuited, as shown in Figure 4.132.

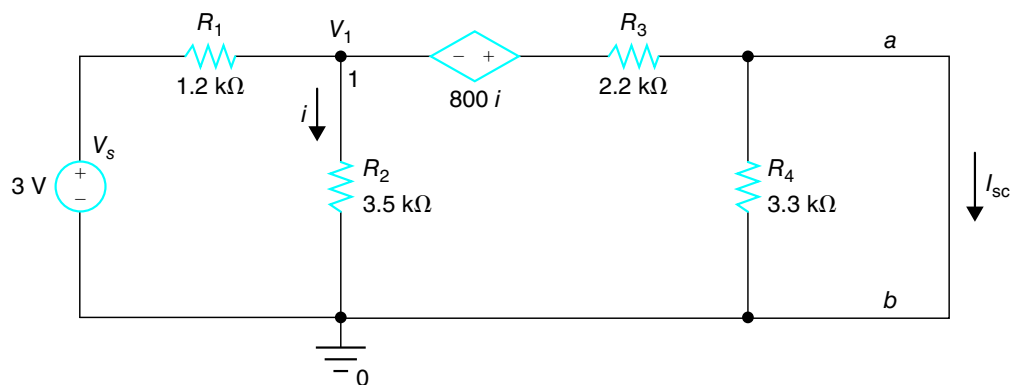**FIGURE 4.132**Circuit with  $a$  and  $b$  short-circuited.

Since the potential difference across  $R_4$  is zero, there is no current through  $R_4$ . The short-circuit current is the current through  $R_3$ . Summing the currents leaving node 1, we obtain

$$\frac{V_1 - 3}{1200} + \frac{V_1}{3500} + \frac{V_1 + 800 \times \frac{V_1}{3500}}{2200} = 0$$

which can be rearranged as

$$\left( \frac{1}{1200} + \frac{1}{3500} + \frac{1 + \frac{800}{3500}}{2200} \right) V_1 = \frac{3}{1200}$$

Thus, we have


$$V_1 = \frac{\frac{3}{1200}}{\frac{1}{1200} + \frac{1}{3500} + \frac{1 + \frac{800}{3500}}{2200}} = 1.4903 \text{ V}$$

continued

Example 4.18 continued

**FIGURE 4.133**

The Norton equivalent circuit.

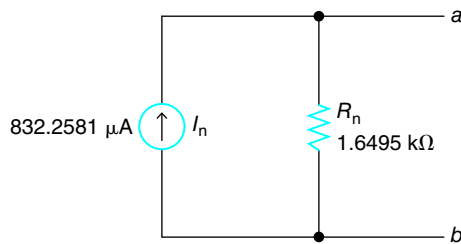

The short-circuit current is given by

$$I_n = I_{sc} = \frac{V_1 + 800 \times \frac{V_1}{3500}}{R_3} = \frac{1.8309 \text{ V}}{2200 \Omega} = 832.2581 \mu\text{A}$$

The Norton equivalent resistance is given by

$$R_n = \frac{V_{oc}}{I_{sc}} = \frac{1.3728 \text{ V}}{832.2581 \mu\text{A}} = 1.6495 \text{ k}\Omega$$

The Norton equivalent circuit is shown in Figure 4.133.

**MATLAB****%EXAMPLE 4.18**


```
clear all;format long;
R1=1200;R2=3500;R3=2200;R4=3300;Vs=3;kr=800;
syms V1 Va
%Voc
V1=solve((V1-Vs)/R1+V1/R2+(V1+kr*V1/R2)/(R3+R4));
Voc=(V1+kr*V1/R2)*R4/(R3+R4);
%Isc
Va=solve((Va-Vs)/R1+Va/R2+(Va+kr*Va/R2)/R3);
Isc=(Va+kr*Va/R2)/R3;
Rn=Voc/Isc;
In=Isc;
V1=vpa(V1,7)
Voc=vpa(Voc,7)
Va=vpa(Va,7)
Rn=vpa(Rn,7)
Isc=vpa(Isc,7)
In=vpa(In,7)
```

Answers:

```
V1 =
1.862302
Voc =
1.372783
Va =
1.490323
Rn =
1649.468
Isc =
0.0008322581
In =
0.0008322581
```

**Exercise 4.18**Find the Norton equivalent circuit between terminals  $a$  and  $b$  for the circuit shown in Figure 4.134.*continued*

Exercise 4.18 continued

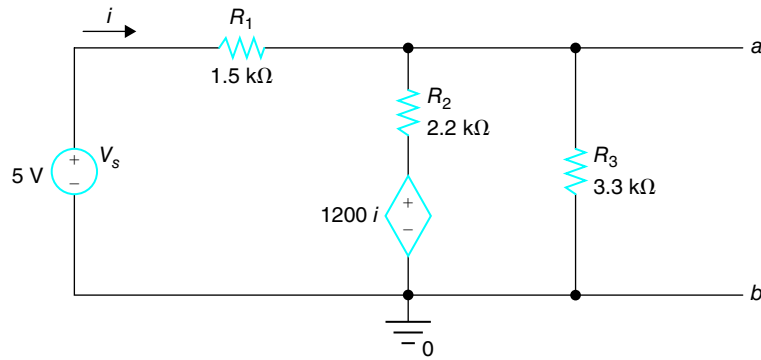
**FIGURE 4.134**Circuit for  
EXERCISE 4.18.**Answer:**

$$I_n = 5.1515 \text{ mA}, R_n = 559.322 \Omega.$$

## 4.6 Maximum Power Transfer

**FIGURE 4.135**

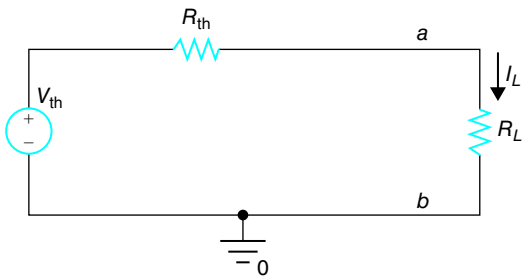A load connected to the Thévenin equivalent circuit.



Suppose that a load with resistance  $R_L$  is connected to a circuit between terminals  $a$  and  $b$ . We are interested in finding the power  $P_L$  delivered to the load and finding the load resistance  $R_L$  that maximizes the power delivered to the load. We first find the Thévenin equivalent circuit with respect to the terminals  $a$  and  $b$ . Let  $V_{th}$  be the Thévenin equivalent voltage and  $R_{th}$  be the Thévenin equivalent resistance. With the original circuit replaced by the Thévenin equivalent circuit, we obtain the circuit shown in Figure 4.135.

The current through the load resistor is given by

$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

and the voltage across the load resistor is given by

$$V_L = R_L I_L = \frac{R_L V_{th}}{R_{th} + R_L}$$

Thus, the power delivered to the load is

$$p_L = I_L V_L = \frac{R_L V_{th}^2}{(R_{th} + R_L)^2}$$


When  $R_L = 0$ ,  $p_L = 0$ ; and when  $R_L = \infty$ ,  $p_L = 0$ . The power delivered to the load  $p_L$  must peak at a certain value. Figure 4.136 shows  $p_L$  as a function of  $R_L$  for  $0 \leq R_L \leq 5R_{th}$  ( $V_{th} = 1 \text{ V}$ ,  $R_{th} = 1 \Omega$ ).

From this figure, we can see that when  $p_L$  is at its maximum, the derivative of  $p_L$  with respect to  $R_L$  is zero; that is,  $dp_L/dR_L = 0$ . Using

$$\frac{d}{dt} \left( \frac{u(t)}{v(t)} \right) = \frac{v(t) \frac{du(t)}{dt} - u(t) \frac{dv(t)}{dt}}{v^2(t)},$$

FIGURE 4.136

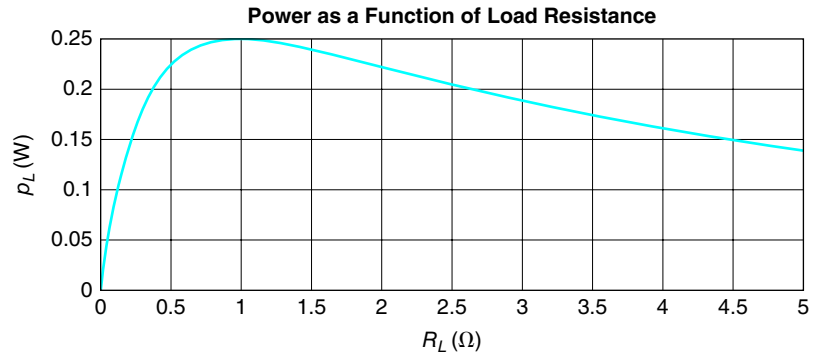Plot of the power on the load as a function of load resistance.



we have

$$\begin{aligned}\frac{dp_L}{dR_L} &= \frac{d}{dR_L} \left( \frac{R_L(V_{th})^2}{(R_{th} + R_L)^2} \right) = \frac{(R_{th} + R_L)^2 \frac{dR_L}{dR_L} - R_L \frac{d(R_{th} + R_L)^2}{dR_L}}{(R_{th} + R_L)^4} (V_{th})^2 \\ &= \frac{(R_{th} + R_L)^2 - 2R_L(R_{th} + R_L)}{(R_{th} + R_L)^4} (V_{th})^2 = \frac{(R_{th} + R_L)(R_{th} - R_L)}{(R_{th} + R_L)^4} (V_{th})^2\end{aligned}$$

Setting  $dp_L/dR_L = 0$ , we have two solutions:  $R_L = -R_{th}$  or  $R_L = R_{th}$ . We take the positive answer. Thus, the load resistance  $R_L$  that maximizes the power delivered to the load is given by the Thévenin equivalent resistance from terminals  $a$  and  $b$ .

The maximum power delivered to the load when the load resistance is  $R_L = R_{th}$  is given by

$$p_{L, \max} = \frac{R_{th} V_{th}^2}{(R_{th} + R_{th})^2} = \frac{V_{th}^2}{4R_{th}} = \frac{V_{th}^2}{4R_L} \quad (4.50)$$

For the Norton equivalent circuit with load  $R_L$  shown in Figure 4.137, let the current through the load be  $I_L$ . Then, from the current divider rule, we have

$$I_L = \frac{R_n}{R_n + R_L} \times I_n$$

The power on the load is given by


$$p_L = I_L^2 R_L = \frac{R_L}{(R_n + R_L)^2} R_n^2 I_n^2$$

$$\begin{aligned}\frac{dp_L}{dR_L} &= \frac{d}{dR_L} \left( \frac{R_L}{(R_n + R_L)^2} (R_n I_n)^2 \right) = \frac{(R_n + R_L)^2 \frac{dR_L}{dR_L} - R_L \frac{d(R_n + R_L)^2}{dR_L}}{(R_n + R_L)^4} (R_n I_n)^2 \\ &= \frac{(R_n + R_L)^2 - 2R_L(R_n + R_L)}{(R_n + R_L)^4} (R_n I_n)^2 = \frac{(R_n + R_L)(R_n - R_L)}{(R_n + R_L)^4} (R_n I_n)^2\end{aligned}$$

Setting  $dp_L/dR_L = 0$ , we have two solutions:  $R_L = -R_n$  and  $R_L = R_n$ . We take the positive answer. Thus, the load resistance  $R_L$  that maximizes the power delivered to the load is given by the Norton equivalent resistance from terminals  $a$  and  $b$ .

FIGURE 4.137

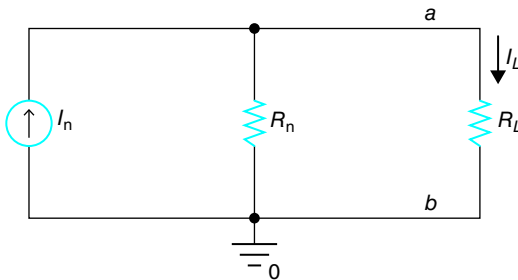A Norton equivalent circuit with load  $R_L$ .



The maximum power delivered to the load when the load resistance is  $R_L = R_n$  is given by

$$p_{L, \max} = \frac{R_n}{(R_n + R_n)^2} R_n^2 I_n^2 = \frac{I_n^2 R_n}{4} = \frac{I_n^2 R_L}{4} \quad (4.51)$$

We can get the same result using source transformation.

### EXAMPLE 4.19

For the circuit shown in Figure 4.138, find the value of the load resistance  $R_L$  that maximizes the power delivered to the load. Also, find the maximum power delivered to  $R_L$ .

FIGURE 4.138

Circuit for  
EXAMPLE 4.19.


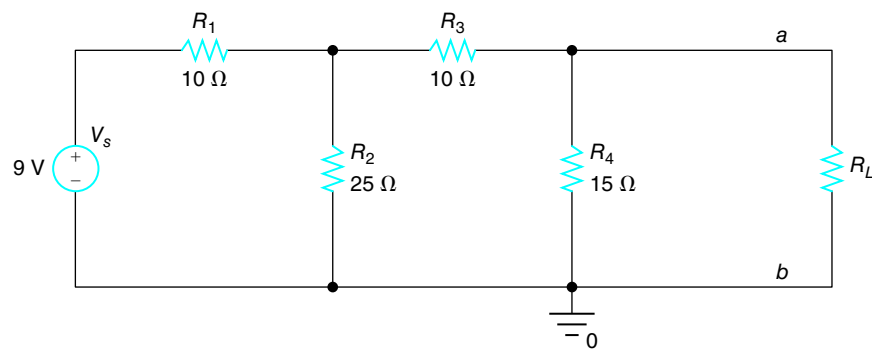


Figure 4.139 shows the circuit in Figure 4.138 without the load resistor.

FIGURE 4.139

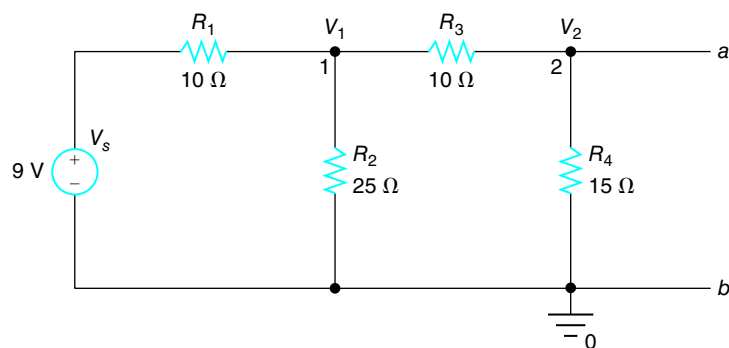Circuit shown in  
Figure 4.138 without  
the load resistor.



Summing the currents leaving node 1, we obtain

$$\frac{V_1 - 9}{10} + \frac{V_1}{25} + \frac{V_1 - V_2}{10} = 0 \quad (4.52)$$

Multiplication by 50 yields

$$5V_1 - 45 + 2V_1 + 5V_1 - 5V_2 = 0$$

*continued*

Example 4.19 continued

which can be simplified to

$$12V_1 - 5V_2 = 45 \quad (4.53)$$

Summing the currents leaving node 2, we obtain

$$\frac{V_2 - V_1}{10} + \frac{V_2}{15} = 0 \quad (4.54)$$

Multiplication by 30 results in

$$3V_2 - 3V_1 + 2V_2 = 0$$

which can be simplified to

$$-3V_1 + 5V_2 = 0 \quad (4.55)$$

Adding Equations (4.53) and (4.55), we get

$$9V_1 = 45$$

Thus,  $V_1 = 5$  V. Substituting this into Equation (4.55), we obtain

$$5V_2 = 15$$


from which we have  $V_2 = 3$  V. The Thévenin equivalent voltage between  $a$  and  $b$  is voltage  $V_2$ . Thus, we have

$$V_{th} = 3 \text{ V}$$

The Thévenin equivalent resistance  $R_{th}$  is the equivalent resistance across  $a$  and  $b$  after deactivating the voltage source by short-circuiting it, as shown in Figure 4.140.

**FIGURE 4.140**

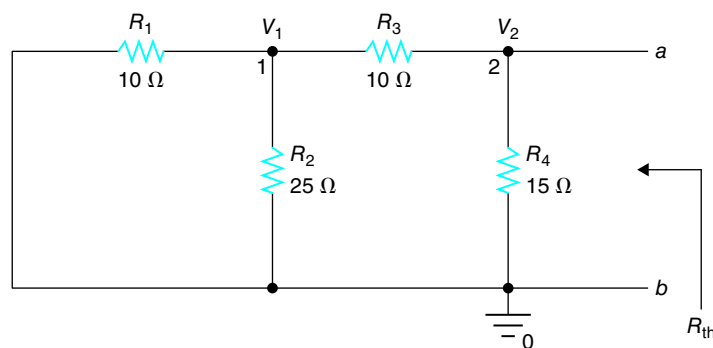The circuit shown in Figure 4.139 with the voltage source deactivated.



Let the equivalent resistance of the parallel connection of  $R_1$  and  $R_2$  be  $R_a$ . Then,  $R_a$  is

$$R_a = R_1 \parallel R_2 = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{10 \, \Omega \times 25 \, \Omega}{10 \, \Omega + 25 \, \Omega} = \frac{250}{35} \, \Omega = \frac{50}{7} \, \Omega$$


continued



Example 4.19 continued

**FIGURE 4.141**

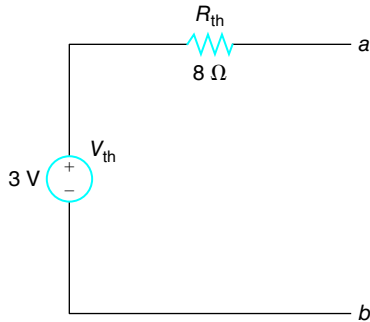The Thévenin equivalent circuit between  $a$  and  $b$ .



Let  $R_b$  be the equivalent resistance of the series connection of  $R_3$  and  $R_a$ . Then, we have

$$R_b = R_3 + R_a = 10\ \Omega + 50/7\ \Omega = 120/7\ \Omega$$

The Thévenin equivalent resistance  $R_{th}$  is given by the equivalent resistance of the parallel connection of  $R_4$  and  $R_b$ . Thus, we obtain

$$R_{th} = R_4 \parallel R_b = \frac{R_4 \times R_b}{R_4 + R_b} = \frac{15\ \Omega \times \frac{120}{7}\ \Omega}{15\ \Omega + \frac{120}{7}\ \Omega} = \frac{1800}{225}\ \Omega = 8\ \Omega$$

The Thévenin equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure 4.139 is shown in Figure 4.141.

The load resistance for maximum power transfer is  $R_L = 8\ \Omega$ , and the maximum power delivered to the load is given by


$$p_L = \frac{V_{th}^2}{4R_L} = \frac{3^2}{4 \times 8} = \frac{9}{32}\ \text{W} = 0.28125\ \text{W} = 281.25\ \text{mW}$$

**Exercise 4.19**

For the circuit shown in Figure 4.142, find the value of the load resistance  $R_L$  that maximizes the power delivered to the load. Also, find the maximum power delivered to  $R_L$ .

**FIGURE 4.142**

Circuit for EXERCISE 4.19.

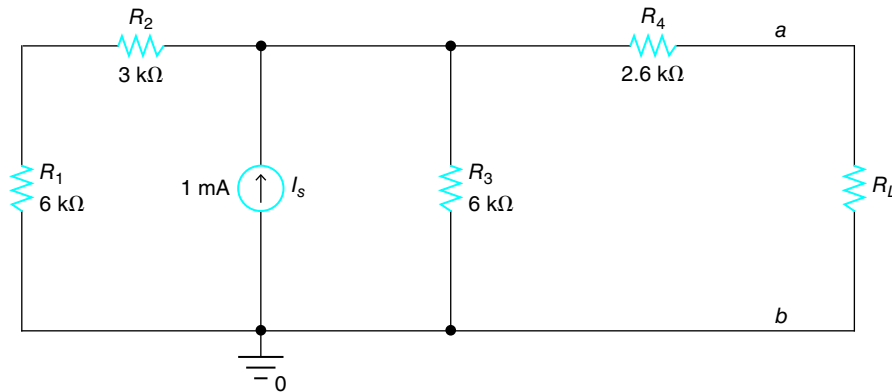

**Answer:**

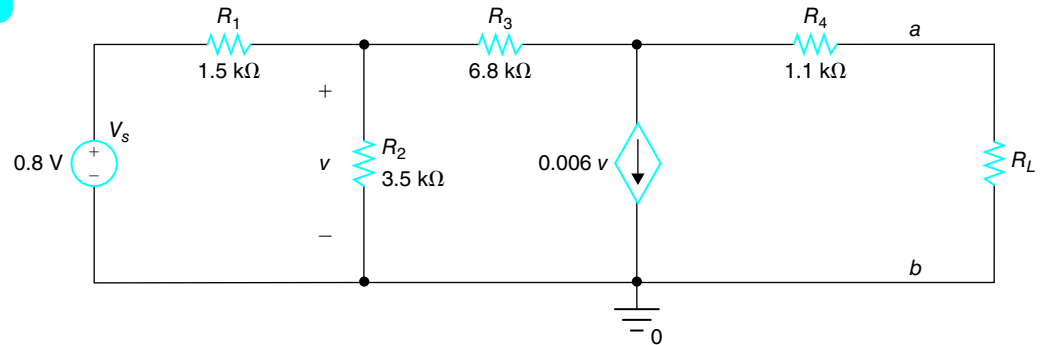
$$V_{th} = 3.6\ \text{V}, R_{th} = 6.2\ \text{k}\Omega, R_L = R_{th} = 6.2\ \text{k}\Omega, p_L = 522.5806\ \mu\text{W}.$$

**EXAMPLE 4.20**


For the circuit shown in Figure 4.143, find the value of the load resistance  $R_L$  that maximizes the power delivered to the load. Also, find the maximum power delivered to  $R_L$ .

*continued*

Example 4.20 continued

**FIGURE 4.143**Circuit for  
EXAMPLE 4.20.

The circuit without the load connected is shown in Figure 4.144.

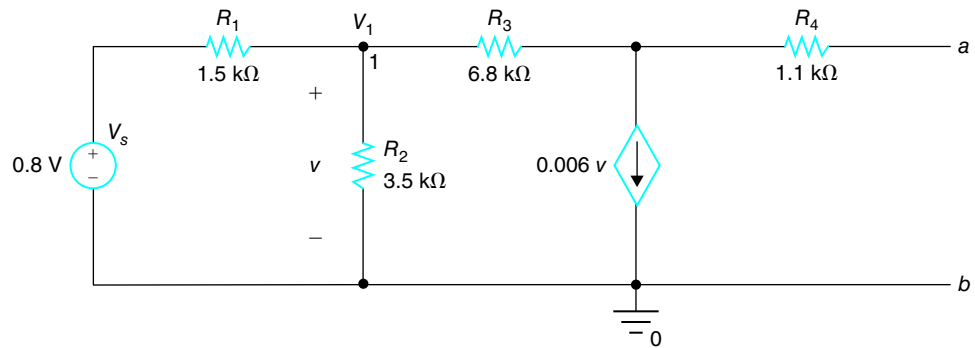**FIGURE 4.144**The circuit in  
Figure 4.143 without  
the load connected.No current flows through  $R_4$ . Summing the currents leaving node 1, we obtain

$$\frac{V_1 - 0.8}{1500} + \frac{V_1}{3500} + 0.006 \times V_1 = 0$$

which can be rearranged as

$$\left( \frac{1}{1500} + \frac{1}{3500} + 0.006 \right) V_1 = \frac{0.8}{1500}$$

Thus, we have

$$V_1 = \frac{\frac{0.8}{1500}}{\frac{1}{1500} + \frac{1}{3500} + 0.006} \times \frac{10,500}{10,500} = \frac{7 \times 0.8}{7 + 3 + 63} = \frac{5.6}{73} = 0.07671233 \text{ V}$$

The open-circuit voltage between  $a$  and  $b$  is given by

$$V_{th} = V_{oc} = V_1 - 0.006V_1 \times R_3 = 0.07671233(1 - 0.006 \times 6800) = -3.05315 \text{ V}$$

To find the short-circuit current,  $a$  and  $b$  are short-circuited, as shown in Figure 4.145. Summing the currents leaving node 1, we obtain


$$\frac{V_1 - 0.8}{1500} + \frac{V_1}{3500} + \frac{V_1 - V_2}{6800} = 0$$

continued

Example 4.20 continued

**FIGURE 4.145**

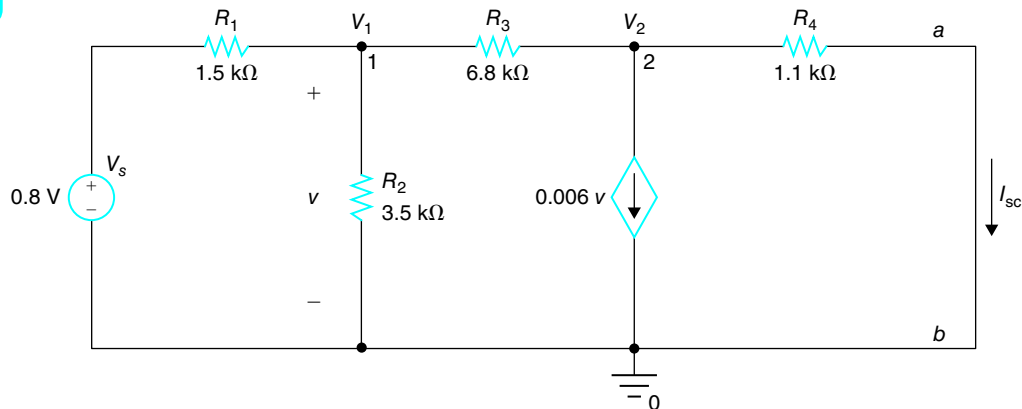The circuit in Figure 4.144 with  $a$  and  $b$  shorted.



which can be rearranged as

$$\left( \frac{1}{1500} + \frac{1}{3500} + \frac{1}{6800} \right) V_1 - \frac{1}{6800} V_2 = \frac{0.8}{1500}$$

or

$$0.00109944 V_1 - 1.470588 \times 10^{-4} V_2 = 5.33333 \times 10^{-4} \quad (4.56)$$

Summing the currents leaving node 2, we obtain

$$\frac{V_2 - V_1}{6800} + 0.006 \times V_1 + \frac{V_2}{1100} = 0$$

which can be rearranged as

$$\left( 0.006 - \frac{1}{6800} \right) V_1 + \left( \frac{1}{6800} + \frac{1}{1100} \right) V_2 = 0$$

or

$$0.00585294 V_1 + 0.00105615 V_2 = 0 \quad (4.57)$$

Solving Equation (4.57) for  $V_2$ , we obtain

$$V_2 = -\frac{0.00585294}{0.00105615} V_1 = -5.54177 V_1$$

Substituting  $V_2$  into Equation (4.56), we get

$$0.00109944 V_1 - 1.470588 \times 10^{-4} (-5.54177 V_1) = 5.33333 \times 10^{-4}$$

Thus,

$$V_1 = \frac{5.33333 \times 10^{-4}}{0.00109944 + 1.470588 \times 10^{-4} \times 5.54177} = 0.27859 \text{ V}$$

$$V_2 = -5.54177 V_1 = -1.54388 \text{ V}$$

continued

Example 4.20 continued

Alternatively, application of Cramer's rule to Equations (4.56) and (4.57) yields

$$V_1 = \frac{\begin{vmatrix} 5.33333 \times 10^{-4} & -1.470588 \times 10^{-4} \\ 0 & 0.00105615 \end{vmatrix}}{\begin{vmatrix} 0.00109944 & -1.470588 \times 10^{-4} \\ 0.00585294 & 0.00105615 \end{vmatrix}} = 0.27859 \text{ V}$$

$$V_2 = \frac{\begin{vmatrix} 0.00109944 & 5.33333 \times 10^{-4} \\ 0.00585294 & 0 \end{vmatrix}}{\begin{vmatrix} 0.00109944 & -1.470588 \times 10^{-4} \\ 0.00585294 & 0.00105615 \end{vmatrix}} = -1.54388 \text{ V}$$

The short-circuit current is given by

$$I_{sc} = \frac{V_2}{R_4} = -0.00140353 \text{ A}$$

The Thévenin equivalent resistance is given by


$$R_{th} = \frac{V_{oc}}{I_{sc}} = 2.1753 \text{ k}\Omega$$

The load resistance that provides maximum power transfer is  $R_L = 2.1753 \text{ k}\Omega$ .  
The maximum power transferred is given by

$$p_L = \frac{V_{th}^2}{4R_L} = 1.0713 \text{ mW}$$

**Exercise 4.20**

For the circuit shown in Figure 4.146, find the value of the load resistance  $R_L$  that maximizes the power delivered to the load. Also, find the maximum power delivered to  $R_L$ .

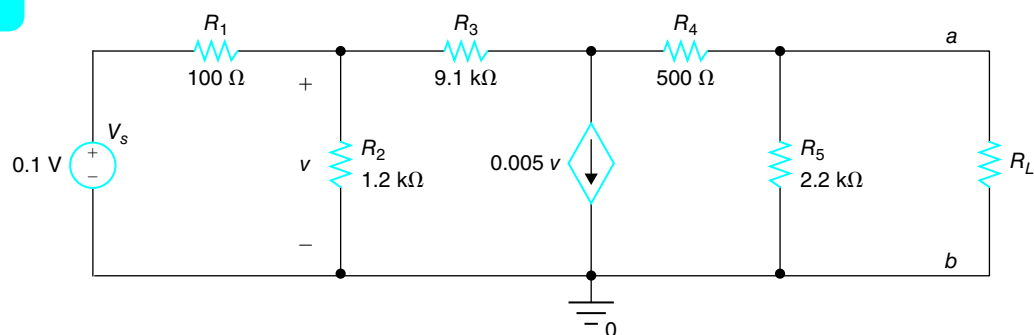**FIGURE 4.146**Circuit for  
EXERCISE 4.20.**Answer:**

$$R_L = 1.6616 \text{ k}\Omega, p_L = 71.1816 \text{ }\mu\text{W}.$$

## EXAMPLE 4.21

For the circuit shown in Figure 4.147, find the value of the load resistance  $R_L$  that maximizes the power delivered to the load. Also, find the maximum power delivered to  $R_L$ .

FIGURE 4.147

Circuit for  
EXAMPLE 4.21.


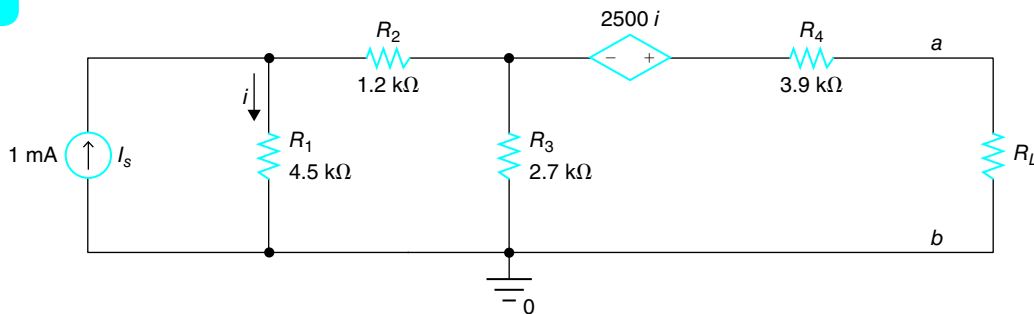


Figure 4.148 shows the circuit without the load resistor. There is no current through  $R_4$ .

FIGURE 4.148

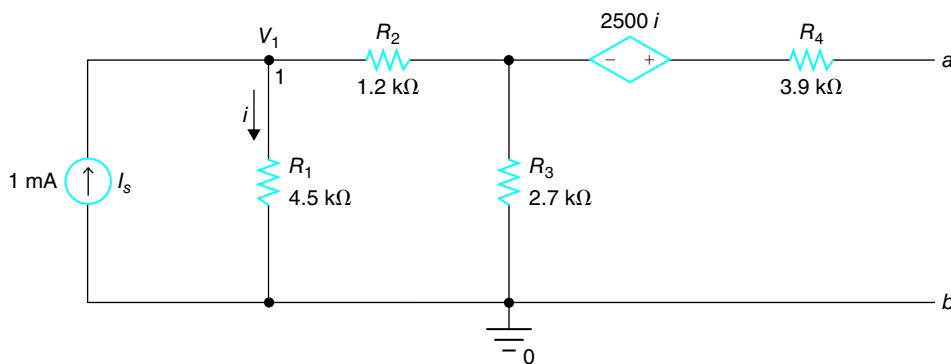The circuit in  
Figure 4.147 without  
the load resistor.



Summing the currents leaving node 1, we obtain

$$-0.001 + \frac{V_1}{4500} + \frac{V_1}{1200 + 2700} = 0$$

which can be rearranged as

$$\left( \frac{1}{4500} + \frac{1}{3900} \right) V_1 = 0.001$$

Thus, we have

$$V_1 = \frac{0.001}{\frac{1}{4500} + \frac{1}{3900}} = 2.0893 \text{ V}$$

The open-circuit voltage, which is also the Thévenin voltage, is given by

$$\begin{aligned} V_{th} = V_{oc} &= V_1 \times \frac{R_3}{R_2 + R_3} + 2500 \times \frac{V_1}{R_1} \\ &= 2.0893 \times \frac{2700}{1200 + 2700} + 2500 \times \frac{2.0893}{4500} = 2.6071 \text{ V} \end{aligned}$$


continued

Example 4.21 continued

To find the short-circuit current, terminals  $a$  and  $b$  are short-circuited, as shown in Figure 4.149.

**FIGURE 4.149**

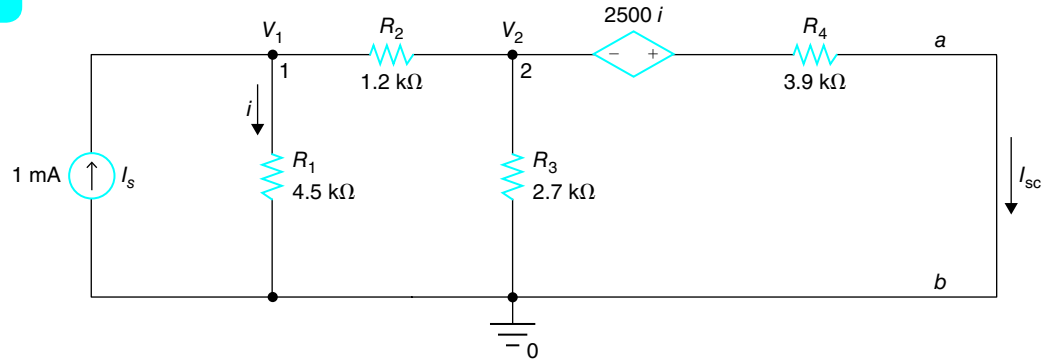The circuit in Figure 4.148 with  $a$  and  $b$  shorted.



Summing the currents leaving node 1, we obtain

$$-0.001 + \frac{V_1}{4500} + \frac{V_1 - V_2}{1200} = 0$$

which can be rearranged as

$$\left( \frac{1}{4500} + \frac{1}{1200} \right) V_1 - \frac{1}{1200} V_2 = 0.001$$

or

$$0.00105556V_1 - 8.33333 \times 10^{-4}V_2 = 0.001 \quad (4.58)$$

Summing the currents leaving node 2, we obtain

$$\frac{V_2 - V_1}{1200} + \frac{V_2}{2700} + \frac{V_2 + 2500 \times \frac{V_1}{4500}}{3900} = 0,$$

which can be rearranged as

$$\left( \frac{-1}{1200} + \frac{5}{9} \right) V_1 + \left( \frac{1}{1200} + \frac{1}{2700} + \frac{1}{3900} \right) V_2 = 0$$

or

$$-6.908832 \times 10^{-4}V_1 + 0.001460114V_2 = 0 \quad (4.59)$$

Solving Equation (4.59) for  $V_2$ , we obtain

$$V_2 = \frac{6.908832 \times 10^{-4}}{0.001460114} V_1 = 0.473171V_1$$

Substituting  $V_2$  into Equation (4.58), we get

$$0.00105556V_1 - 8.33333 \times 10^{-4}(0.473171V_1) = 0.001$$

continued

Example 4.21 continued

Thus,

$$V_1 = \frac{0.001}{0.00105556 - 8.33333 \times 10^{-4} \times 0.473171} = 1.5123 \text{ V}$$

$$V_2 = 0.473171 V_1 = 0.7156 \text{ V}$$

Alternatively, application of Cramer's rule to Equations (4.58) and (4.59) yields

$$V_1 = \frac{\begin{vmatrix} 0.001 & -8.33333 \times 10^{-4} \\ 0 & 0.001460114 \end{vmatrix}}{\begin{vmatrix} 0.00105556 & -8.33333 \times 10^{-4} \\ -6.908832 \times 10^{-4} & 0.001460114 \end{vmatrix}} = 1.5123 \text{ V}$$

$$V_2 = \frac{\begin{vmatrix} 0.00105556 & 0.001 \\ -6.908832 \times 10^{-4} & 0 \end{vmatrix}}{\begin{vmatrix} 0.00105556 & -8.33333 \times 10^{-4} \\ -6.908832 \times 10^{-4} & 0.001460114 \end{vmatrix}} = 0.7156 \text{ V}$$

The short-circuit current is given by

$$I_{sc} = \frac{V_2 + 2500 \times \frac{V_1}{R_1}}{R_4} = 0.3989 \text{ mA}$$

The Thévenin equivalent resistance is the ratio of  $V_{oc}$  to  $I_{sc}$ :

$$R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{V_{th}}{I_{sc}} = 6.5357 \text{ k}\Omega$$

The load resistance value that provides the maximum power transfer is  $R_L = R_{th} = 6.5357 \text{ k}\Omega$ . The maximum power delivered to the load is given by

$$p_L = \frac{V_{th}^2}{4R_L} = 0.26 \text{ mW}$$

**MATLAB****%EXAMPLE 4.21**

```
clear all;format long;
Is=1e-3;R1=4500;R2=1200;R3=2700;R4=3900;
syms V1 V2 Va Vb
%Voc = Vth
[V1,V2]=solve(-Is+V1/R1+(V1-V2)/R2,(V2-V1)/R2+V2/R3);
Vth=V2+2500*V1/R1;
%Isc
[Va,Vb]=solve(-Is+Va/R1+(Va-Vb)/R2,...
(Vb-Va)/R2+Vb/R3+(Vb+2500*Va/R1)/R4);
Isc=(Vb+2500*Va/R1)/R4;
Rth=Vth/Isc;
PL=Vth^2/(4*Rth);
V1=vpa(V1,7)
```

continued

Example 4.21 continued  
MATLAB continued

```
V2=vpa(V2,7)
Va=vpa(Va,7)
Vb=vpa(Vb,7)
Isc=vpa(Isc,7)
Vth=vpa(Vth,7)
Rth=vpa(Rth,7)
PL=vpa(PL,7)
```

Answers:


```
V1 =
2.089286
V2 =
1.446429
Va =
1.512295
Vb =
0.7155738
Isc =
0.0003989071
Vth =
2.607143
Rth =
6535.714
PL =
0.000260002
```

### Exercise 4.21

For the circuit shown in Figure 4.150, find the value of the load resistance  $R_L$  that maximizes the power delivered to the load. Also, find the maximum power delivered to  $R_L$ .

FIGURE 4.150

Circuit for  
EXERCISE 4.21.

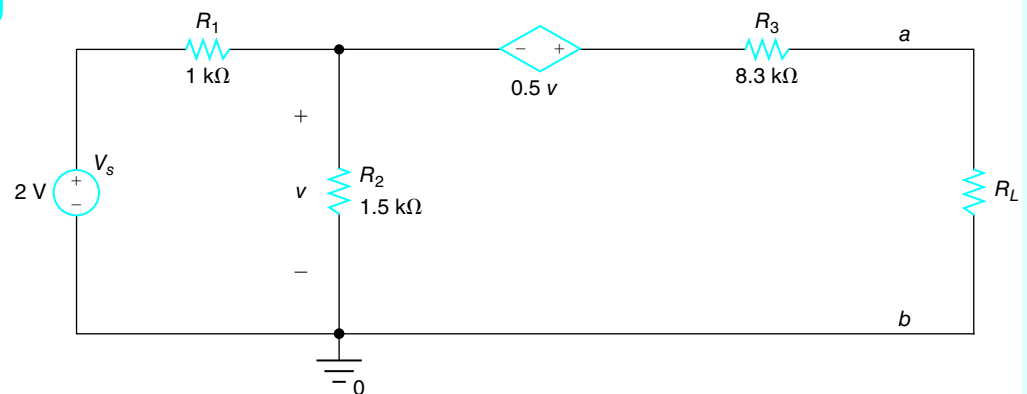

Answer:

$R_L = 9.2 \text{ k}\Omega, p_L = 88.0435 \text{ }\mu\text{W}$ .




## 4.7 PSpice

In PSpice, the **transfer function** can be used to find the Thévenin equivalent resistance. The Thévenin equivalent voltage can be found by finding the open-circuit voltage. In EXAMPLE 4.7, earlier in this chapter, we showed that the Thévenin equivalent voltage is  $V_{th} = 14\text{ V}$  and the Thévenin equivalent resistance is  $R_{th} = 20\text{ k}\Omega$  between  $a$  and  $b$  for the circuit shown in Figure 4.151. We can verify these values using PSpice. If we try to run the circuit as shown in Figure 4.151, we get an error message that says that there are fewer than two connections at node  $a$ . To avoid this error, we can add a resistor with large resistance ( $10^{12}\text{ }\Omega$ ) between  $a$  and  $b$ , as shown in Figure 4.152. Because of the large resistance value, it is virtually an open circuit between  $a$  and  $b$ .


**FIGURE 4.151**

Circuit for  
EXAMPLE 4.7.

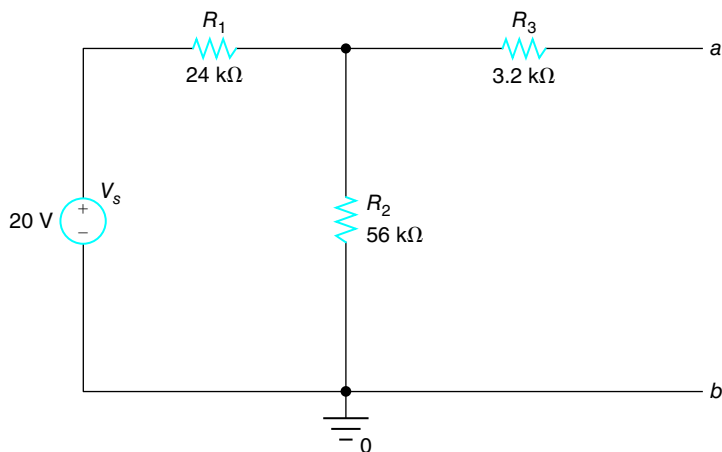

**FIGURE 4.152**

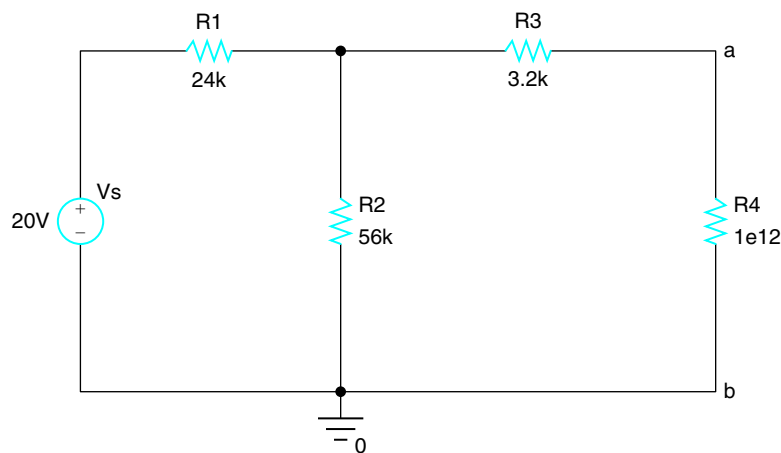The circuit shown  
in Figure 4.151 with  
a large resistor  $R_4$   
between  $a$  and  $b$ .



In the Edit Simulation Profile, check Calculate small-signal DC gain (.TF) and enter  $V_s$  and  $V(R_4)$  respectively for the Input source name and Output variable fields, as shown in Figure 4.153.

After running the simulation, click on the  $V$  (Enable Bias Voltage Display) to display the voltages, as shown in Figure 4.154.

The voltage across  $R_4$  is 14 V. This is the open-circuit voltage and the Thévenin equivalent voltage; that is,

$$V_{th} = V_{oc} = 14\text{ V}$$

FIGURE 4.153

Setting the transfer function.  
(Source: OrCAD PSpice by Cadence)


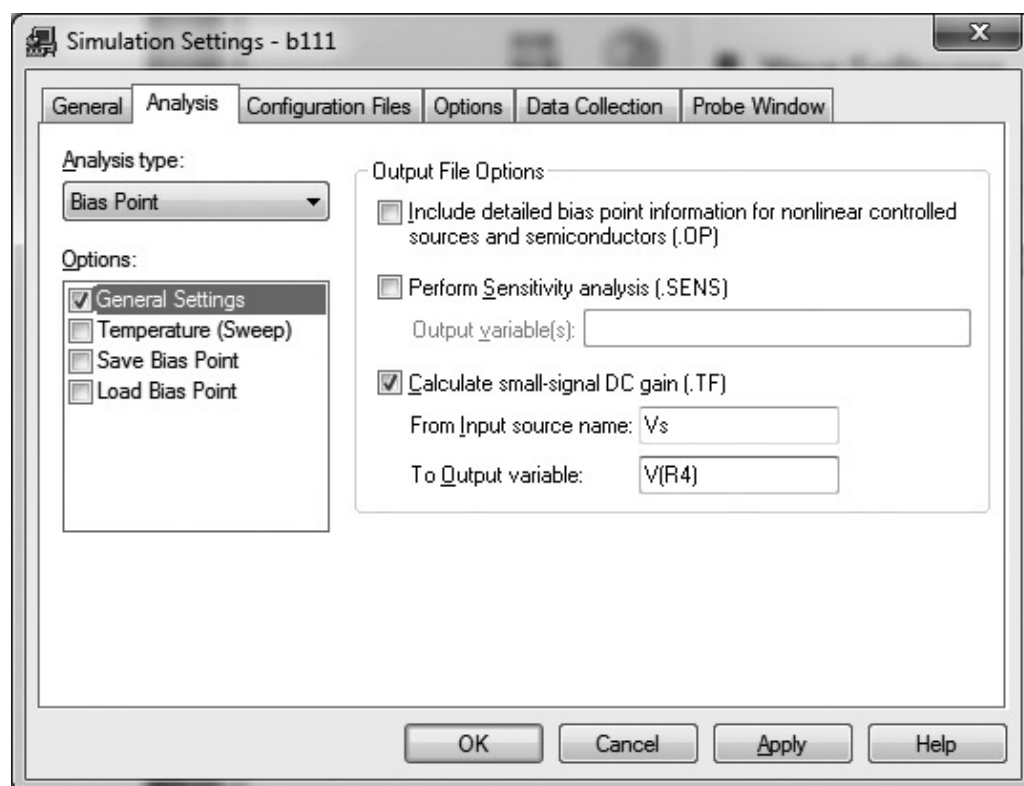


FIGURE 4.154

Node voltages.

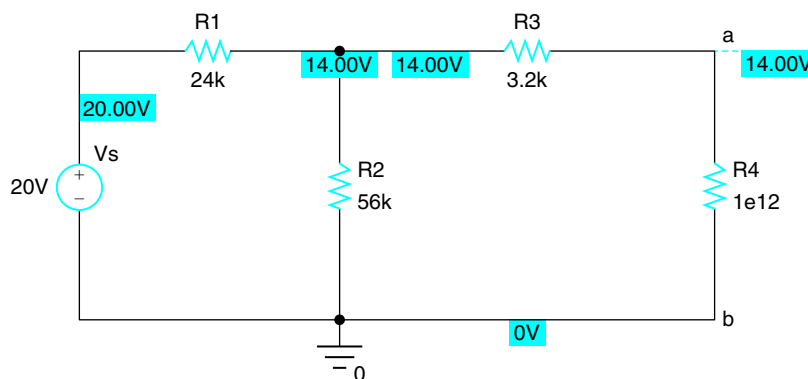

If you click on View Simulation Output File (📄) in the SCHEMATIC1 window, or select View → Output File and scroll down, the following results are shown near the end of the output file:

\*\*\*\* SMALL-SIGNAL CHARACTERISTICS

V(R\_R4)/V\_Vs = 7.000E-01

INPUT RESISTANCE AT V\_Vs = 8.000E+04

OUTPUT RESISTANCE AT V(R\_R4) = 2.000E+04

The first line shows the ratio of the voltage across  $R_4$  to the voltage of the voltage source  $V_s$ , called transfer function; that is,

$$\frac{V(R_4)}{V_s} = 0.7$$

Thus, the voltage across  $R_4$  is given by

$$V(R_4) = 0.7 \times V_s = 0.7 \times 20 = 14 \text{ V}$$

which is the Thévenin equivalent voltage. The second line shows the input resistance of  $80 \text{ k}\Omega$  from the source. Notice that

$$\begin{aligned} R_{in} &= R_1 + [R_2 \parallel (R_3 + R_4)] = 24,000 \Omega + [56,000 \Omega \parallel (3200 \Omega + 10^{12} \Omega)] \\ &= 24,000 \Omega + 56,000 \Omega = 80 \text{ k}\Omega \end{aligned}$$


The third line shows the output resistance of  $20 \text{ k}\Omega$  from the output. Notice that

$$\begin{aligned} R_{out} &= R_{th} = R_3 + (R_1 \parallel R_2) = 3.2 \text{ k}\Omega + (24 \text{ k}\Omega \parallel 56 \text{ k}\Omega) \\ &= 3.2 \text{ k}\Omega + 16.8 \text{ k}\Omega = 20 \text{ k}\Omega \end{aligned}$$

If the value of  $R_4$  is changed to  $10^{-12} \Omega$ , as shown in Figure 4.155, we can find the short-circuit current between  $a$  and  $b$ .

**FIGURE 4.155**

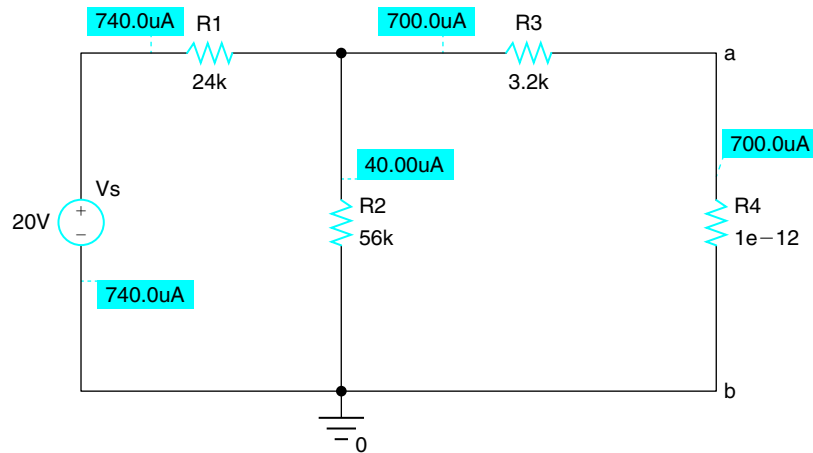A short-circuit current between  $a$  and  $b$ .



The short-circuit current is  $I_{sc} = 700 \mu\text{A}$ . The Thévenin equivalent resistance can also be found by taking the ratio of  $V_{oc}$  to  $I_{sc}$ :

$$R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{14 \text{ V}}{0.7 \text{ mA}} = 20 \text{ k}\Omega$$

The short-circuit current is the Norton equivalent current  $I_n$ .


### EXAMPLE 4.22

**Use PSpice to find the Thévenin equivalent voltage  $V_{th}$  and the Thévenin equivalent resistance  $R_{th}$  between  $a$  and  $b$  for the circuit shown in Figure 4.156.**


The Thévenin equivalent voltage is  $V_{th} = -3.053 \text{ V}$ , as shown in Figure 4.157. From the transfer function, we obtain the Thévenin equivalent resistance  $R_{th} = 2.175 \text{ k}\Omega$ , as shown here.

*continued*

Example 4.22 continued

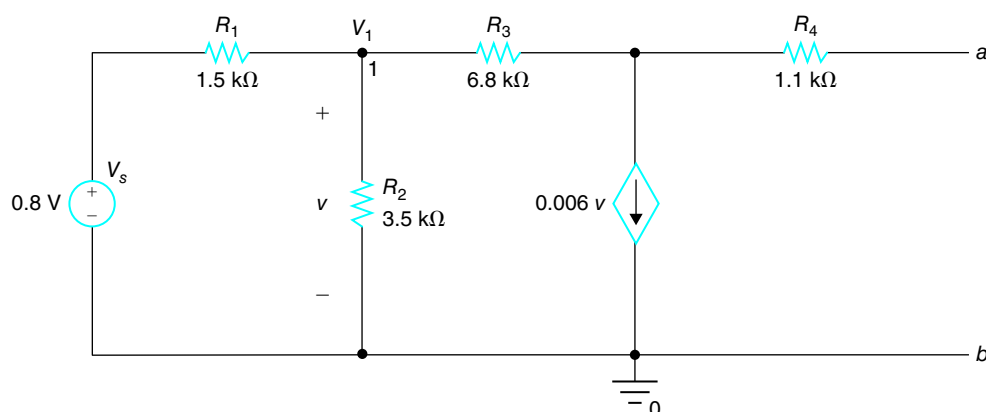**FIGURE 4.156**Circuit for  
EXAMPLE 4.22.**FIGURE 4.157**

Node voltages.

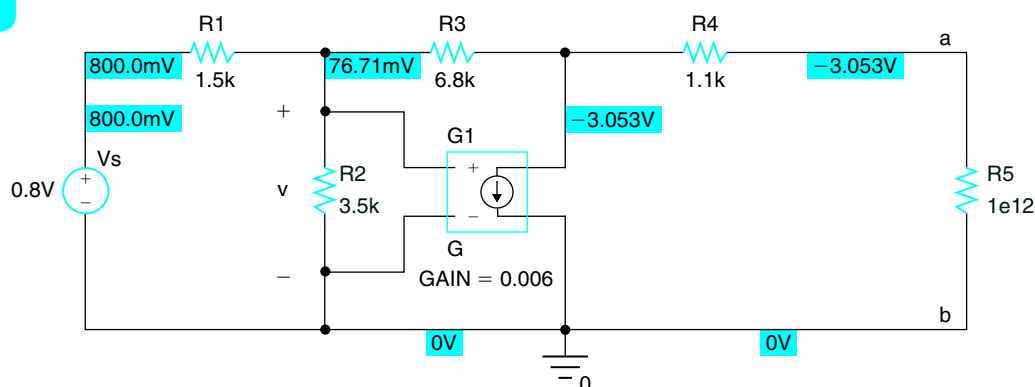

\*\*\*\* SMALL-SIGNAL CHARACTERISTICS

 $V(R\_R5)/V\_Vs = -3.816E+00$ INPUT RESISTANCE AT  $V\_Vs = 1.659E+03$ OUTPUT RESISTANCE AT  $V(R\_R5) = 2.175E+03$ 

### 4.7.1 SIMULINK

Figure 4.158 shows a Simulink model to measure the Thévenin voltage for the circuit shown in Figure 4.151. Figure 4.159 shows a Simulink model to measure the Thévenin resistance for the circuit shown in Figure 4.151. A test voltage of 1 V is applied across the terminals *a* and *b* after deactivating the source. The ratio of the test voltage to the current flowing out of the positive terminal of the test source is the Thévenin resistance. The answer from the model is 20 kΩ.

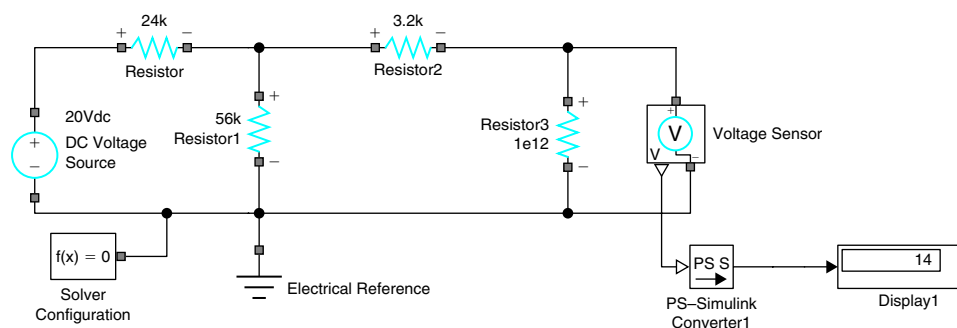
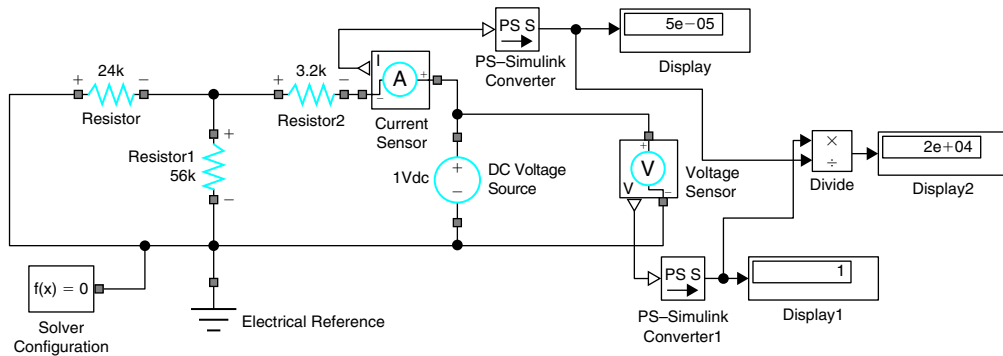
**FIGURE 4.158**A Simulink model  
to measure the  
Thévenin voltage.

FIGURE 4.159

A Simulink model to measure the Thévenin resistance for the circuit shown in Figure 4.151.



## SUMMARY

In this chapter, four important circuit theorems have been presented: the superposition principle, source transformation, Thévenin's theorem, and Norton's theorem. A brief summary is given for each of these theorems.

The *superposition principle* says that if a circuit contains more than one independent source, we can find the response of the circuit from one source at a time while the rest are deactivated and add the responses from individual sources to get the response.

The *source transformation* says that a voltage source with voltage  $V_s$  in series with a resistor with resistance  $R$  can be replaced by a current source with current  $V_s/R$  and a parallel resistor with resistance  $R$ . Also, a current source with current  $I_s$  in parallel with a resistor with resistance  $R$  can be replaced by a voltage source with voltage  $RI_s$  and a series resistor with resistance  $R$ .

*Thévenin's theorem* says that given terminals  $a$  and  $b$ , the circuit looking from the terminals  $a$  and  $b$  can be represented by a voltage source with voltage  $V_{th}$ , called the *Thévenin equivalent voltage*, and a series resistor with resistance  $R_{th}$ , called the *Thévenin equivalent resistance*. The Thévenin equivalent voltage  $V_{th}$  can be found by calculating the open-circuit voltage between terminals  $a$  and  $b$ . There are three methods to find the Thévenin equivalent resistance  $R_{th}$ . The first method is to find the equivalent resistance looking into the circuit from terminals  $a$  and  $b$  after deactivating independent sources. The second method is to find the short-circuit current from  $a$  to  $b$ , and to take the ratio of the open-circuit voltage to the short-circuit current (i.e.,  $R_{th} = V_{oc}/I_{sc}$ ). The third method is to apply a test voltage from  $a$  to  $b$  into the circuit after deactivating the independent sources, measure the current flowing out of the positive terminal of the test voltage source, and then take the ratio of the voltage to current. Alternatively, a test current can be applied to the circuit from terminals  $a$  and  $b$  after deactivating the independent sources. Then,

measure the voltage across the test current source. The Thévenin equivalent resistance is the ratio of the voltage to current.

*Norton's theorem* says that given terminals  $a$  and  $b$ , the circuit looking from the terminals  $a$  and  $b$  can be represented by a current source with current  $I_n$ , called the *Norton equivalent current*, and a parallel resistor with resistance  $R_n$ , called the *Norton equivalent resistance*. The Norton equivalent current  $I_n$  can be found by calculating the short-circuit current from  $a$  to  $b$ . There are three methods to find the Norton equivalent resistance  $R_n$ . The first method is to find the equivalent resistance looking into the circuit from terminals  $a$  and  $b$  after deactivating independent sources. The second method is to find the open-circuit voltage between terminals  $a$  and  $b$ , and to take the ratio of the open-circuit voltage to the short-circuit current (i.e.,  $R_n = V_{oc}/I_{sc}$ ). The third method is to apply a test voltage from  $a$  to  $b$  into the circuit after deactivating the independent sources, measure the current flowing out of the positive terminal of the test voltage source, and then take the ratio of the voltage to current. Alternatively, a test current can be applied to the circuit from terminals  $a$  and  $b$  after deactivating the independent sources. Then, measure the voltage across the test current source. The Norton equivalent resistance is the ratio of the voltage to the current.


Suppose that a load with resistance  $R_L$  is connected to a circuit between terminals  $a$  and  $b$ . We are interested in finding the load resistance  $R_L$  that maximizes the power delivered to the load. We first find the Thévenin equivalent circuit with respect to the terminals  $a$  and  $b$ . Let  $V_{th}$  be the Thévenin equivalent voltage and  $R_{th}$  be the Thévenin equivalent resistance. Then, the load resistance  $R_L$  that maximizes the power delivered to the load is given by the Thévenin equivalent resistance from terminals  $a$  and  $b$ .

## PROBLEMS

### Superposition Principle


**4.1** Use the superposition principle to find voltage  $V_1$  in the circuit shown in Figure P4.1.

**FIGURE P4.1**

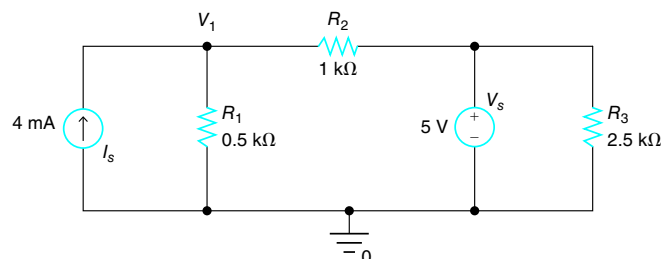


**4.2** Use the superposition principle to find voltage  $V_1$  in the circuit shown in Figure P4.2.

**FIGURE P4.2**

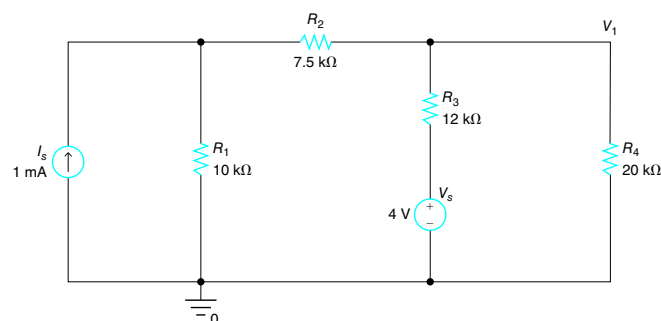


**4.3** Use the superposition principle to find voltage  $V_1$  in the circuit shown in Figure P4.3.

**FIGURE P4.3**

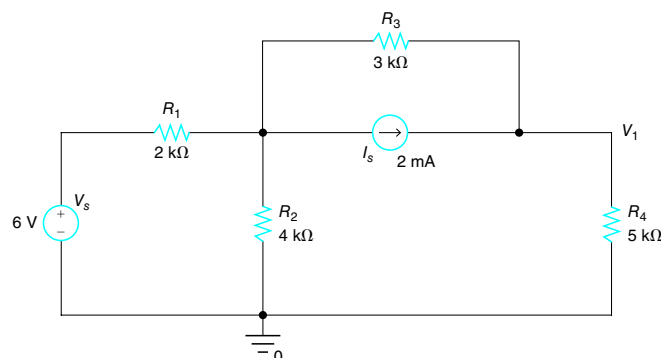


**4.4** Use the superposition principle to find voltage  $V_1$  in the circuit shown in Figure P4.4.

**FIGURE P4.4**

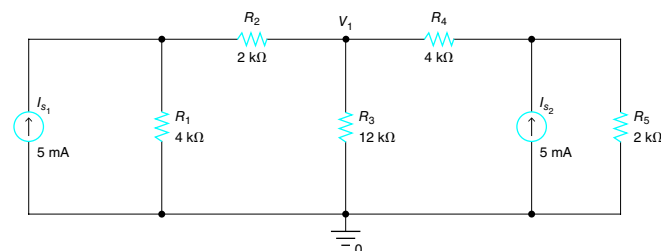


**4.5** Use the superposition principle to find voltage  $V_1$  in the circuit shown in Figure P4.5.

**FIGURE P4.5**

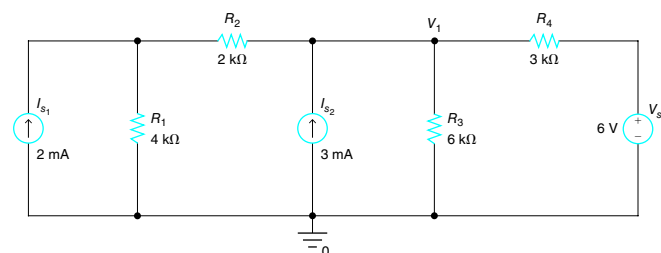


**4.6** Use the superposition principle to find voltages  $V_1$  and  $V_2$  in the circuit shown in Figure P4.6.

**FIGURE P4.6**

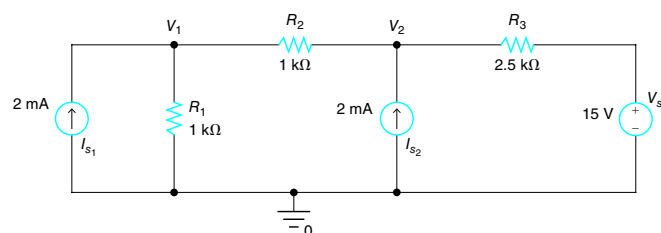


**4.7** Use the superposition principle to find voltages  $V_1$  and  $V_2$  in the circuit shown in Figure P4.7.

**FIGURE P4.7**

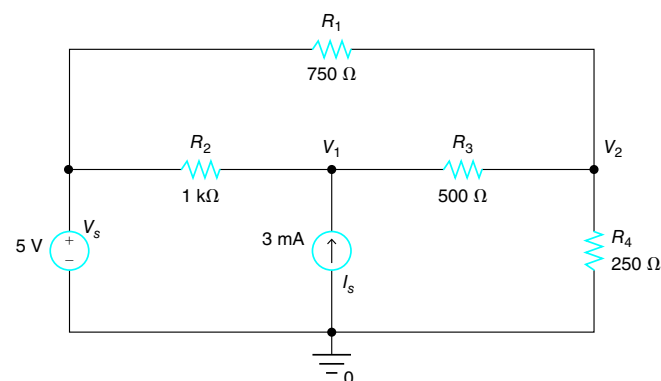


**4.8** Use the superposition principle to find voltages  $V_1$ ,  $V_2$ , and  $V_3$  in the circuit shown in Figure P4.8.

**FIGURE P4.8**

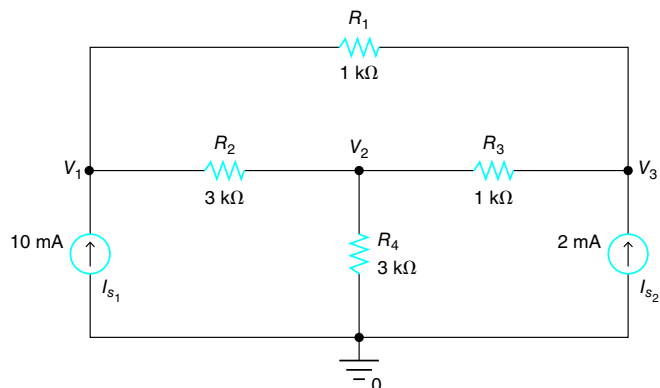


**4.9** Use the superposition principle to find voltages  $V_1$  and  $V_2$  in the circuit shown in Figure P4.9.

**FIGURE P4.9**

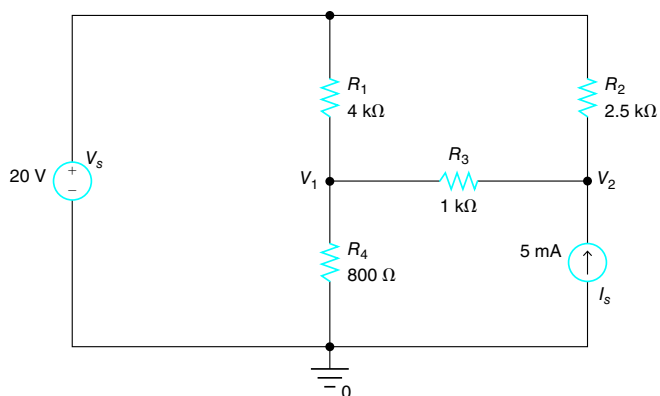


**4.10** Use the superposition principle to find voltages  $V_1$ ,  $V_2$ , and  $V_3$  in the circuit shown in Figure P4.10.

**FIGURE P4.10**

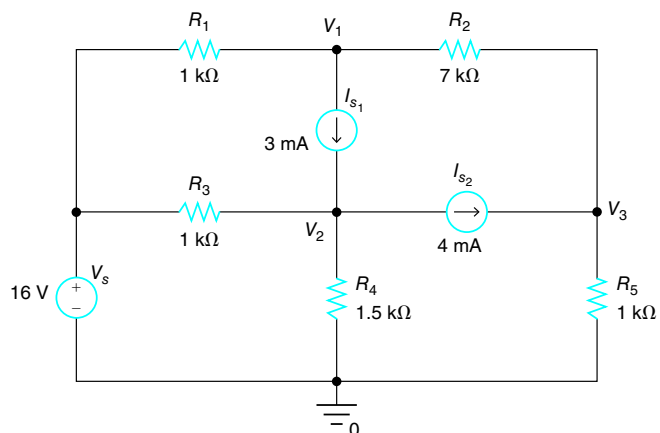


**4.11** Use the superposition principle to find voltages  $V_1$  and  $V_2$  in the circuit shown in Figure P4.11.

**FIGURE P4.11**

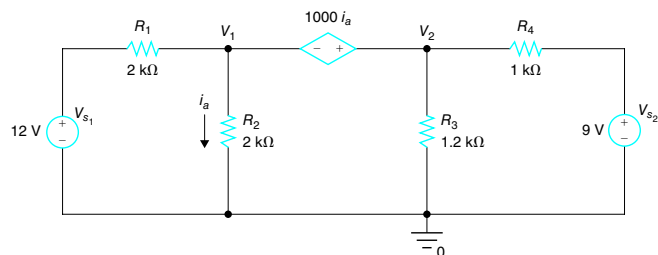


**4.12** Use the superposition principle to find voltages  $V_1$  and  $V_2$  in the circuit shown in Figure P4.12.

**FIGURE P4.12**

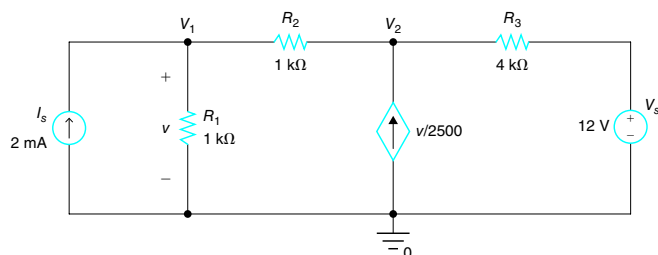


**4.13** Use the superposition principle to find voltages  $V_1$  and  $V_2$  in the circuit shown in Figure P4.13.

**FIGURE P4.13**

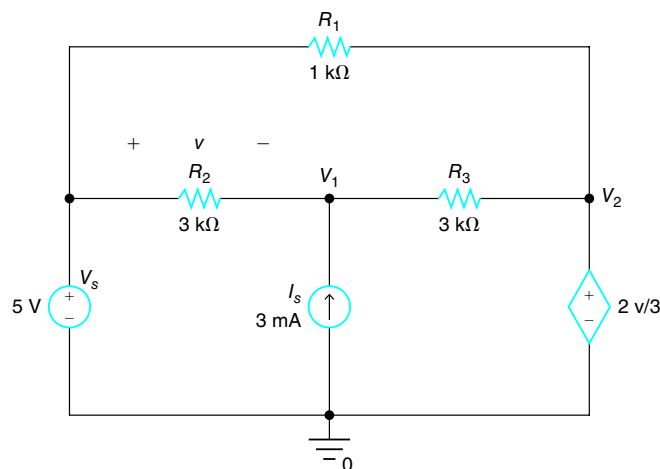


**4.14** Use the superposition principle to find voltages  $V_1$ ,  $V_2$ , and  $V_3$  in the circuit shown in Figure P4.14.

**FIGURE P4.14**

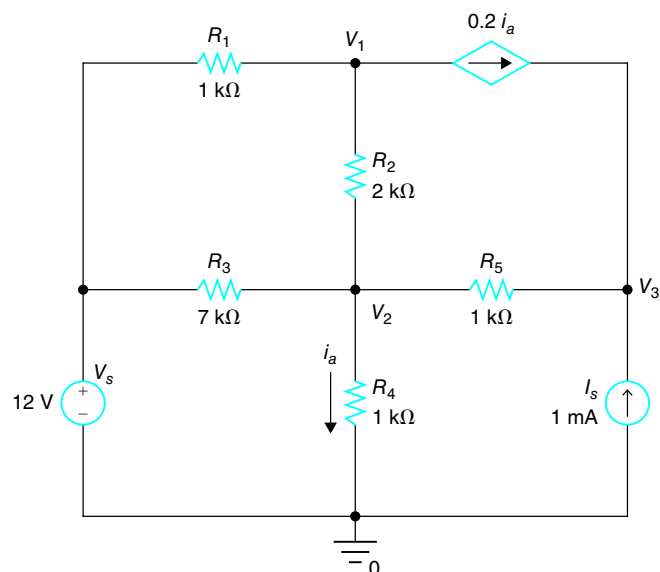

**4.15** Use the superposition principle to find voltages  $V_1$ ,  $V_2$ , and  $V_3$  in the circuit shown in Figure P4.15.


**FIGURE P4.15**

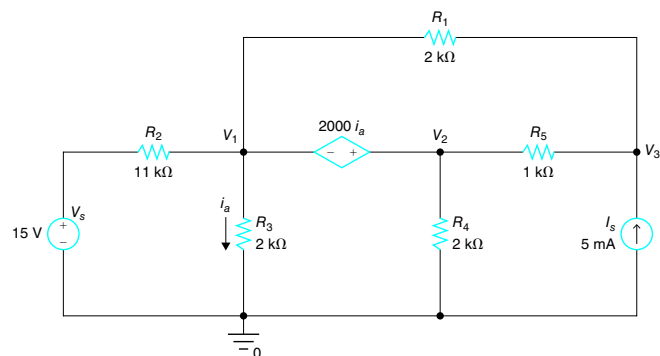

### Source Transformation


**4.16** Use source transformation to find voltages  $V_1$  and  $V_2$  in the circuit shown in Figure P4.16.

**FIGURE P4.16**

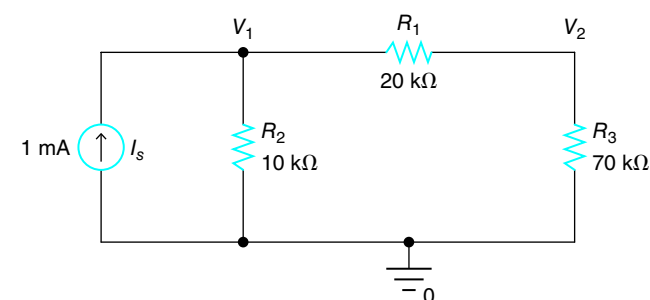


**4.17** Use source transformation to find currents  $I_1$  and  $I_2$  in the circuit shown in Figure P4.17.

**FIGURE P4.17**

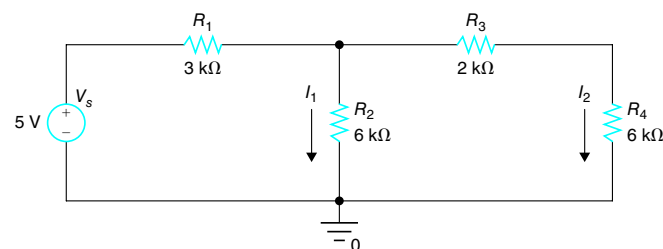


**4.18** Use source transformation to find voltage  $V_o$  in the circuit shown in Figure P4.18.

**FIGURE P4.18**

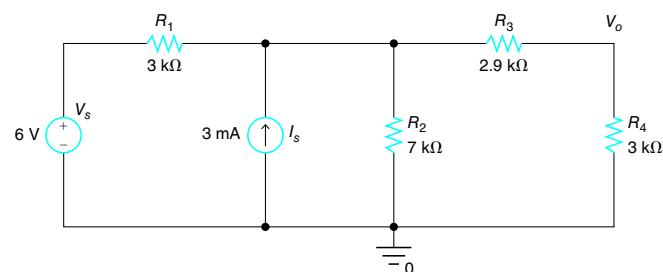


**4.19** Use source transformation to find voltage  $V_o$  in the circuit shown in Figure P4.19.

**FIGURE P4.19**

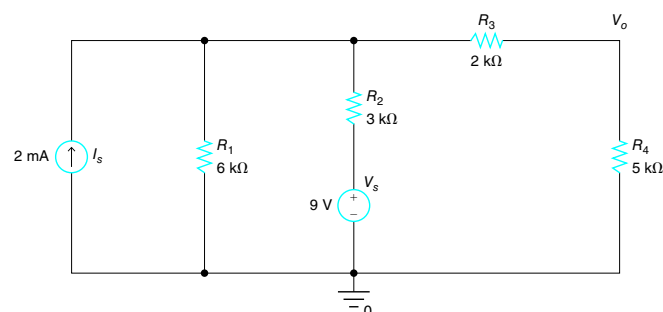

**4.20** Use source transformation to find voltage  $V_o$  in the circuit shown in Figure P4.20.


**FIGURE P4.20**

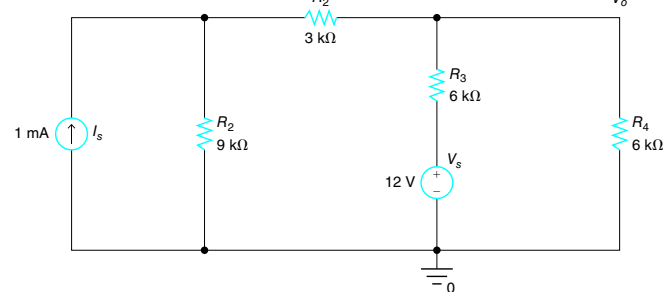




**4.21** Use source transformation to find voltage  $V_o$  in the circuit shown in Figure P4.21.

**FIGURE P4.21**

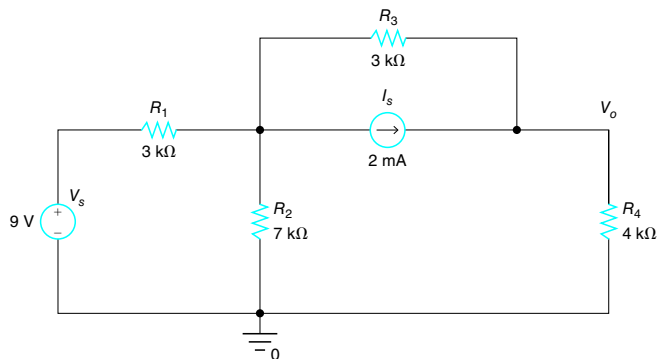


**4.22** Use source transformation to find voltage  $V_o$  in the circuit shown in Figure P4.22.

**FIGURE P4.22**

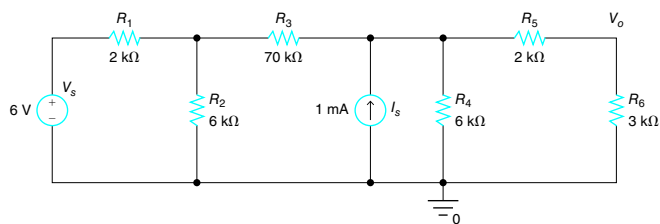


**4.23** Use source transformation to find voltage  $V_o$  in the circuit shown in Figure P4.23.

**FIGURE P4.23**

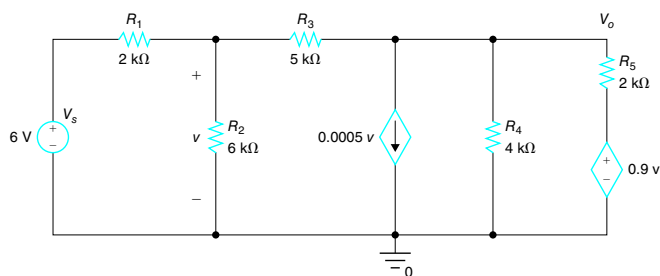


**4.24** Use source transformation to find voltages  $V_1$ ,  $V_2$ , and  $V_3$  in the circuit shown in Figure P4.24.

**FIGURE P4.24**

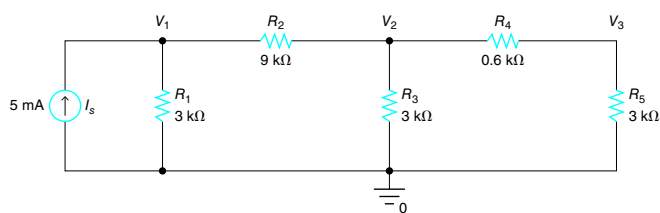


**4.25** Use source transformation to find voltages  $V_1$  and  $V_2$  in the circuit shown in Figure P4.25.

**FIGURE P4.25**

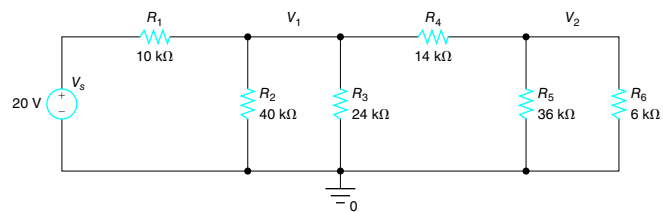


**4.26** Use source transformation to find voltages  $V_1$ ,  $V_2$ , and  $V_3$  in the circuit shown in Figure P4.26.

**FIGURE P4.26**

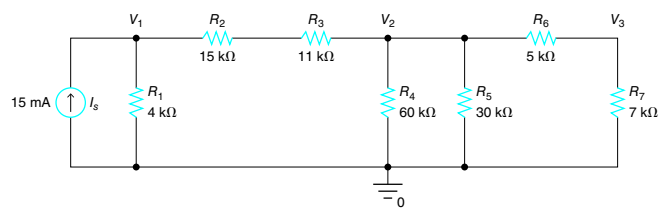


**4.27** Use source transformation to find voltages  $V_1$ ,  $V_2$ , and  $V_3$  in the circuit shown in Figure P4.27.

**FIGURE P4.27**

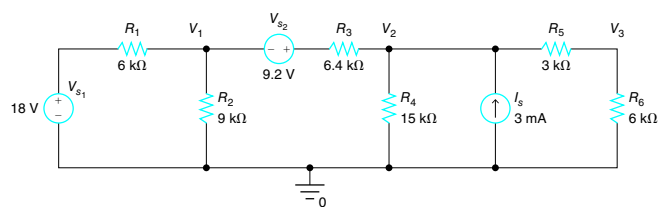


**4.28** Use source transformation to find voltages  $V_1$ ,  $V_2$ ,  $V_3$ , and  $V_4$  in the circuit shown in Figure P4.28.

**FIGURE P4.28**

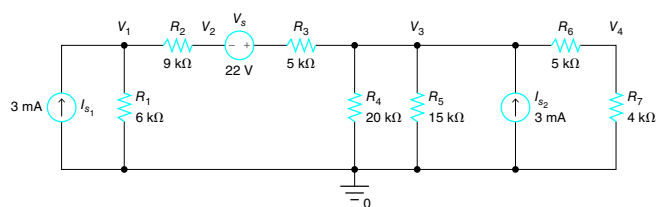


**4.29** Use source transformation to find voltages  $V_1$ ,  $V_2$ , and  $V_3$  in the circuit shown in Figure P4.29.

**FIGURE P4.29**

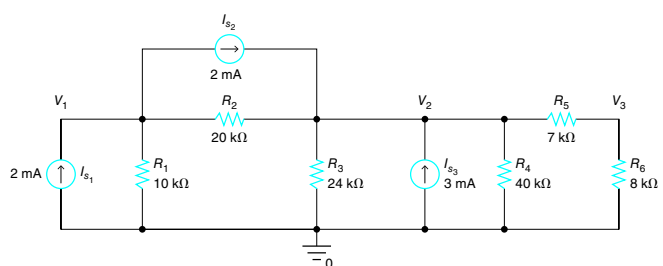

- 4.30** Use source transformation to find voltages  $V_1$ ,  $V_2$ , and  $V_3$  in the circuit shown in Figure P4.30.


FIGURE P4.30

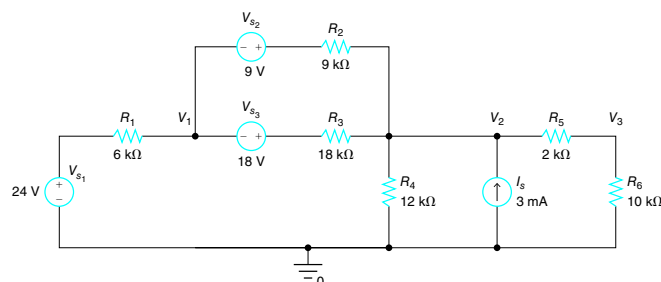

### Thévenin Equivalent Circuit


- 4.31** Find the Thévenin equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.31.

FIGURE P4.31

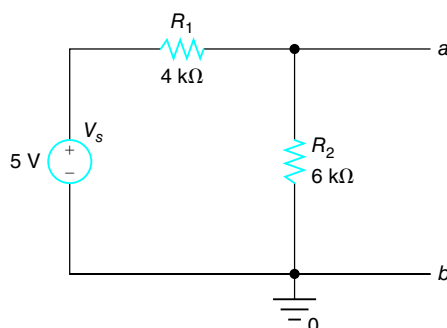


- 4.32** Find the Thévenin equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.32.

FIGURE P4.32

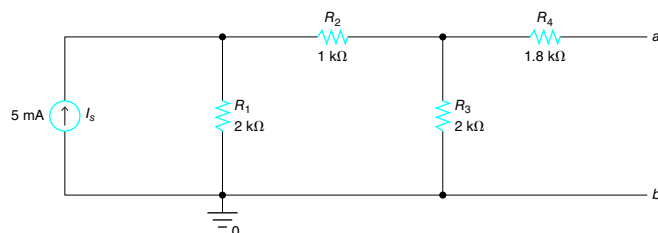


- 4.33** Find the Thévenin equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.33.

FIGURE P4.33

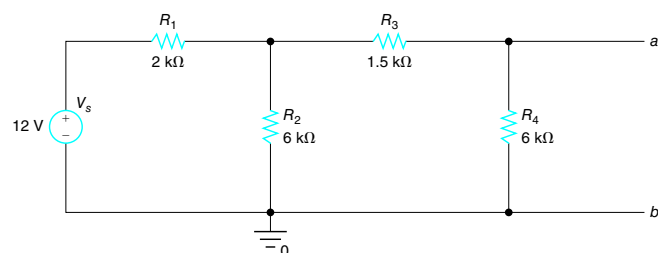


- 4.34** Find the Thévenin equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.34.

FIGURE P4.34

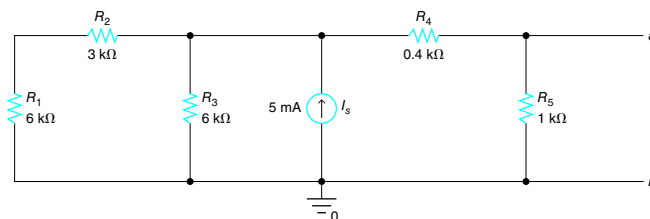


- 4.35** Find the Thévenin equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.35.

FIGURE P4.35

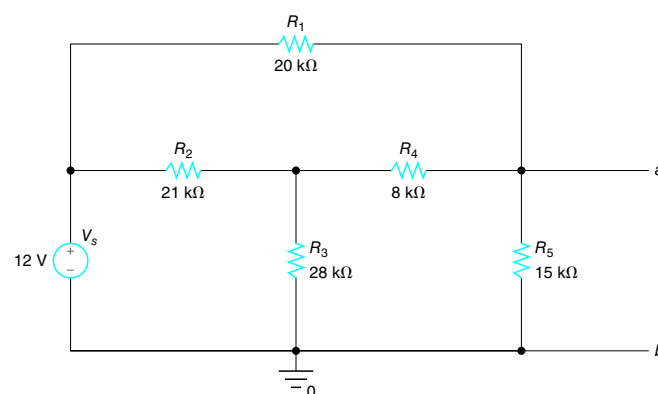


- 4.36** Find the Thévenin equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.36.

FIGURE P4.36

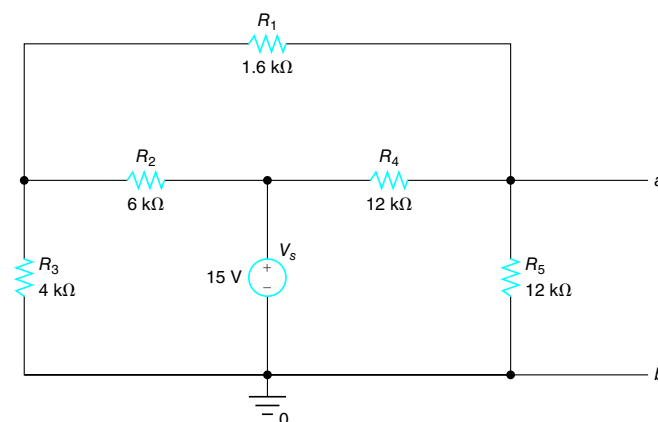


**4.37** Find the Thévenin equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.37.

FIGURE P4.37

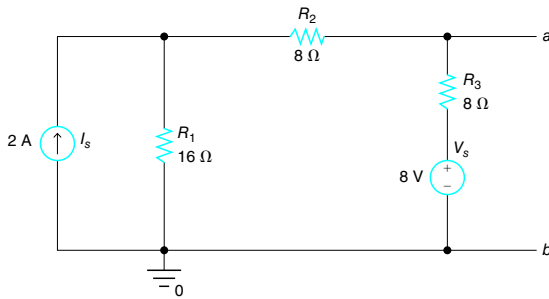


**4.38** Find the Thévenin equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.38.

FIGURE P4.38

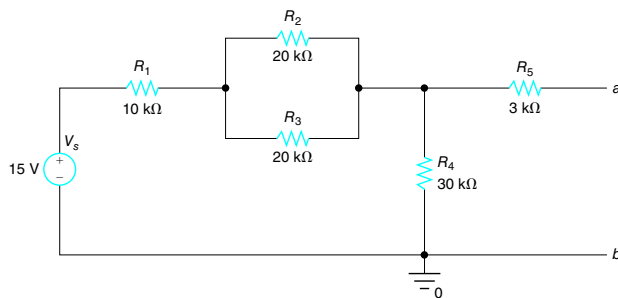


**4.39** Find the Thévenin equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.39.

FIGURE P4.39

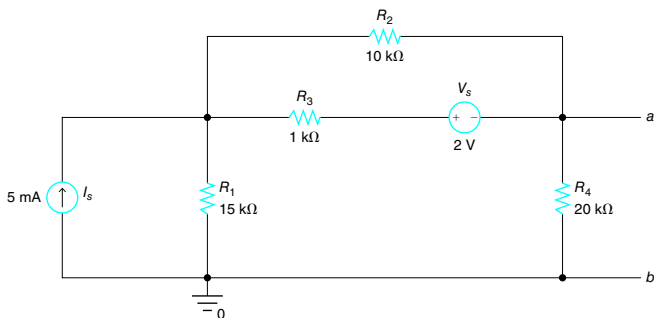


**4.40** Find the Thévenin equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.40.

FIGURE P4.40

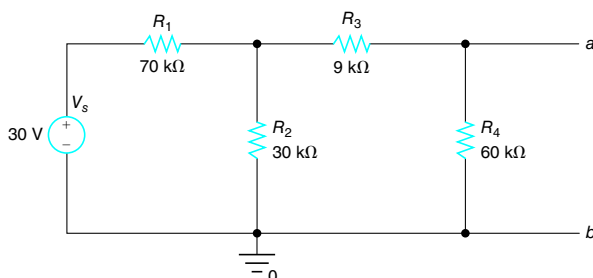


**4.41** Find the Thévenin equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.41.

FIGURE P4.41

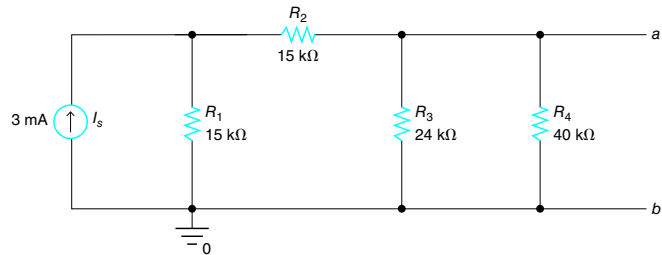


**4.42** Find the Thévenin equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.42.

FIGURE P4.42

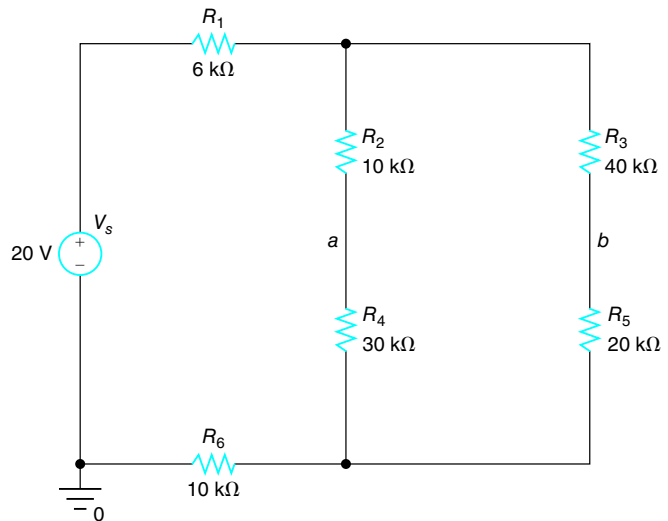


**4.43** Find the Thévenin equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.43.

FIGURE P4.43

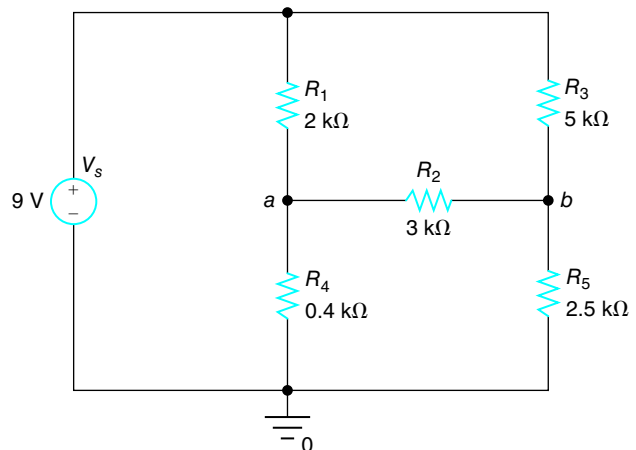


**4.44** Find the Thévenin equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.44.

**FIGURE P4.44**

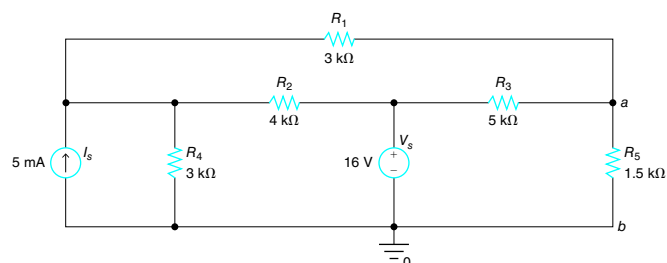


**4.45** Find the Thévenin equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.45.

**FIGURE P4.45**

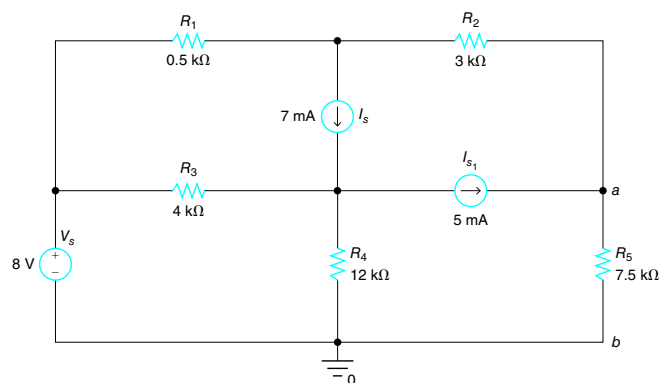


**4.46** Find the Thévenin equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.46.

**FIGURE P4.46**

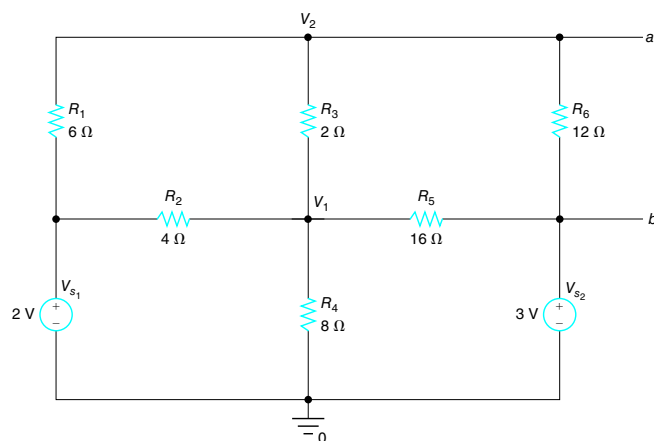


**4.47** Find the Thévenin equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.47.

**FIGURE P4.47**

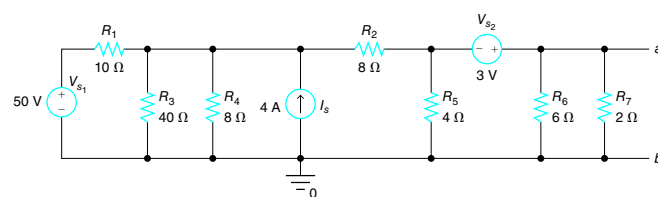


**4.48** Find the Thévenin equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.48.

**FIGURE P4.48**

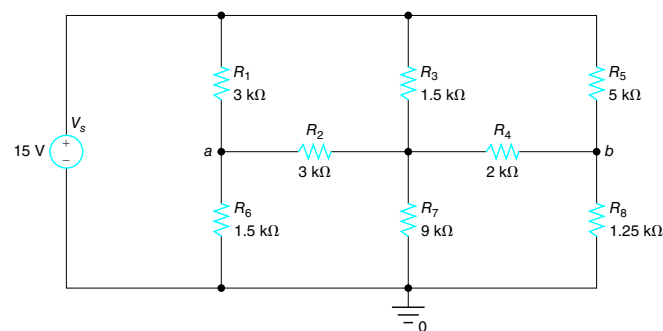


**4.49** Find the Thévenin equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.49.

**FIGURE P4.49**

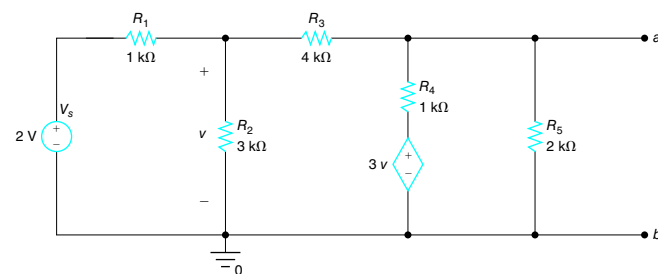


**4.50** Find the Thévenin equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.50.

**FIGURE P4.50**

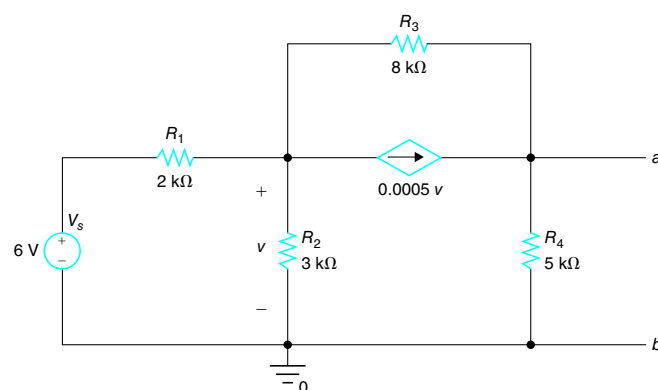


**4.51** Find the Thévenin equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.51.

FIGURE P4.51

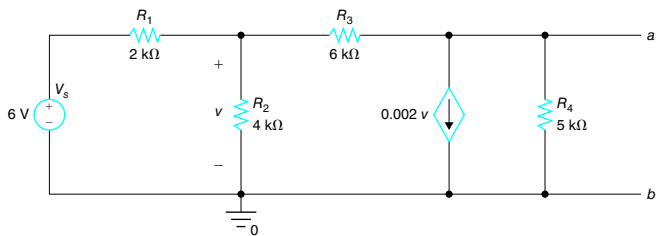


**4.52** Find the Thévenin equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.52.

FIGURE P4.52

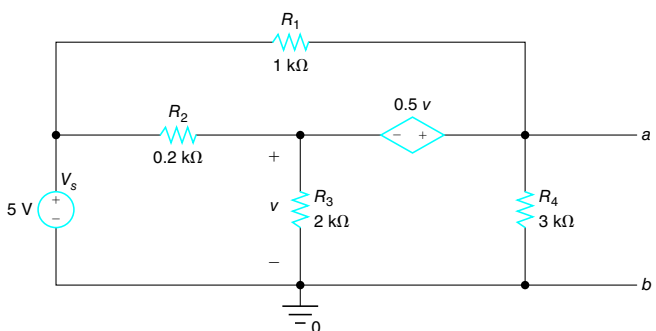


**4.53** Find the Thévenin equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.53.

FIGURE P4.53

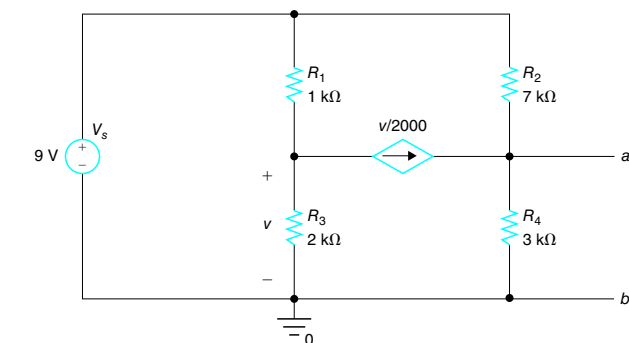


**4.54** Find the Thévenin equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.54.

FIGURE P4.54

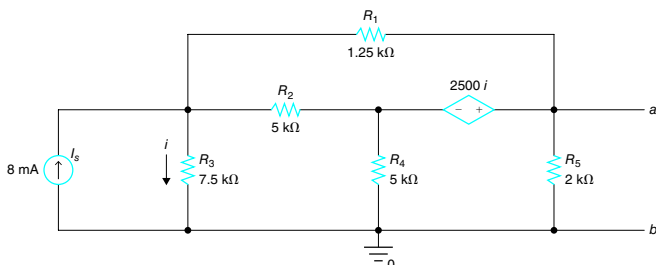


**4.55** Find the Thévenin equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.55.

FIGURE P4.55

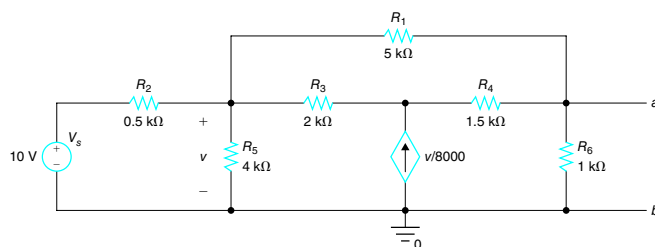


**4.56** Find the Thévenin equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.56.

FIGURE P4.56

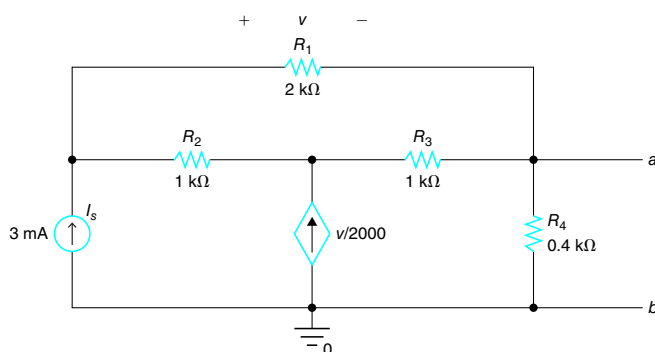


**4.57** Find the Thévenin equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.57.

FIGURE P4.57

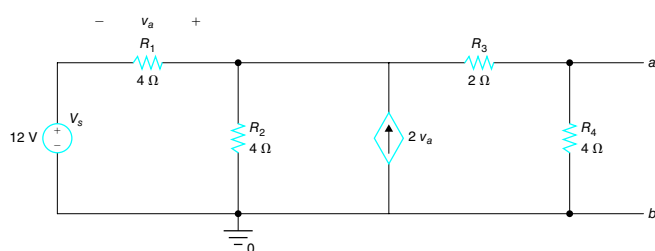


**4.58** Find the Thévenin equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.58.

FIGURE P4.58

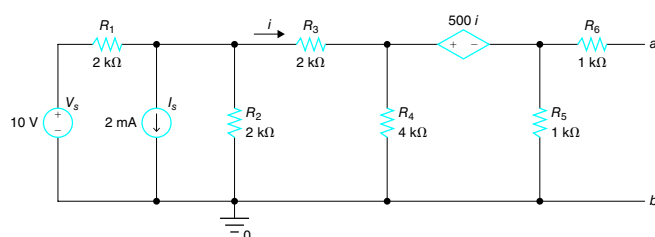


**4.59** Find the Thévenin equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.59.

**FIGURE P4.59**

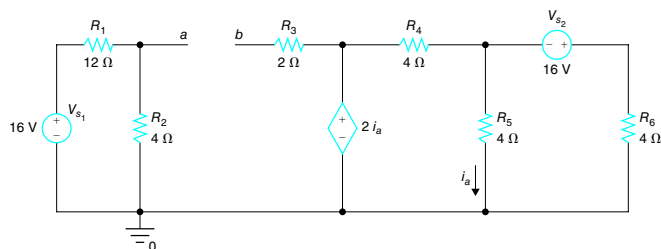


**4.60** Find the Thévenin equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.60.

**FIGURE P4.60**

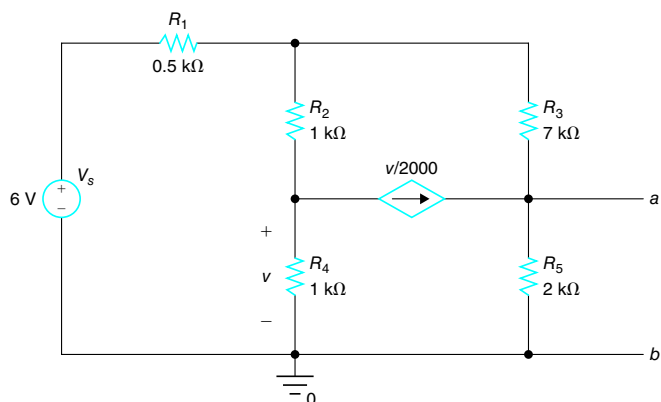


**4.61** Find the Thévenin equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.61.

**FIGURE P4.61**

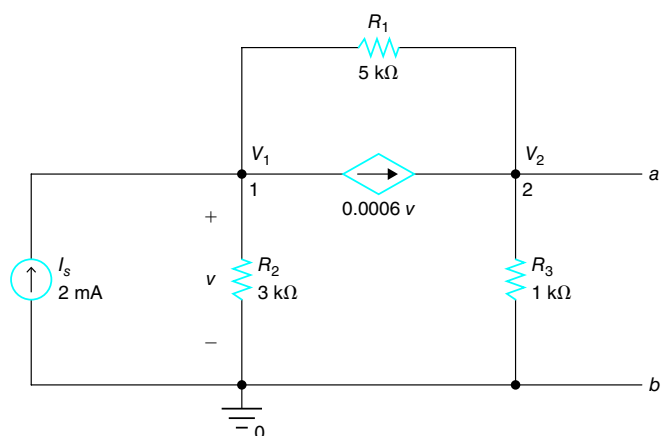

**4.62** Find the Thévenin equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.62.


**FIGURE P4.62**

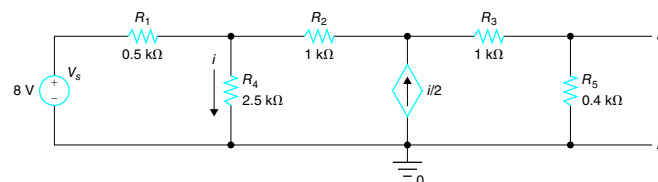

**Norton Equivalent Circuit**


**4.63** Find the Norton equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.63.

**FIGURE P4.63**

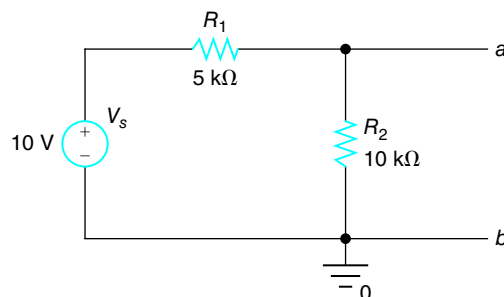


**4.64** Find the Norton equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.64.

**FIGURE P4.64**

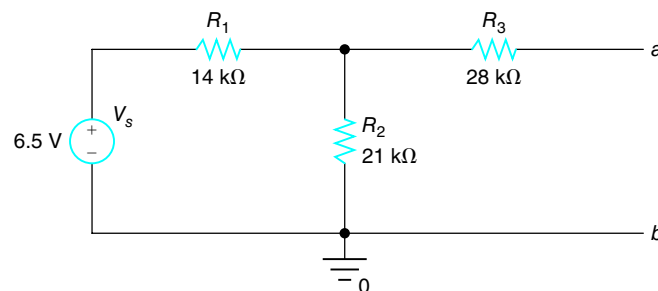


**4.65** Find the Norton equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.65.

**FIGURE P4.65**

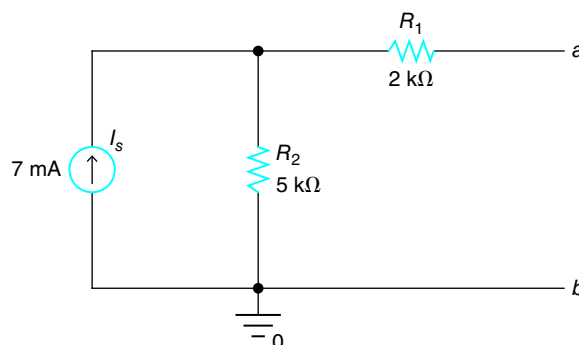


**4.66** Find the Norton equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.66.

FIGURE P4.66

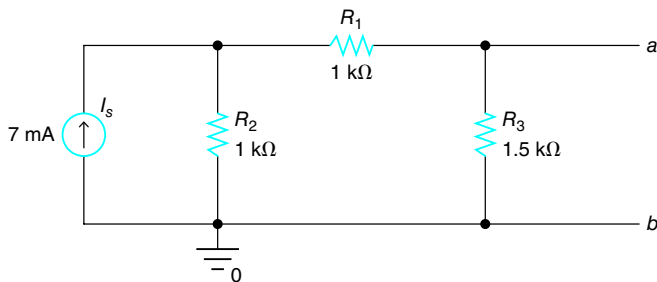


**4.67** Find the Norton equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.67.

FIGURE P4.67

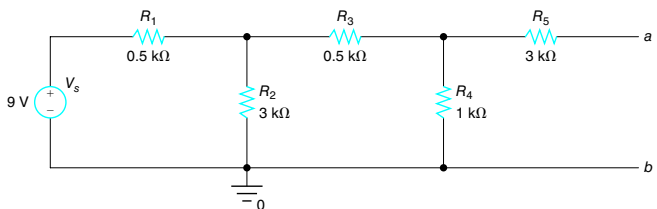


**4.68** Find the Norton equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.68.

FIGURE P4.68

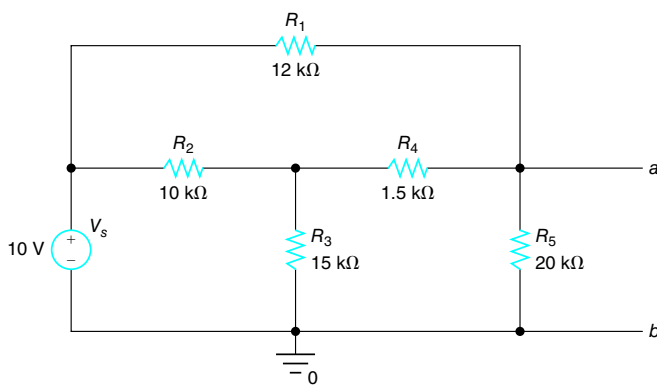


**4.69** Find the Norton equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.69.

FIGURE P4.69

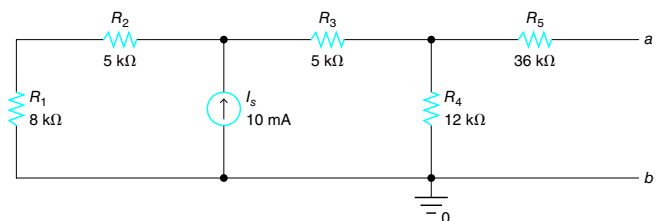


**4.70** Find the Norton equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.70.

FIGURE P4.70

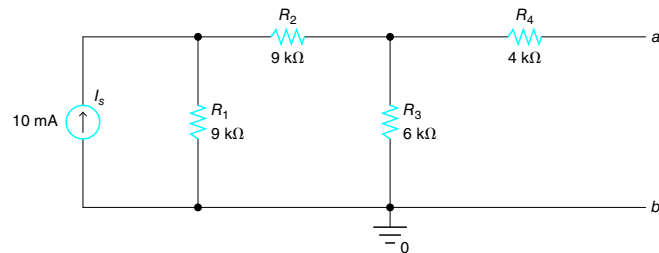


**4.71** Find the Norton equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.71.

FIGURE P4.71

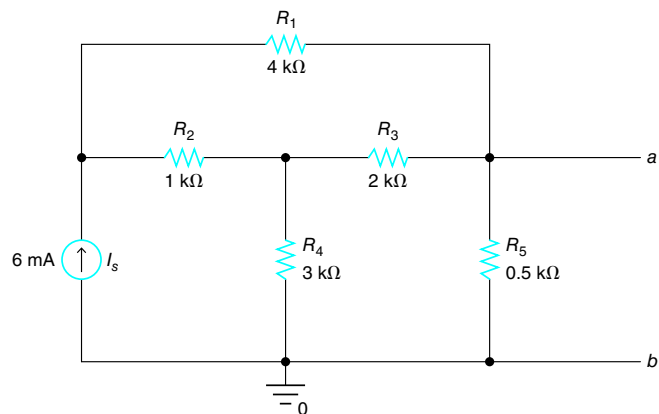


**4.72** Find the Norton equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.72.

FIGURE P4.72

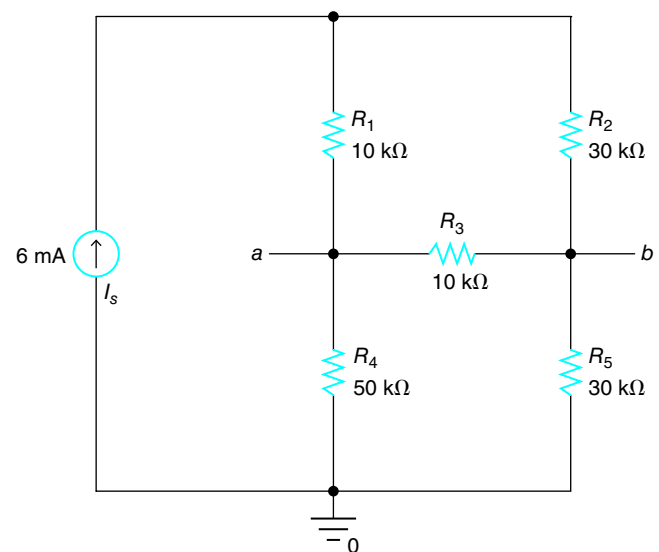


**4.73** Find the Norton equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.73.

FIGURE P4.73

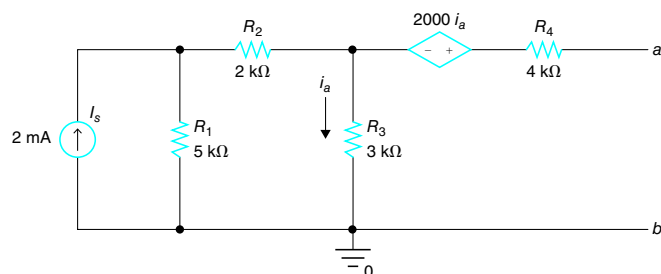


**4.74** Find the Norton equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.74.

FIGURE P4.74

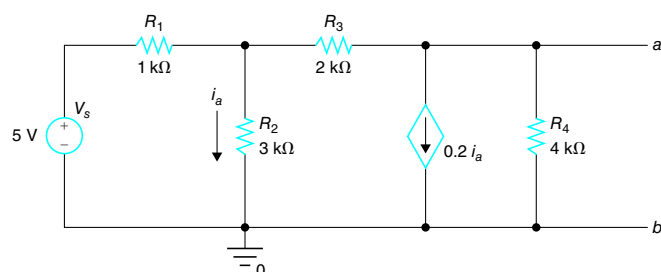


**4.75** Find the Norton equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.75.

FIGURE P4.75

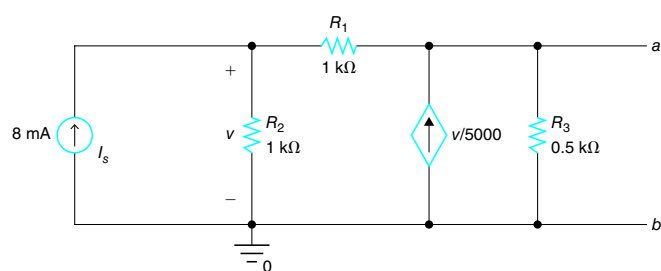


**4.76** Find the Norton equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.76.

FIGURE P4.76

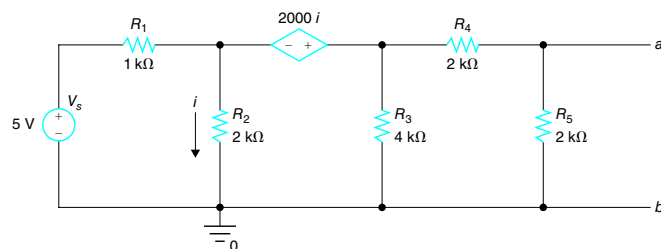

**4.77** Find the Norton equivalent circuit between  $a$  and  $b$  for the circuit shown in Figure P4.77.


FIGURE P4.77

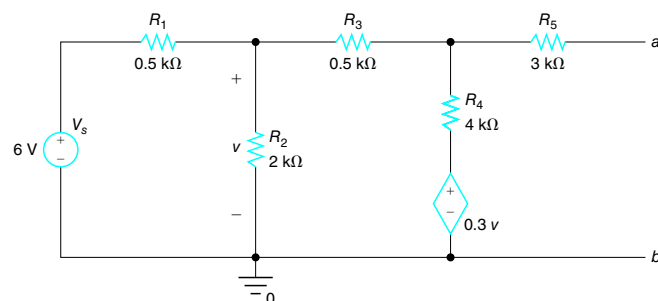

### Maximum Power Transfer


**4.78** Find the load resistance value  $R_L$  for maximum power transfer, and find the maximum power transferred to the load for the circuit shown in Figure P4.78.

FIGURE P4.78

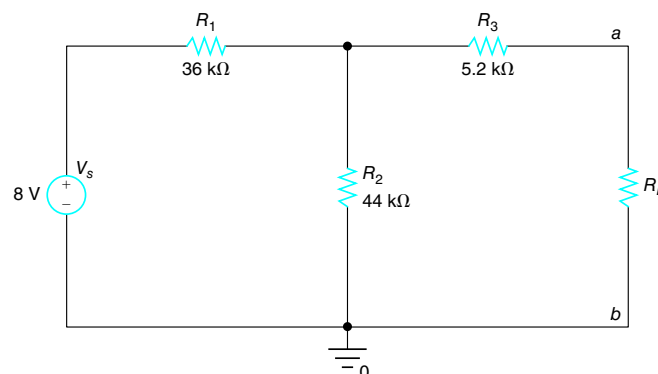

**4.79** Find the load resistance value  $R_L$  for maximum power transfer, and find the maximum power transferred to the load for the circuit shown in Figure P4.79.


FIGURE P4.79

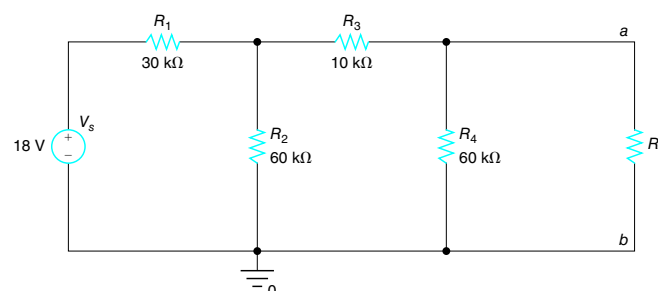




**4.80** Find the load resistance value  $R_L$  for maximum power transfer, and find the maximum power transferred to the load for the circuit shown in Figure P4.80.

FIGURE P4.80

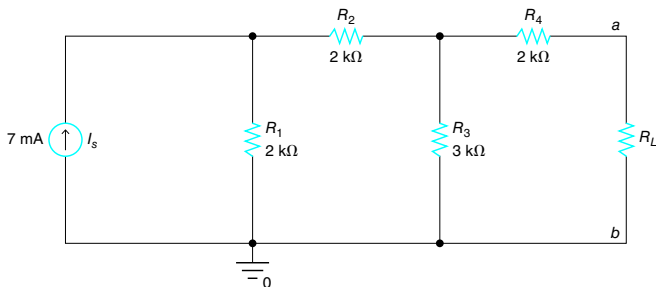


**4.81** Find the load resistance value  $R_L$  for maximum power transfer, and find the maximum power transferred to the load for the circuit shown in Figure P4.81.

FIGURE P4.81

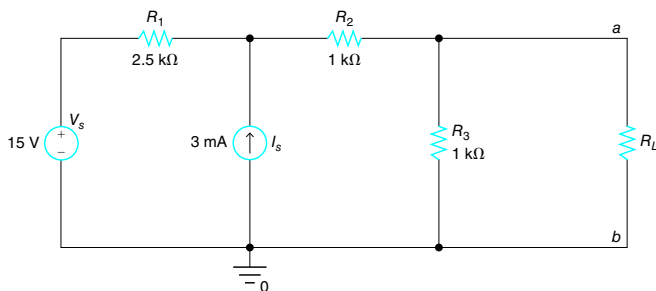


**4.82** Find the load resistance value  $R_L$  for maximum power transfer, and find the maximum power transferred to the load for the circuit shown in Figure P4.82.

FIGURE P4.82

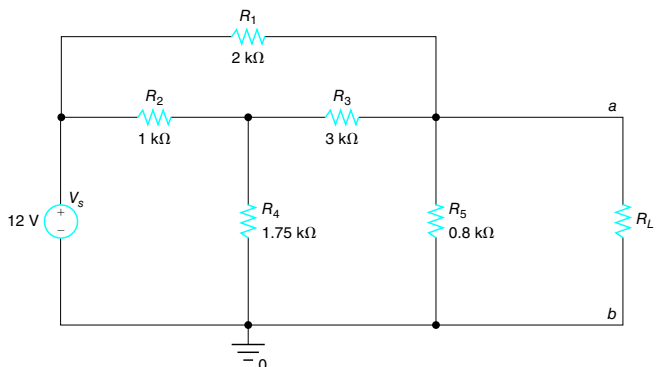


**4.83** Find the load resistance value  $R_L$  for maximum power transfer, and find the maximum power transferred to the load for the circuit shown in Figure P4.83.

FIGURE P4.83

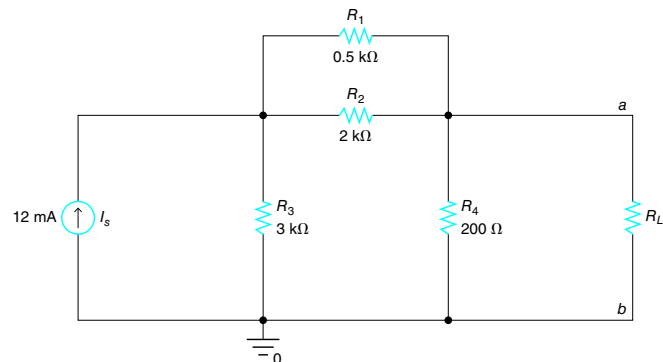


**4.84** Find the load resistance value  $R_L$  for maximum power transfer, and find the maximum power transferred to the load for the circuit shown in Figure P4.84.

FIGURE P4.84

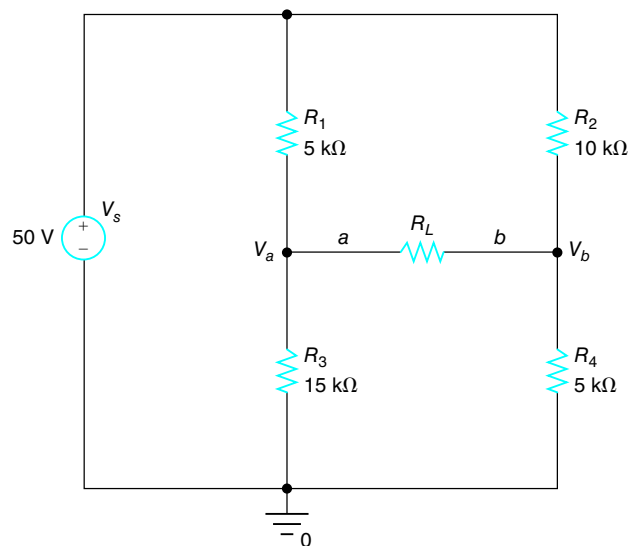


**4.85** Find the load resistance value  $R_L$  for maximum power transfer, and find the maximum power transferred to the load for the circuit shown in Figure P4.85.

FIGURE P4.85

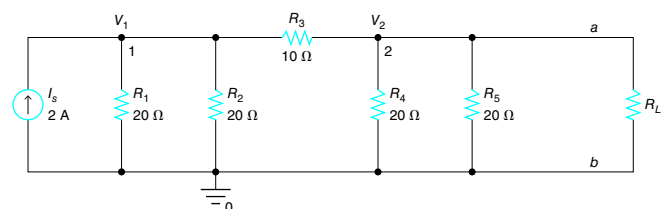


- 4.86** Find the load resistance value  $R_L$  for maximum power transfer, and find the maximum power transferred to the load for the circuit shown in Figure P4.86.

FIGURE P4.86

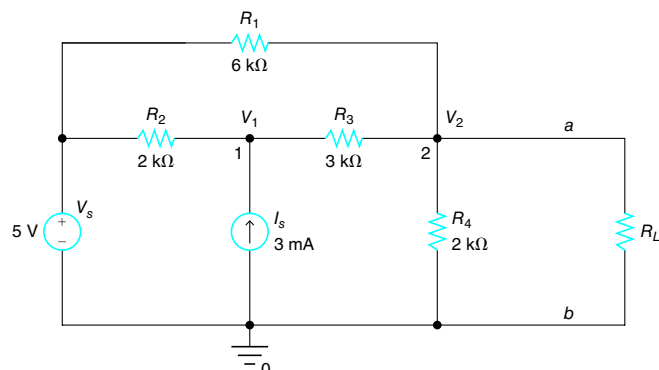


- 4.87** Find the value of  $R_L$  for the maximum power transfer for the circuit shown in Figure P4.87. Also, find the maximum power dissipated at  $R_L$ .

FIGURE P4.87

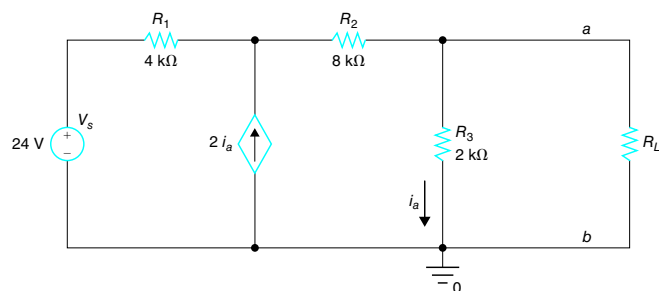


- 4.88** Find the load resistance value  $R_L$  for maximum power transfer, and find the maximum power transferred to the load for the circuit shown in Figure P4.88.

FIGURE P4.88

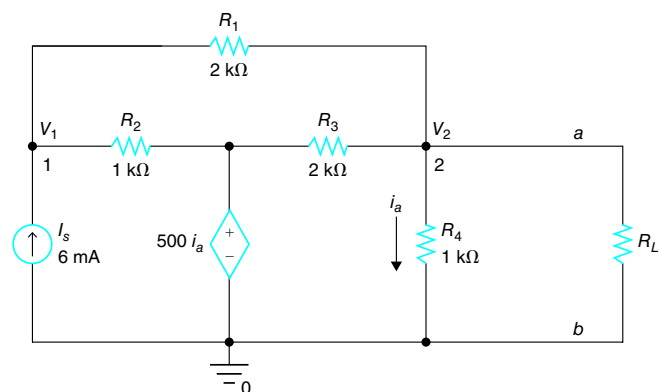

- 4.89** Find the load resistance value  $R_L$  for maximum power transfer, and find the maximum power transferred to the load for the circuit shown in Figure P4.89.

FIGURE P4.89

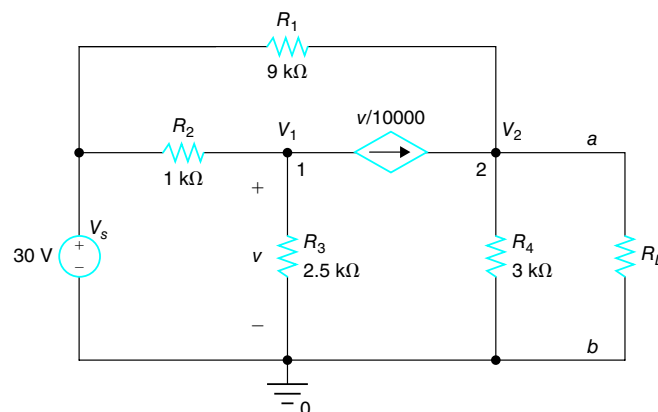

- 4.90** Find the load resistance value  $R_L$  for maximum power transfer, and find the maximum power transferred to the load for the circuit shown in Figure P4.90.

FIGURE P4.90

